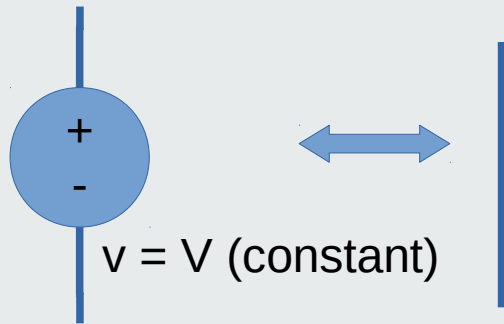


Circuit Theory and Electronics Fundamentals

Lecture 13: Diode circuit properties

- Incremental model of independent and dependent sources
- Incremental impedance of passive components
- Diodes in series
- Diodes in parallel
- Temperature effect
- Optical transmitter/receiver system

Incremental model of independent sources




$$V = \text{constant}$$

$$dv = 0$$

$$r_v = \frac{dv}{di} = 0$$

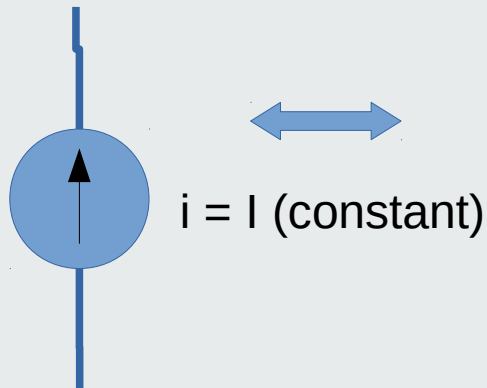An independent voltage source is a short-circuit in incremental terms!




$$i = \text{constant}$$

$$di = 0$$

$$g_i = \frac{di}{dv} = 0 \Rightarrow r_i = \frac{1}{g_i} = \infty$$

An independent current source is an open-circuit in incremental terms!


Incremental model of dependent sources

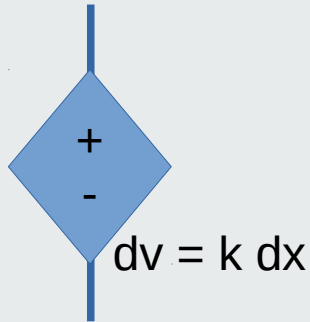

$$v = kx$$

$$dv = k dx$$

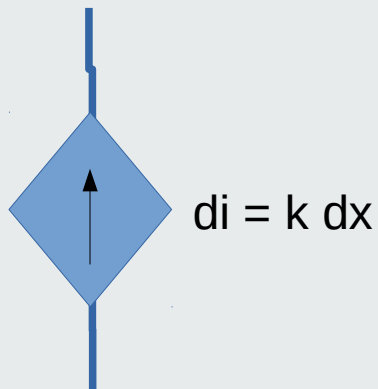Dependent sources remain dependent sources in incremental terms!



$$i = kx$$

$$di = k dx$$


Incremental model of linear passive components



$$v = Ri$$
$$dv = R di$$



$$\phi = Li$$
$$d\phi = L di$$

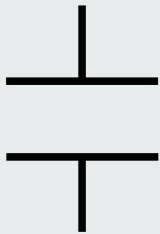

$$q = C v$$
$$dq = C dv$$

Passive linear components unchanged in incremental terms!

Diodes in series


$$i = I_s \left(e^{\frac{v}{\eta V_T}} - 1 \right)$$

Diode equation

$$v = \frac{V_X}{n}$$


All diodes have same voltage because all have same current
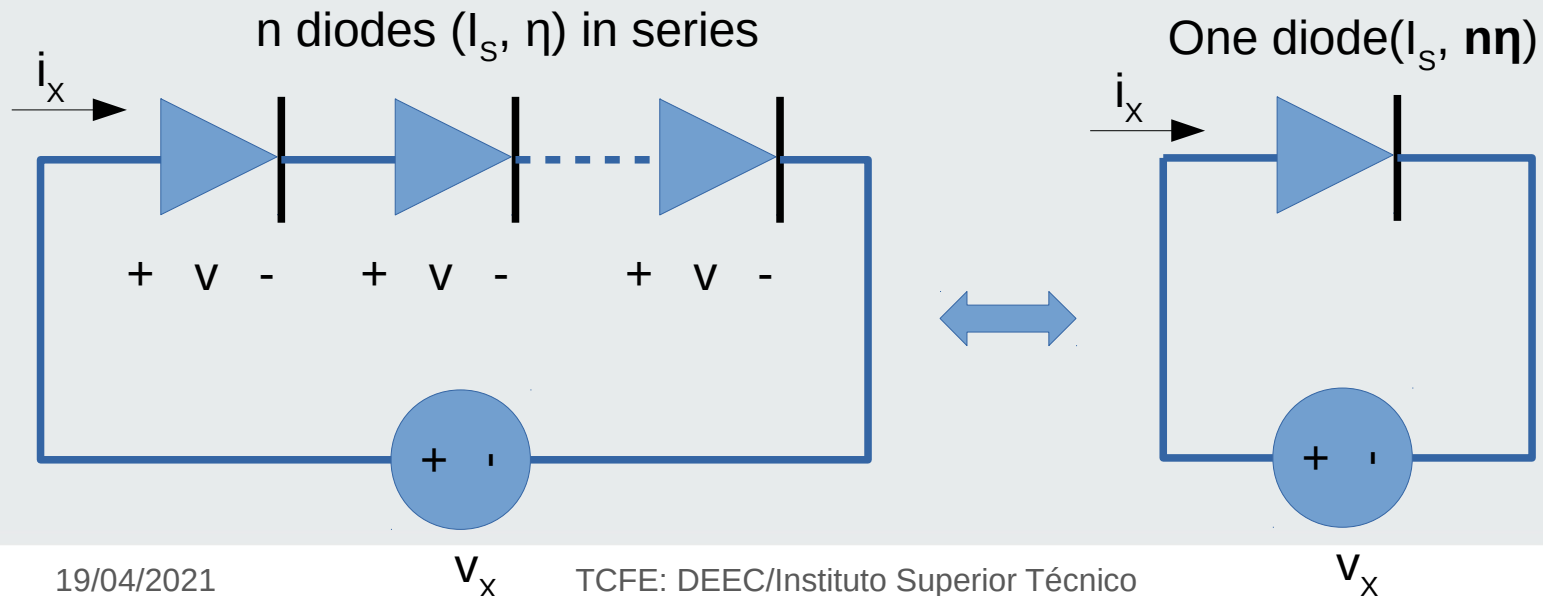
$$i_X = I_s \left(e^{\frac{V_X}{n \eta V_T}} - 1 \right)$$



Diodes in series: incremental resistance
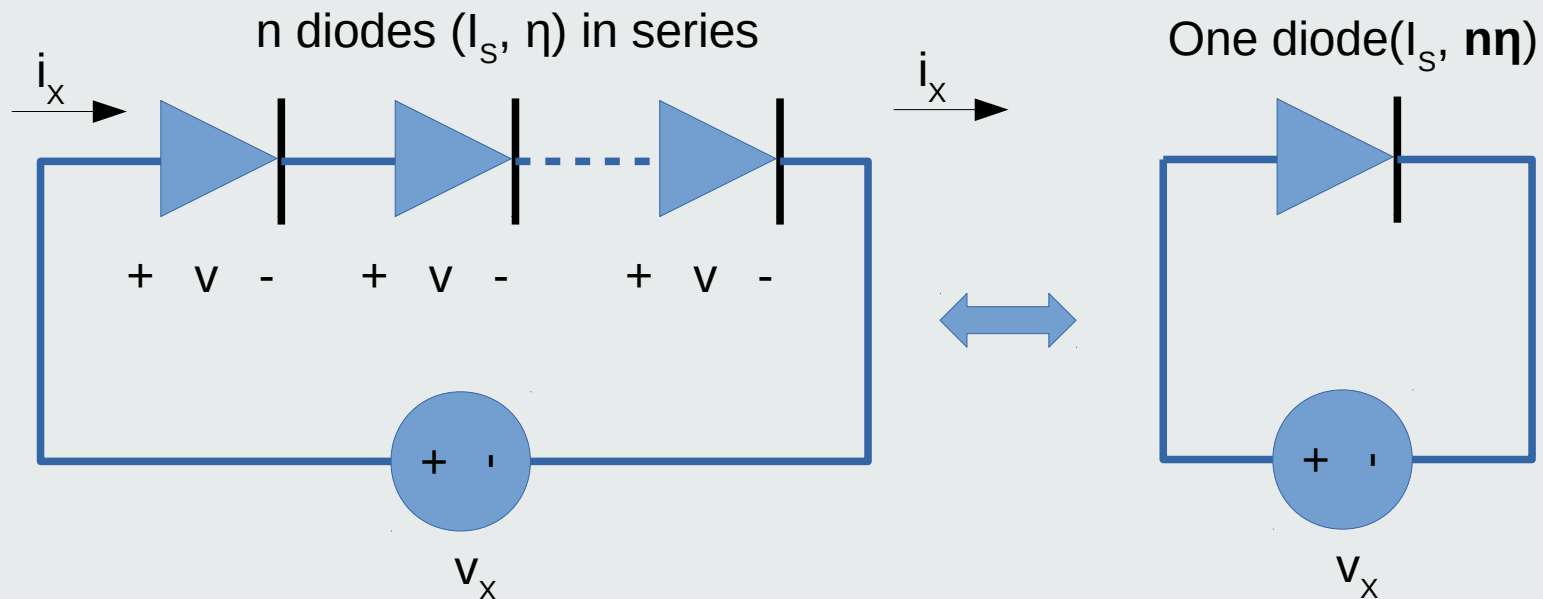
$$r_x = \frac{\eta_X V_T}{\frac{V_X}{I_S e^{\frac{V_X}{\eta_X V_T}}}} = \frac{n \eta V_T}{\frac{n V_D}{I_S e^{\frac{n V_D}{n \eta V_T}}}} = n \frac{\eta V_T}{\frac{V_D}{I_S e^{\frac{V_D}{\eta V_T}}}} = n r_d \quad \text{Series of incremental resistances!}$$



Diodes in parallel

$$i = I_s \left(e^{\frac{v}{\eta V_T}} - 1 \right)$$



Diode equation

$$i_X = n i$$


$$i_X = n I_s \left(e^{\frac{v_X}{\eta V_T}} - 1 \right)$$

All diodes have same current because all have same voltage

n diodes (I_s, η) in parallel

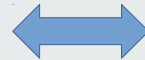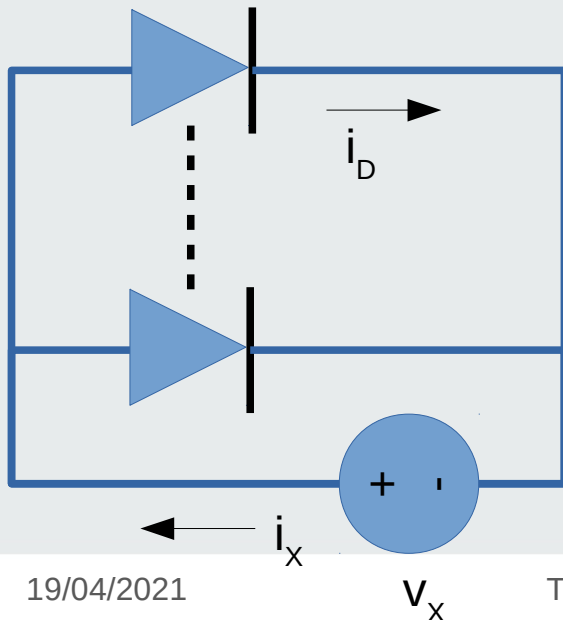




One diode ($n I_s, \eta$)

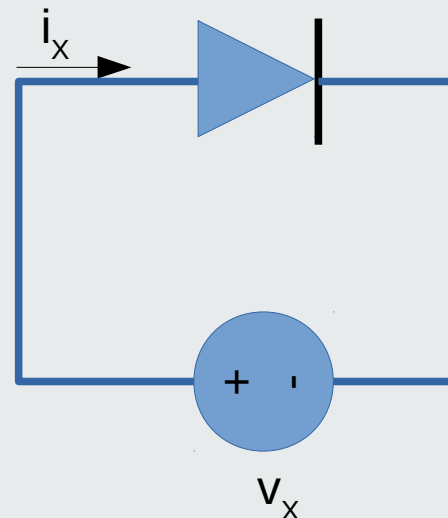

Diodes in parallel: incremental resistance

$$r_x = \frac{\eta_X V_T}{I_{SX} e^{\frac{V_X}{\eta_X V_T}}} = \frac{\eta V_T}{n I_S e^{\frac{V_D}{\eta V_T}}} = \frac{r_d}{n}$$

Parallel of incremental resistances!

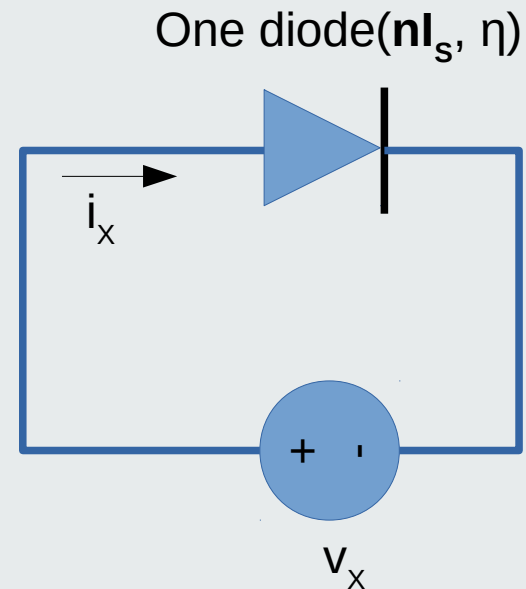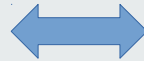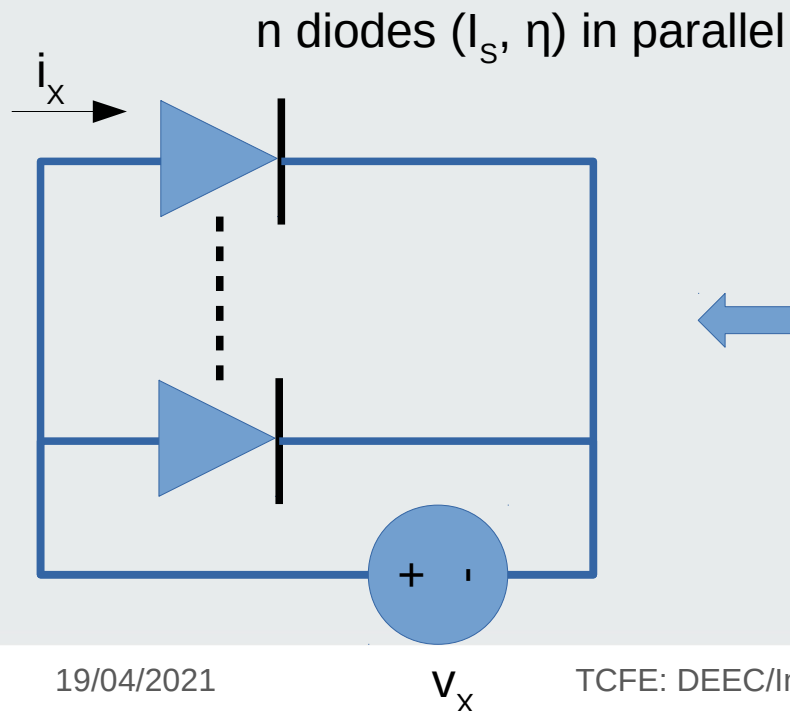

Temperature effect

$$i_D = I_S \left(e^{\frac{v_D}{\eta V_T}} - 1 \right)$$

$$V_T = \frac{kT}{q} \quad V_T \text{ increase lowers current}$$

$$I_S = q S n_i^2 \left(\frac{1}{N_D} \sqrt{\frac{D_p}{\tau_p}} + \frac{1}{N_A} \sqrt{\frac{D_n}{\tau_n}} \right)$$

$$I_S \propto 2^{\frac{T}{10}}$$

Each 10°C doubles the current I_S
 Stronger effect than decrease due to V_T


- N_D : Donor (impurity that **D**onates electrons) concentration in n-side
 N_A : Acceptor (impurity that **A**ccept electrons) concentration in p-side
 S : Junction cross-sectional area
 D_p : Diffusion coefficients for holes and electrons – T dependent
 D_n :
 τ_p : Lifetime for holes and electrons – also T dependent
 τ_n :

- The diode equation suggests the current decreases exponentially with the temperature
- But I_S is a complex function of the temperature...
 - Quantum mechanics
 - Statistical mechanics

Conclusion: diode current increases with T


Temperature risk

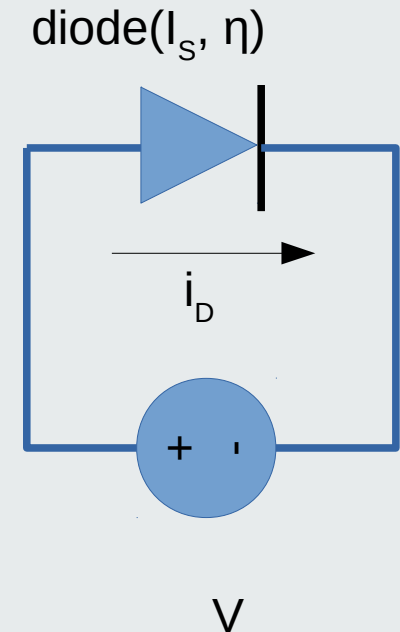- Temperature increases I_s
- I_s increases i_D
- Excess current can heat up and burn material
- Protect your material!



Diode protection resistor from temperature effect

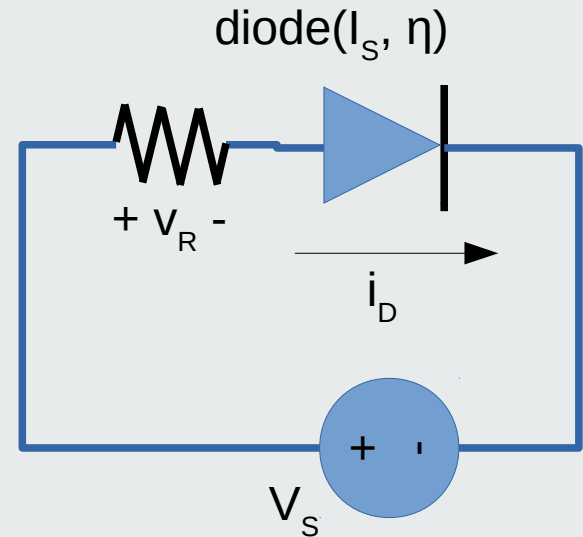
- Temperature increases i_D
- i_D increases v_R
- v_R decreases v_D :
 $v_R + v_D = v_S$ (constant, KVL)
- v_D decreases i_D
- This is called a negative feedback loop
- Resistor stabilizes i_D and protects diode!!




$$i_D = I_S \left(e^{\frac{v_D}{\eta V_T}} - 1 \right)$$

$$v_R = R i_D$$

Optical Transmitter / Receiver System

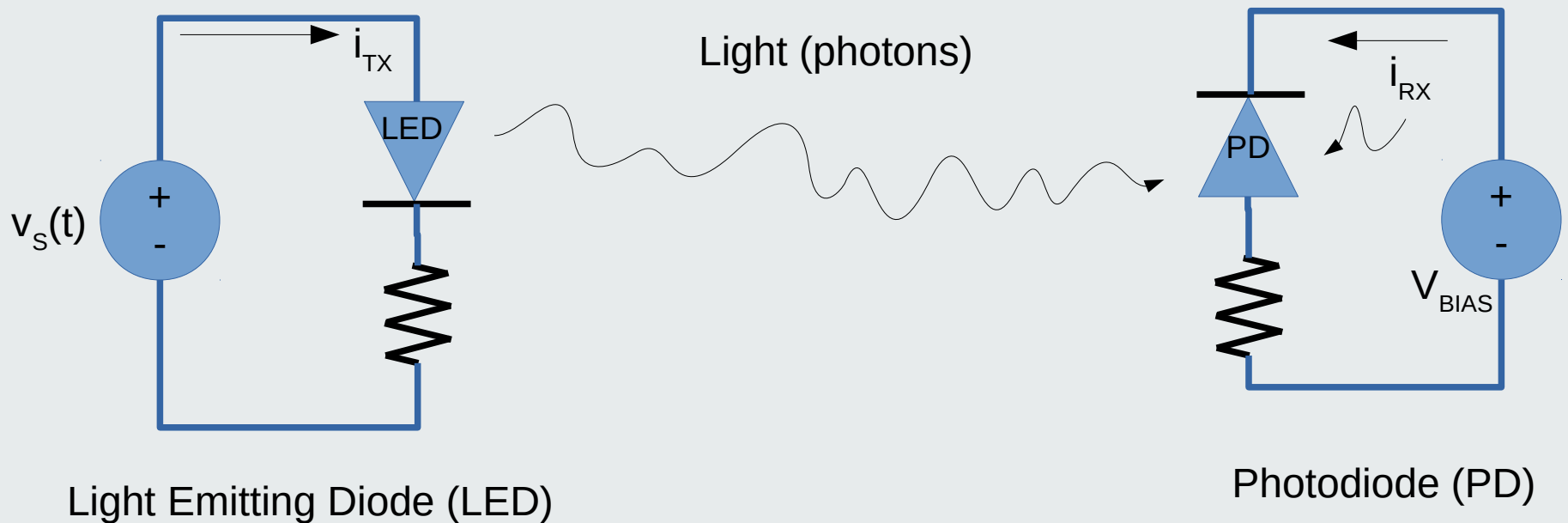

Light Emitting Diode (LED) Transmitter

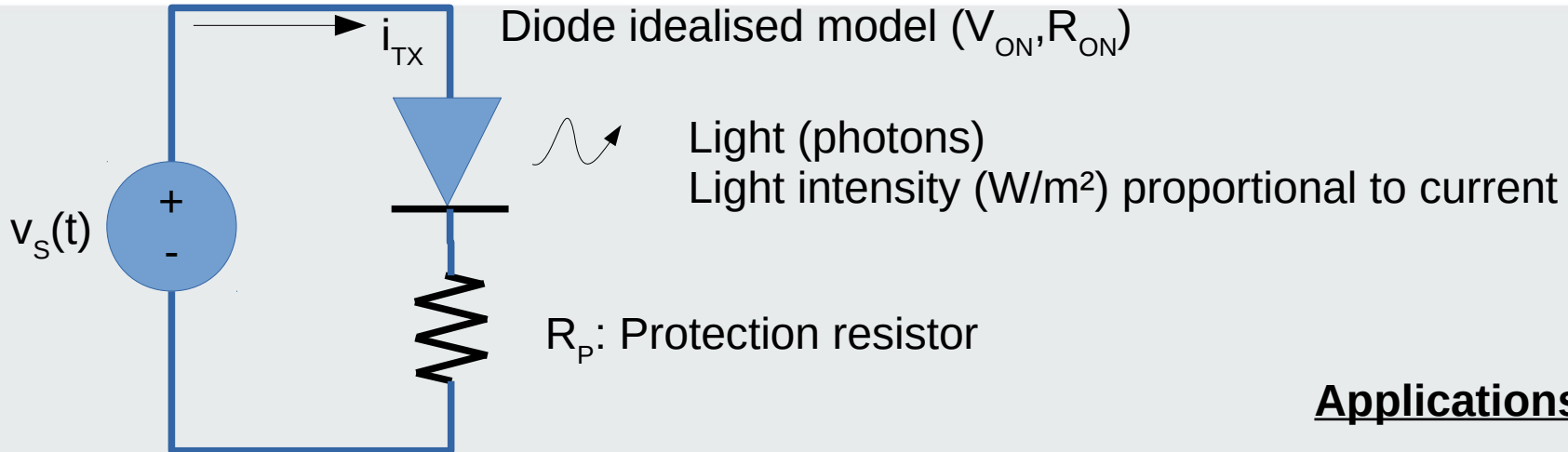

$$i_{TX}(t) = \frac{v_S(t) - V_{ON}}{R + R_{ON}}$$

Total current

$$I_I(t) = K_{TX} i_{TX}(t)$$

Light intensity

$$I_{TX} = \frac{V_S - V_{ON}}{R + R_{ON}}$$


Operating point DC current

$$L_I = K_{TX} I_{TX}$$

Applications


- Signalling, e.g. ON/OFF light
- Character displays
- Infrared light for remote controls
- Etc

Photo Diode (PD) Receiver

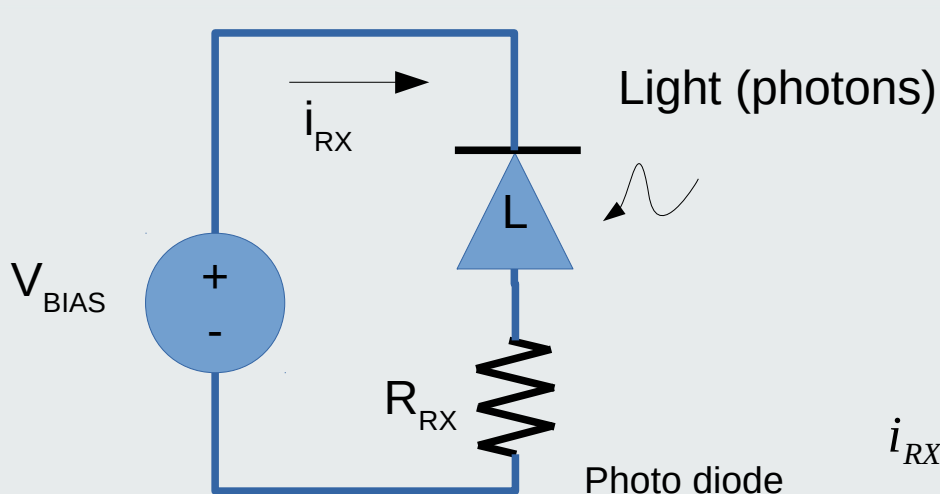

$$i_{RX} = K_{RX} l_I(t) - I_S \left(e^{\frac{v_D}{\eta V_T}} - 1 \right)$$

$$v_{RX} = R_{RX} i_{RX}$$

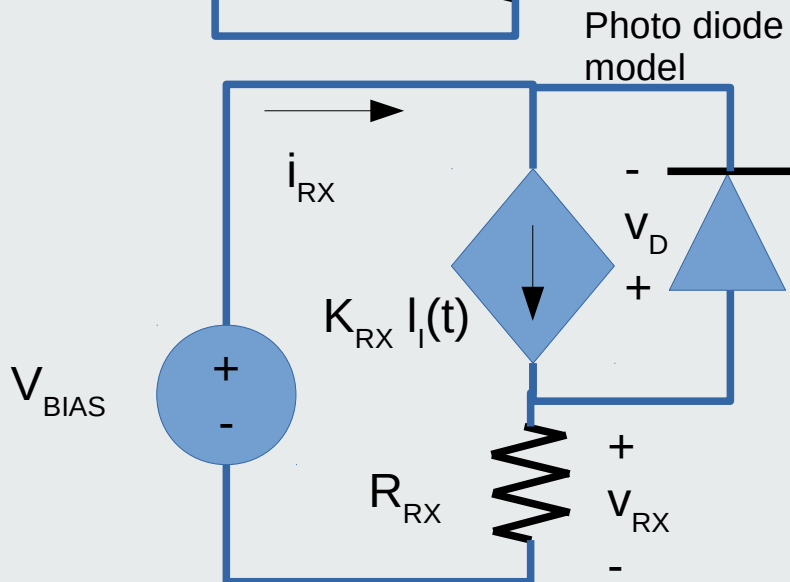

$$i_{RX}(t) = K_{RX} l_I(t) - I_S \left(e^{\frac{v_D}{\eta V_T}} - 1 \right)$$


$$v_{RX}(t) = R_{RX} i_{RX}(t)$$

$$v_{RX}(t) = R_{RX} K_{RX} l_I(t) - R_{RX} I_S \left(e^{\frac{v_{RX} - V_{BIAS}}{\eta V_T}} - 1 \right)$$

$$v_{RX}(t) = R_{RX} K_{RX} K_{TX} i_{TX}(t) + R_{RX} I_S$$

$$v_{RX}(t) = R_{RX} K_{RX} K_{TX} \frac{v_S(t) - V_{ON}}{R_{TX} + R_{ON}} + R_{RX} I_S$$

Receiver Incremental Model

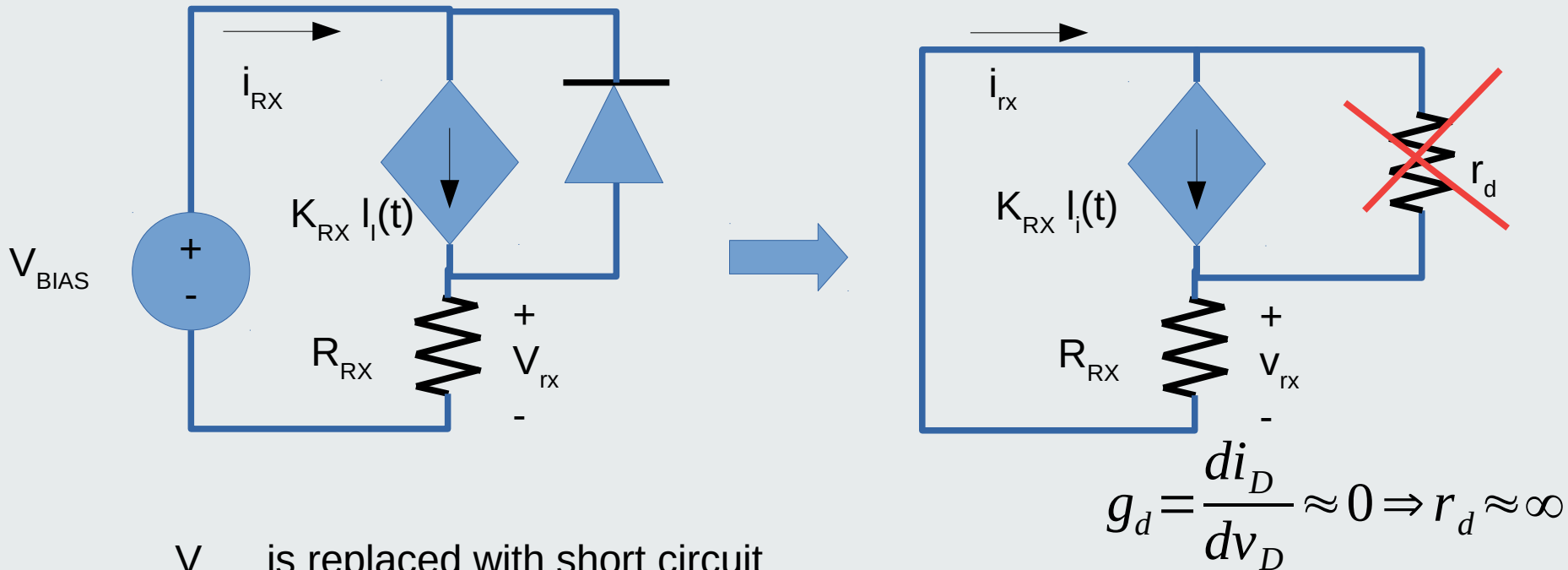


V_{BIAS} is replaced with short circuit

Diode reversely biased has large incremental resistor r_d

Resistor r_d in parallel with R_{RX} can be neglected

Photo Diode Received Signal

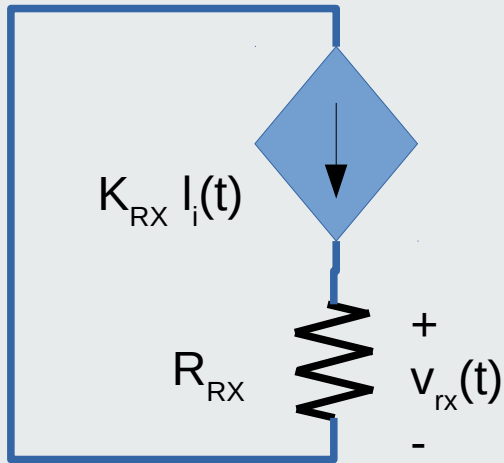

$$v_{rx}(t) = R_{RX} K_{RX} l_i(t)$$

$$v_{rx}(t) = \frac{R_{RX} K_{RX} K_{TX}}{R_{TX} + R_{ON}} v_s(t)$$

$$l_i(t) = l_I(t) - L_I$$

$$l_I(t) = K_{TX} i_{TX}(t)$$

$$l_I(t) = K_{TX} \frac{v_s(t) - V_{ON}}{R_{TX} + R_{ON}}$$

$$v_s(t) = V_S + v_s(t)$$

$$L_I = K_{TX} \frac{V_S - V_{ON}}{R + R_{ON}}$$

$$l_i(t) = \frac{K_{TX}}{R_{TX} + R_{ON}} v_s(t)$$

Conclusion

- Incremental model of independent and dependent sources
- Incremental impedance of linear passive components
- Diodes in series
- Diodes in parallel
- Temperature effect
- Optical transmitter/receiver system