

Circuit Theory and Electronics Fundamentals

Lecture 3: RC and RL circuits

- Resistor images
- Capacitors and inductors
- Capacitors and inductors in series and in parallel
- RC circuits
- RL circuits

Resistor Images



Discrete
Resistors




Discrete
SMD
Resistors

Voltage and
Current sources
may be complex
circuits! Not
shown as yet.





© Can Stock Photo - csp30163484

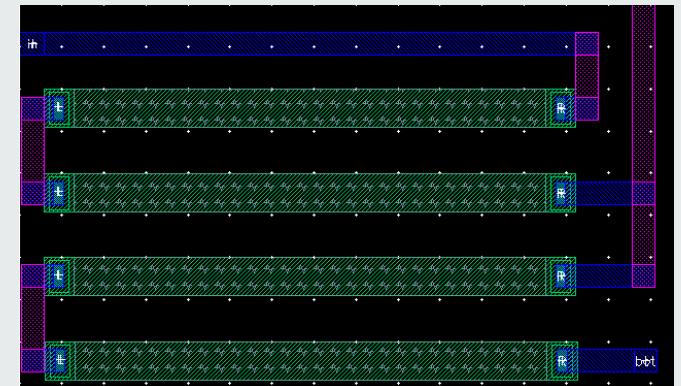SMD resistors mounted on Printed
Circuit Board (PCB)



Integrated resistor
(nanometric size: 10^{-9} meter)

Component: Capacitor

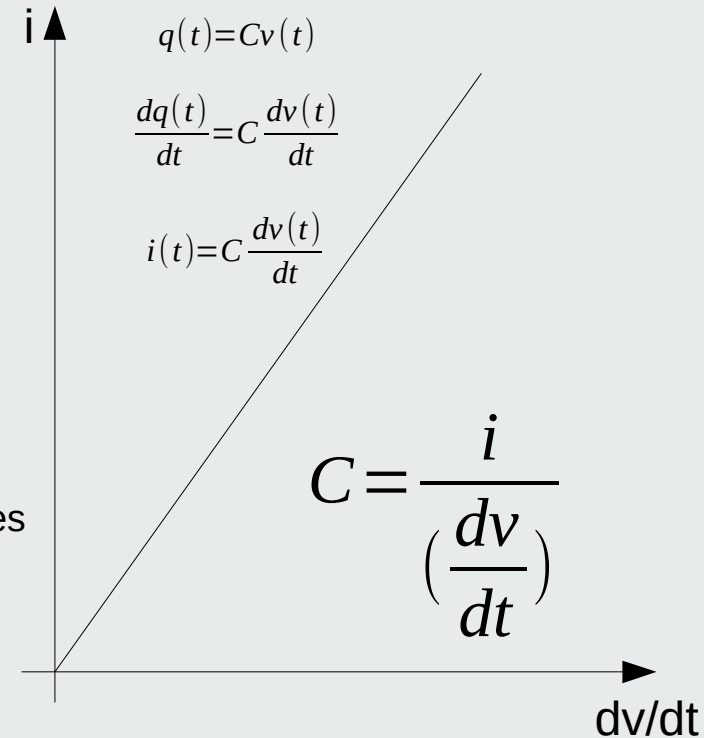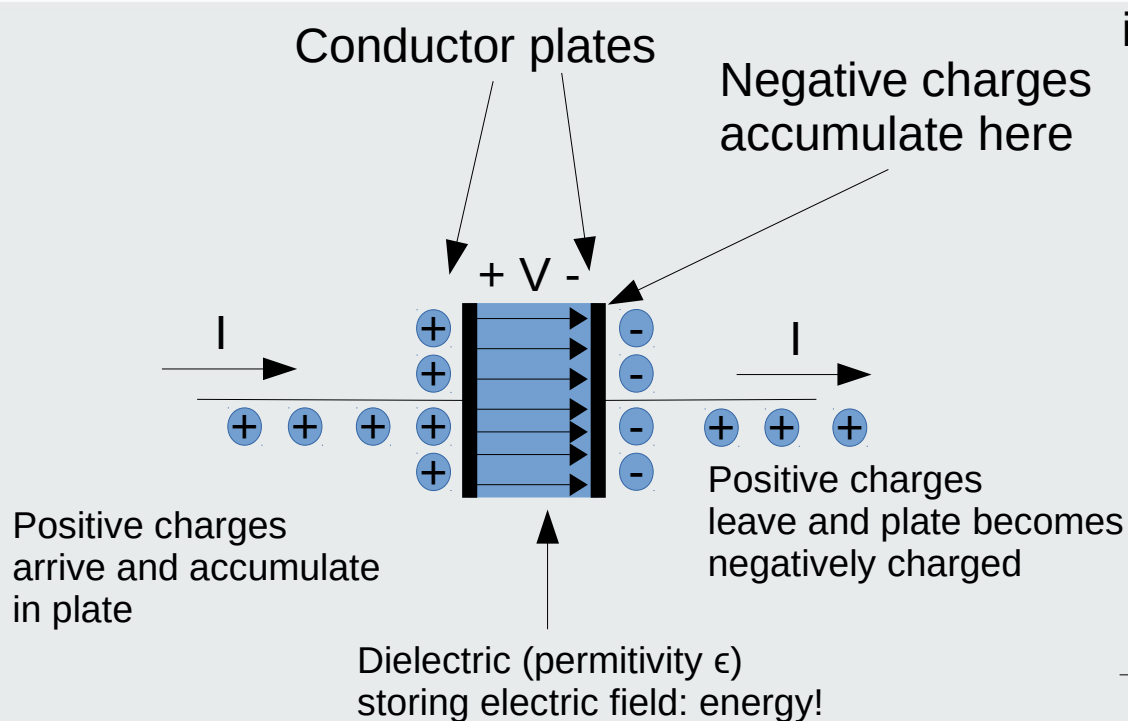


- Linear Capacitor: $Q = CV$
- C is capacitance expressed in Farad: $F = C/V$

Analysis methods are the same but generate linear differential equations instead of algebraic equations


Solutions are time functions (*lower case notation*)

Component: inductor

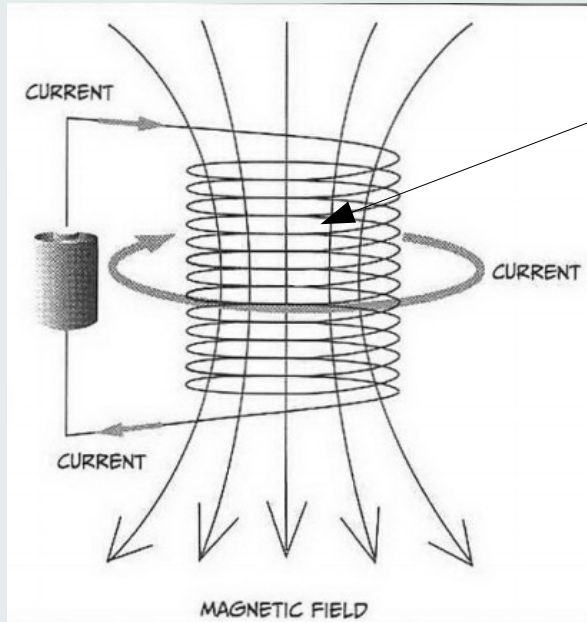


Inductor core
(permeability μ)
Storing magnetic
field: energy!

CURL RIGHT HAND RULE

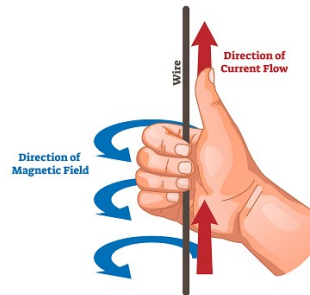

Current keeps magnetic
field on, and magnetic field
keeps current going

L given Henry: $H = Vs^2/C$

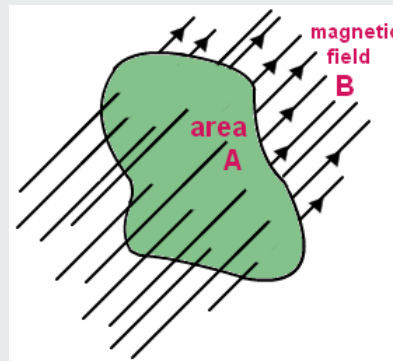


$$\Phi = \iint_A \vec{B} \cdot \vec{n} dA$$

$$\Phi = Li$$

$$\frac{d\Phi}{dt} = L \frac{di}{dt}$$

$$v(t) = L \frac{di(t)}{dt}$$

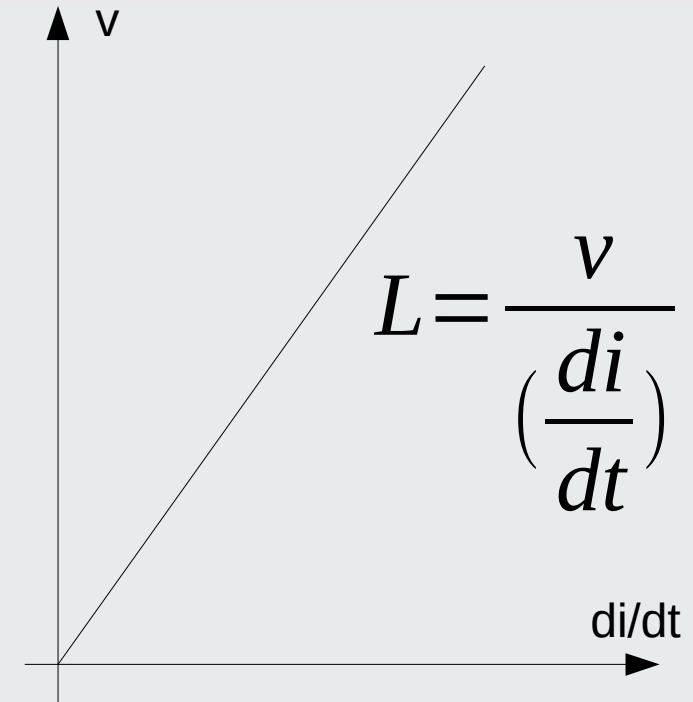


Capacitor and inductors images


Discrete capacitors




Integrated capacitor

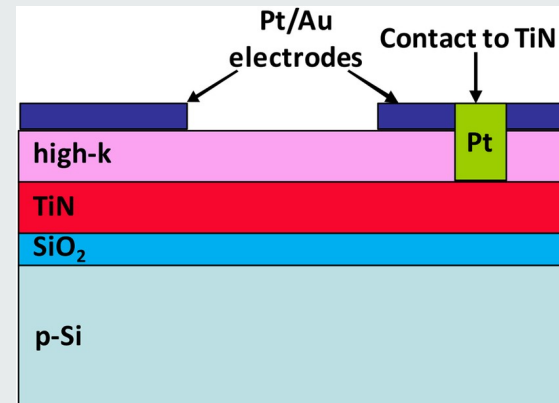

Discrete inductors

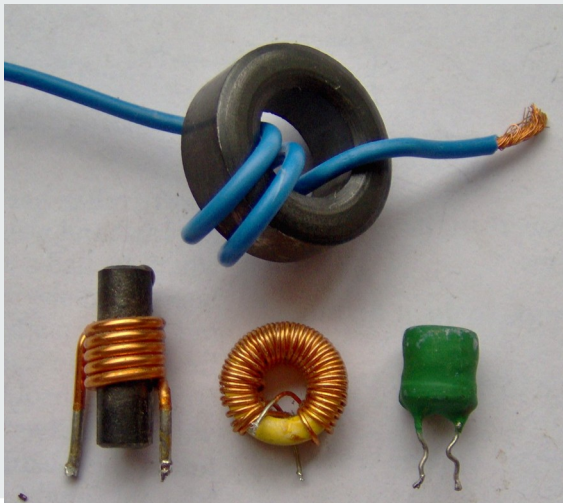

Integrated inductor

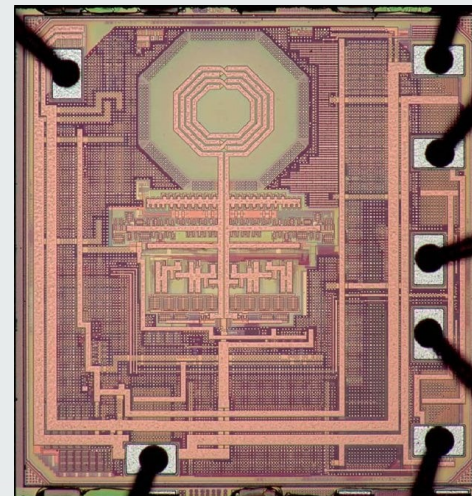

Parallel of Capacitors


$$i = \sum_{i=1}^n i_i \quad \text{KCL}$$

$$i = \sum_{i=1}^n C_i \frac{dv}{dt}$$

$$i = \left(\sum_{i=1}^n C_i \right) \frac{dv}{dt}$$

$$C = \sum_{i=1}^n C_i$$

All Cs have the same voltage v

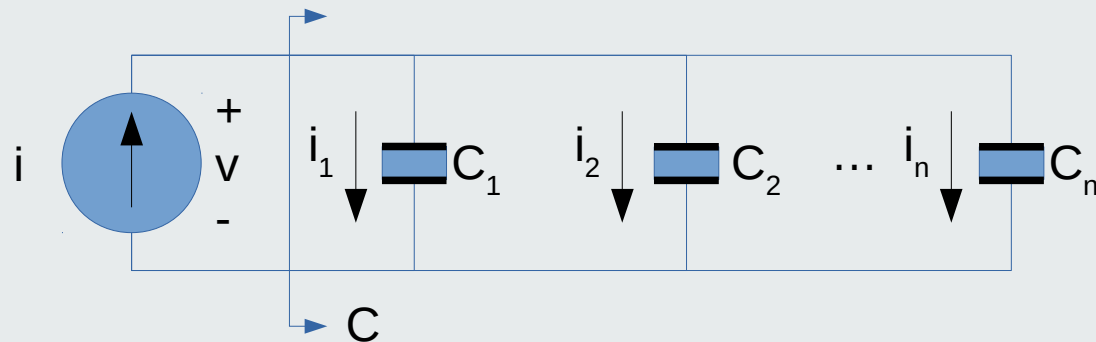

Similar to **series** of resistors

Series of Capacitors

$$v = \sum_{i=1}^n v_i$$


KVL

$$\frac{dv}{dt} = \sum_{i=1}^n \frac{dv_i}{dt}$$

$$\frac{dv}{dt} = \sum_{i=1}^n \frac{i}{C_i}$$

All Cs have the same current i
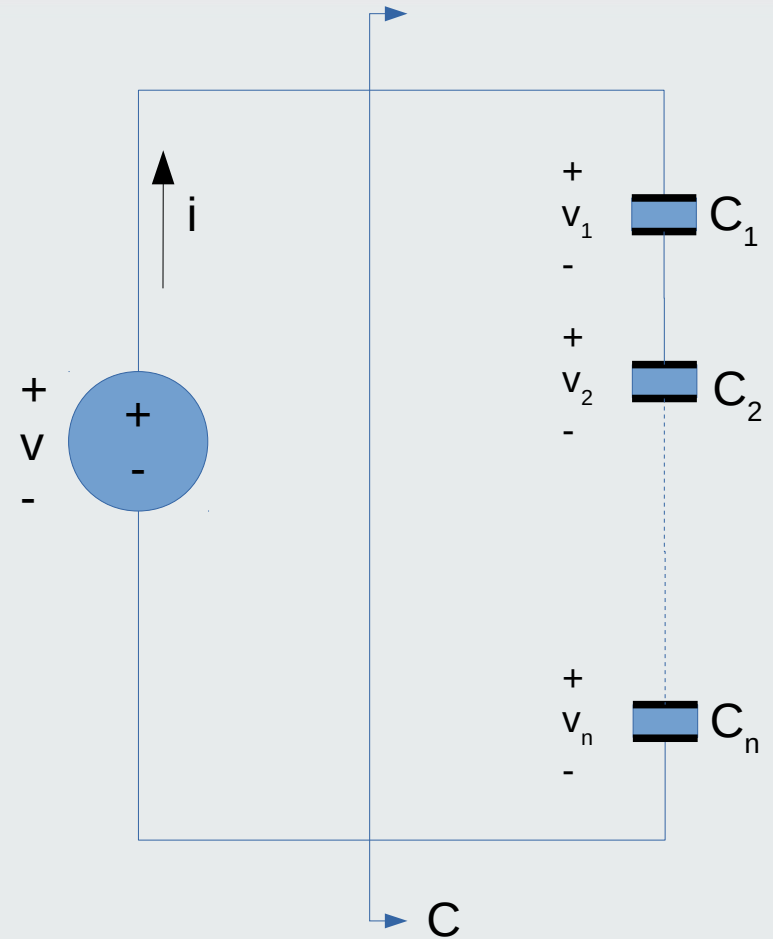
$$C = \frac{1}{\sum_{i=1}^n \frac{1}{C_i}}$$



Similar to **parallel** of resistors

Parallel of Inductors

$$i = \sum_{i=1}^n i_i$$


$$\frac{di}{dt} = \sum_{i=1}^n \frac{di_i}{dt}$$

$$\frac{di}{dt} = \sum_{i=1}^n \frac{v}{L_i}$$

$$L = \frac{1}{\sum_{i=1}^n \frac{1}{L_i}}$$

KCL

All Ls have the same voltage v

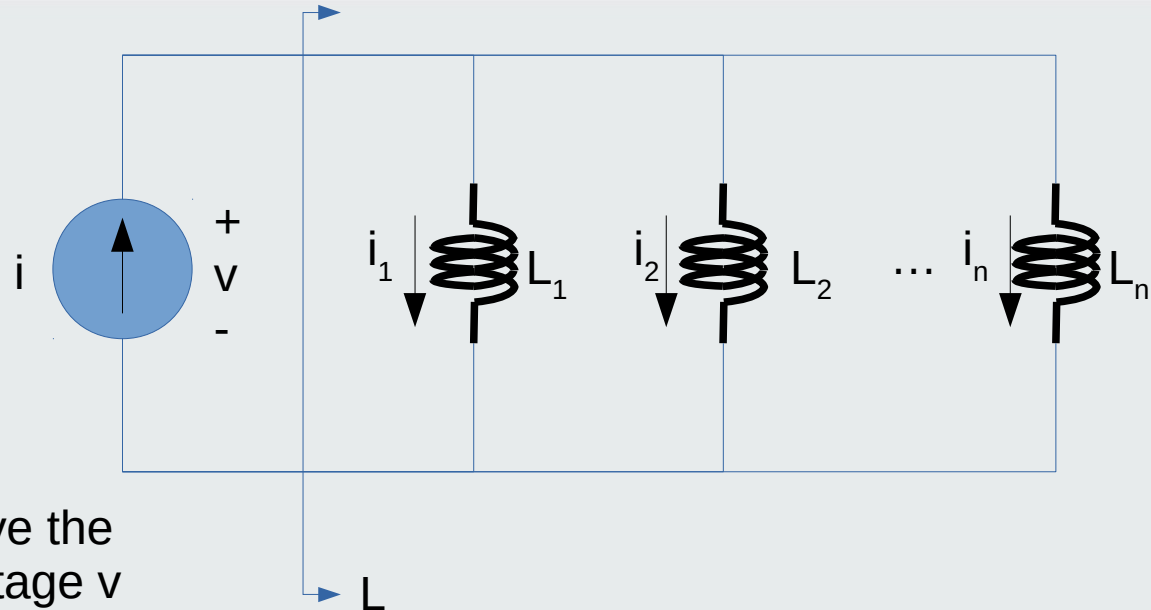

Similar to **parallel** of resistors

Series of Inductors

$$v = \sum_{i=1}^n v_i$$


$$v = \sum_{i=1}^n L_i \frac{di}{dt}$$

$$v = \left(\sum_{i=1}^n L_i \right) \frac{di}{dt}$$

$$L = \sum_{i=1}^n L_i$$

KVL

All L s have the same current i

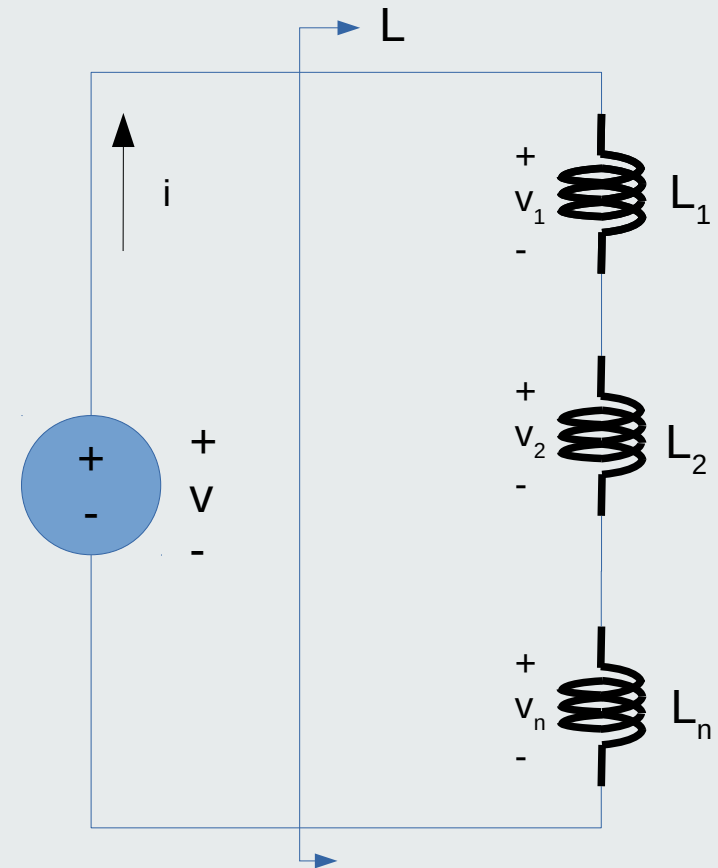


Similar to **series** of resistors

RC series: circuit analysis

$$v_s = Ri + v_1 \quad \text{KVL}$$

$$i = C \frac{dv_1}{dt}$$
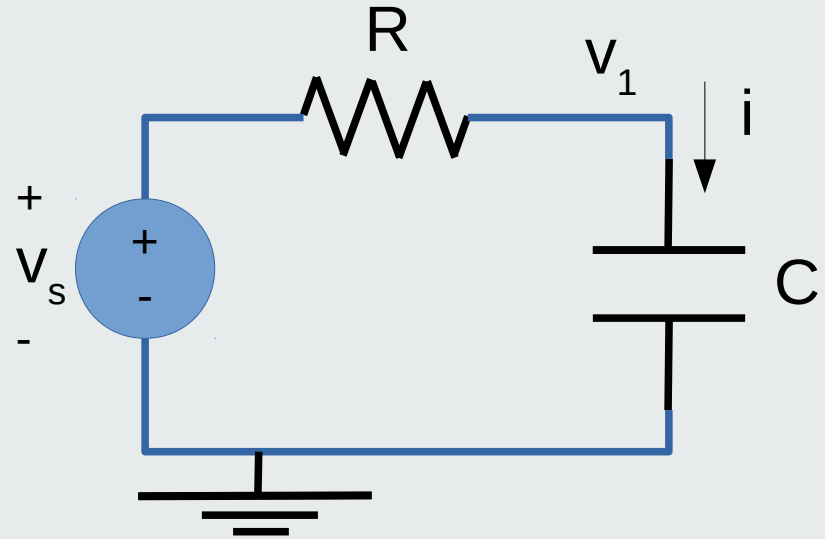
$$RC \frac{dv_1}{dt} + v_1 = v_s \quad \text{1st order linear differential equation!}$$



Solution:

$$v_1(t) = v_{1n}(t) + v_{1f}(t) \quad \rightarrow \text{Forced solution: depends on voltage source } v_s(t) \text{ and } R, C$$

\nwarrow
 Natural solution: depends on initial charge (voltage) and R, C

RC series: natural solution

$$RC \frac{dv_1}{dt} + v_1 = 0 \quad \leftarrow \text{Remove voltage source}$$

$$\left(RC \frac{d}{dt} + 1 \right) v_1 = 0$$

$$RC \frac{d}{dt} + 1 = 0 \vee v_1 = 0$$

$$RC s + 1 = 0$$

$$s = -\frac{1}{RC}$$

$$v_{1n}(t) = A e^{st} = A e^{-\frac{t}{RC}}$$


Note d/dt is a linear operator

Two solutions, $v_1 = 0$ is a trivial (uninteresting) solution

Characteristic equation: replace d/dt with s , aka complex frequency. Solve for s . RC is called “time constant”

Natural solution, A is a constant to be determined

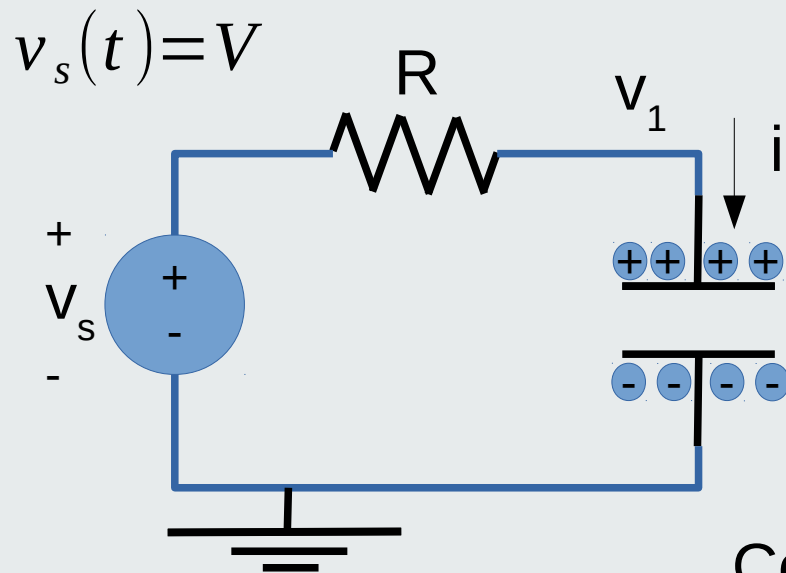RC series: forced solution with constant excitation



Voltage source drives constant voltage V

Eventually C charges up, v_1 reaches $v_1 = V$, and current stops: $i=0$

Constant excitation \Rightarrow constant forced solution!

$$v_{1f}(t) = V$$

Capacitor behaves like an *open-circuit* after charged!

RC series: final solution

$$v_1(t) = v_{1n}(t) + v_{1f}(t)$$

$$v_1(t) = Ae^{-\frac{t}{RC}} + V$$

$$v_1(0) = 0$$

$$v_1(0) = 0 \Rightarrow A = -V$$

$$v_1(t) = V \left(1 - e^{-\frac{t}{RC}} \right)$$


$$i(t) = C \frac{dv_1}{dt} = \frac{V}{R} e^{-\frac{t}{RC}}$$

Superimpose natural and forced solutions

Constant A can now be determined by a boundary condition: charge (voltage) of C at some instant. A common boundary condition is the initial capacitor voltage at $t=0$, here assumed 0. Constant A is thus determined



Final solutions voltage and current are now computed

RC series: final solution plots

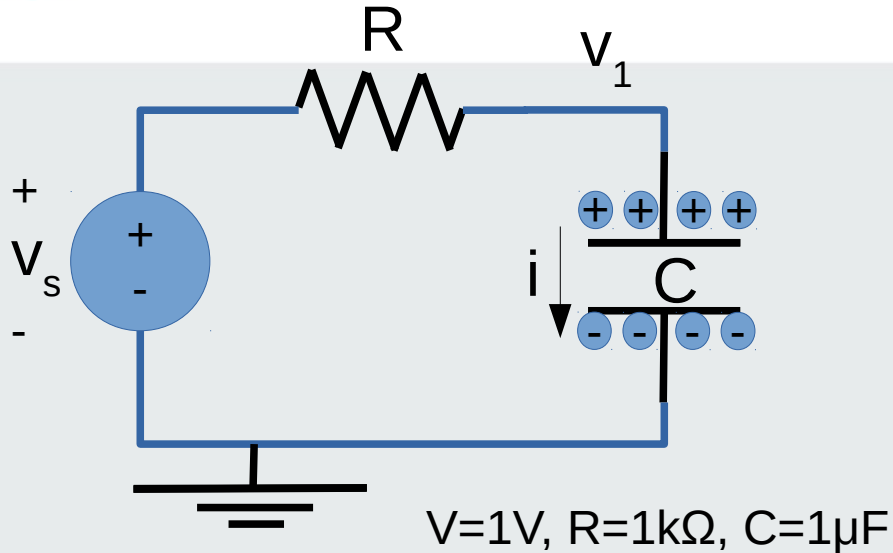


$t=0$: no voltage across C (electric field build up starts), v_1 is null, all voltage across R , and i is max.

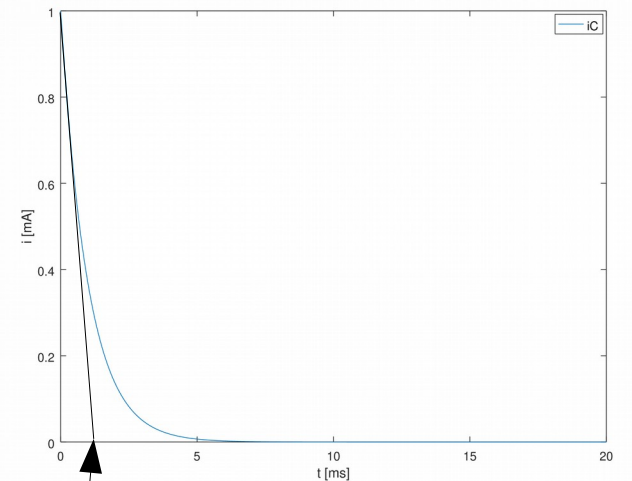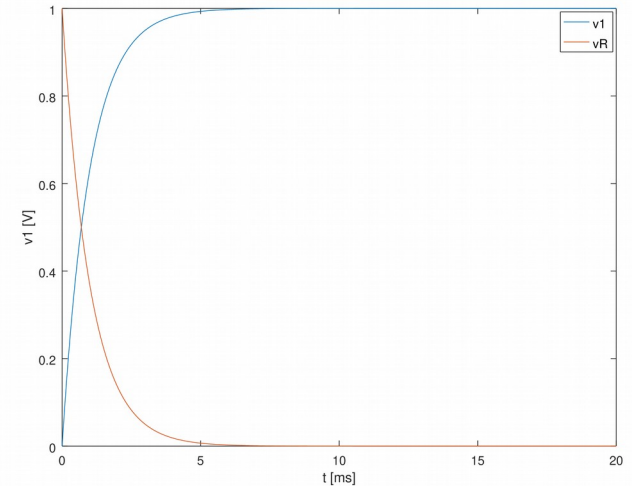$t=\infty$: all voltage across C (open-circuit behaviour), v_1 is max, no voltage across R and i is null.



$RC=1ms$

RL parallel: circuit analysis

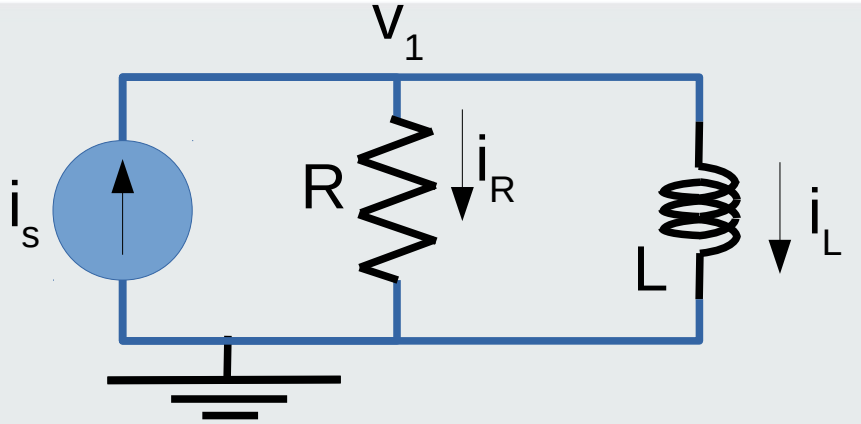

$$i_s = i_R + i_L \quad \text{KCL}$$

$$v_1 = L \frac{di_L}{dt}$$

$$i_R = \frac{v_1}{R}$$

$$\frac{L}{R} \frac{di_L}{dt} + i_L = i_s$$

Solution for constant current source

$$i_s(t) = I$$


$$i_L(t) = I \left(1 - e^{-\frac{R}{L}t} \right)$$

$$i_R = i_s - i_L$$

$$i_R(t) = I e^{-\frac{R}{L}t}$$



$$v_1(t) = RI e^{-\frac{R}{L}t}$$

RL parallel: final solution plots

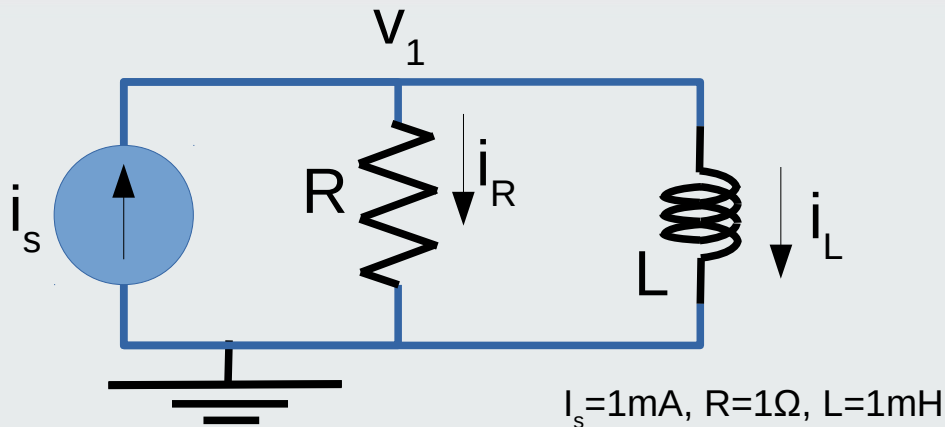


$t=0$: no current through L
(magnetic field build up starts)
All current through R
 v_1 is max

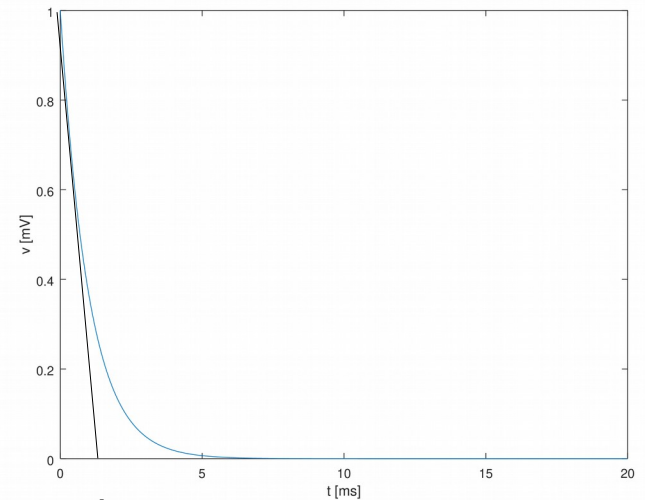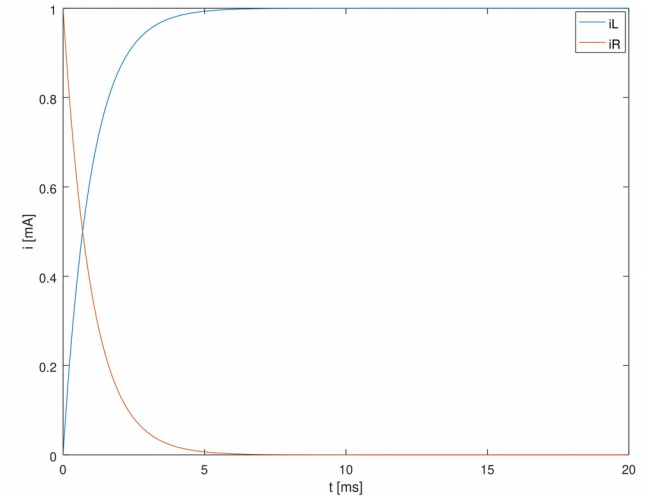$t=\infty$: all current through L
(short-circuit behavior)
No current through R
 v_1 is null



$L/R = 1\text{ms}$

RC parallel: circuit analysis

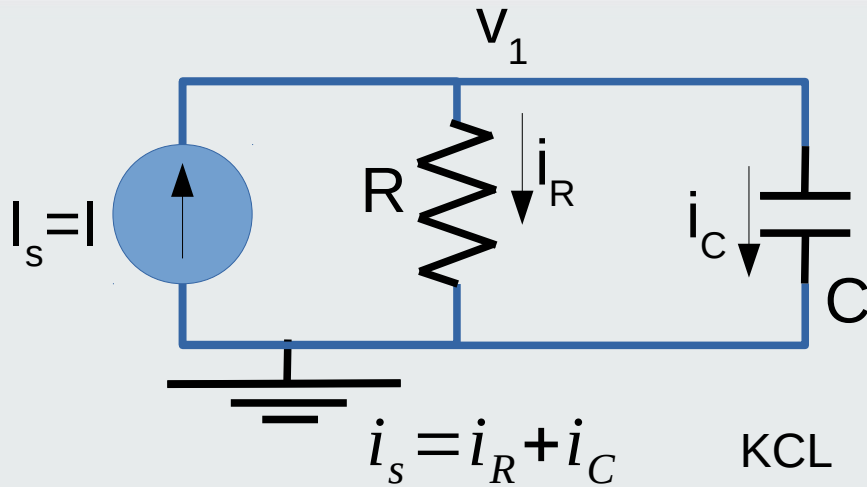

$$i_C = C \frac{dv_1}{dt}$$

$$i_R = \frac{v_1}{R}$$

$$C \frac{dv_1}{dt} + \frac{v_1}{R} = i_s$$

Solution for constant i_s

$$i_s(t) = I$$


$$v_1(t) = RI \left(1 - e^{-\frac{t}{RC}} \right)$$

$$i_C(t) = I e^{-\frac{t}{RC}}$$

$$i_R = i_s - i_C$$



$$i_R(t) = I \left(1 - e^{-\frac{t}{RC}} \right)$$

RC parallel circuit analysis

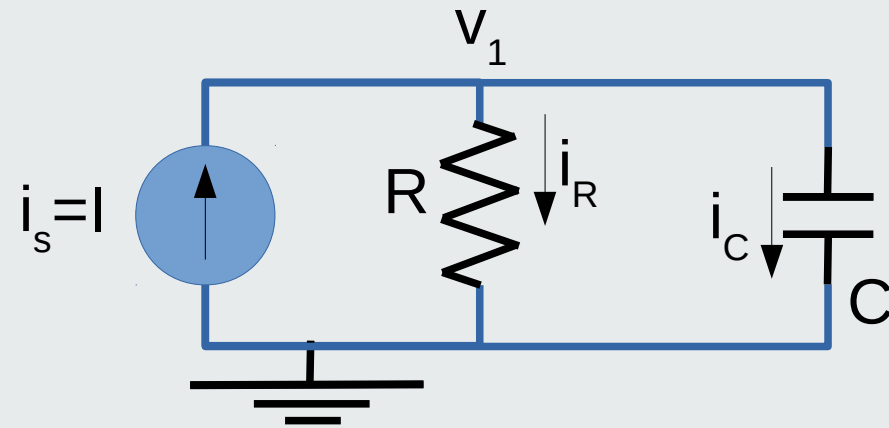

$t=0$: no current through R
(electric field build starts)
All current through C
 v_1 is nul

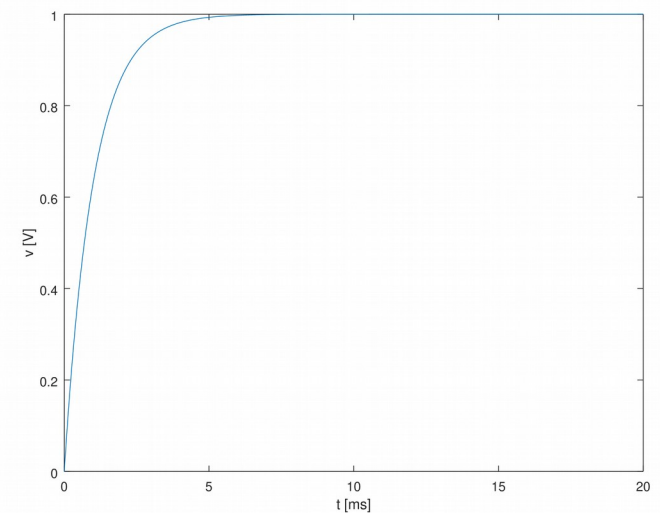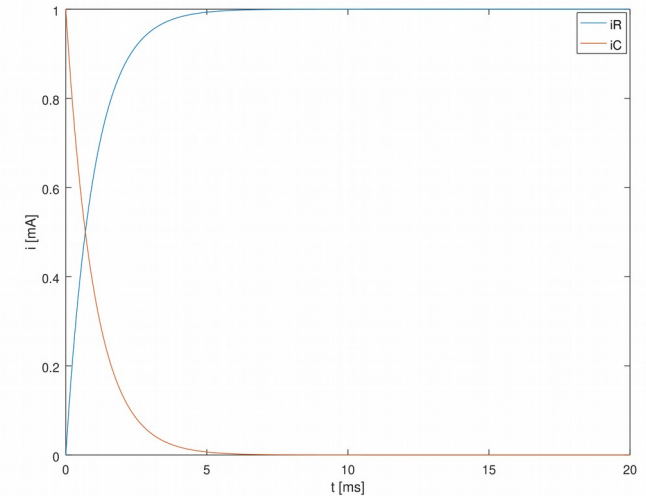$t=\infty$: all current through R
No current through C
(open-circuit behavior)
 v_1 is max ($v_1=RI$)



Conclusion

- Images of components R, L and C shown
- Capacitor and inductor laws
- Series and parallel of capacitors and inductors
- Analysis of circuits containing a single capacitor or single inductor, using 1st order linear differential equations
 - RC series
 - RC parallel
 - RL parallel