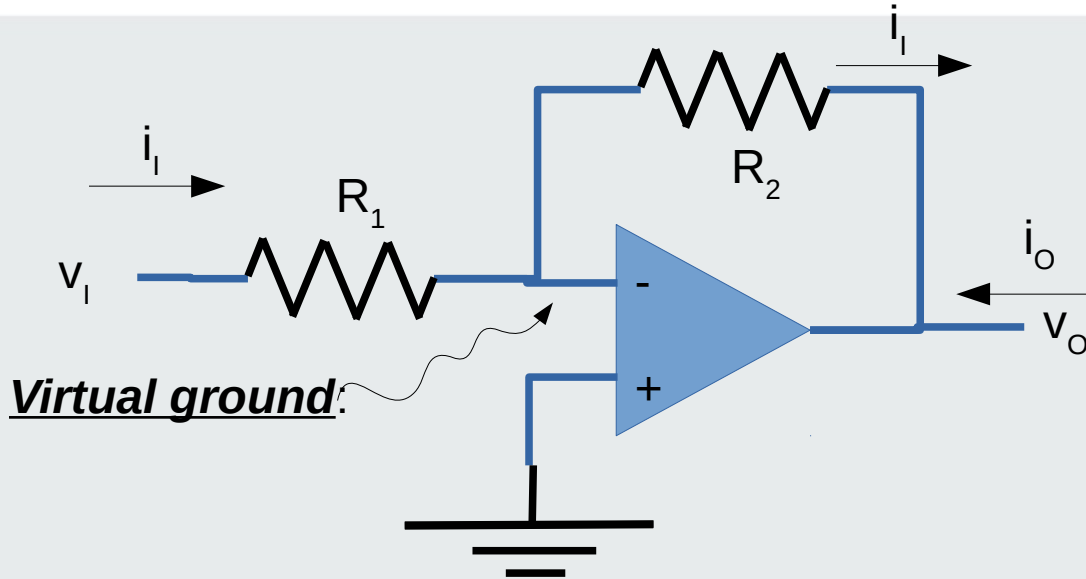


# Circuit Theory and Electronics Fundamentals

## Lecture 23: Operational Amplifier Circuits

- Analogue negation circuit
- The addition circuit
- Summation circuits
- Subtraction circuits
- The subtraction of summations circuit

# Remember: inverting amplifier with resistive feedback loop




$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} \quad \text{Gain}$$

$$Z_I = \left. \frac{v_I}{i_I} \right|_{Z_L = \infty} = \frac{v_I}{\frac{v_I - 0}{R_1}} = R_1$$

$$Z_O = \left. \frac{v_O}{i_O} \right|_{v_I = 0} = R_2 \parallel 0 = 0$$

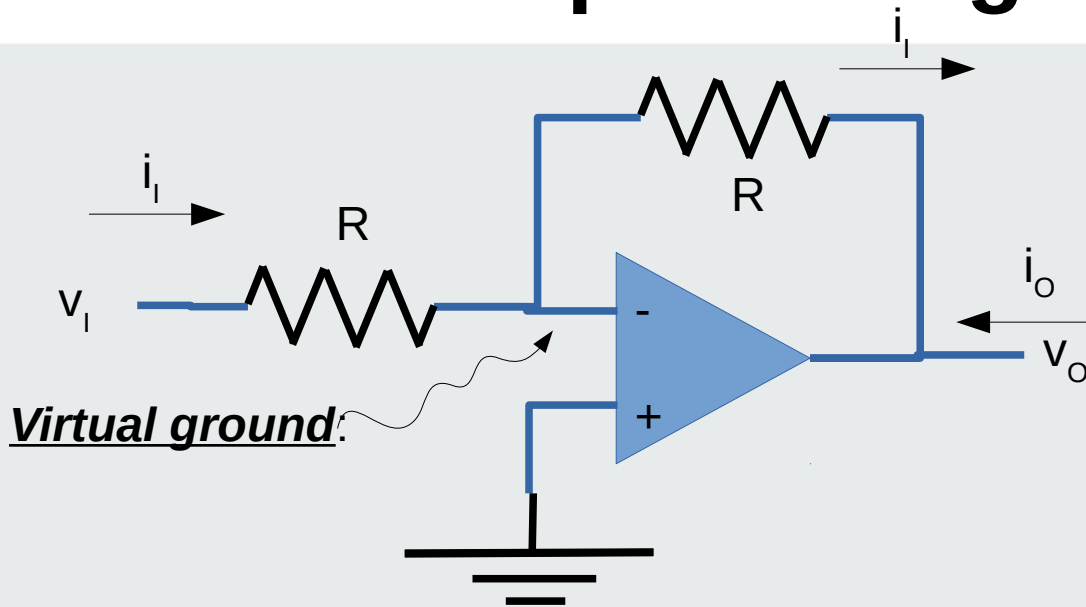
# Compute the negative of an input voltage




Just make  $R_1 = R_2 = R$

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} = -\frac{R}{R} = -1$$
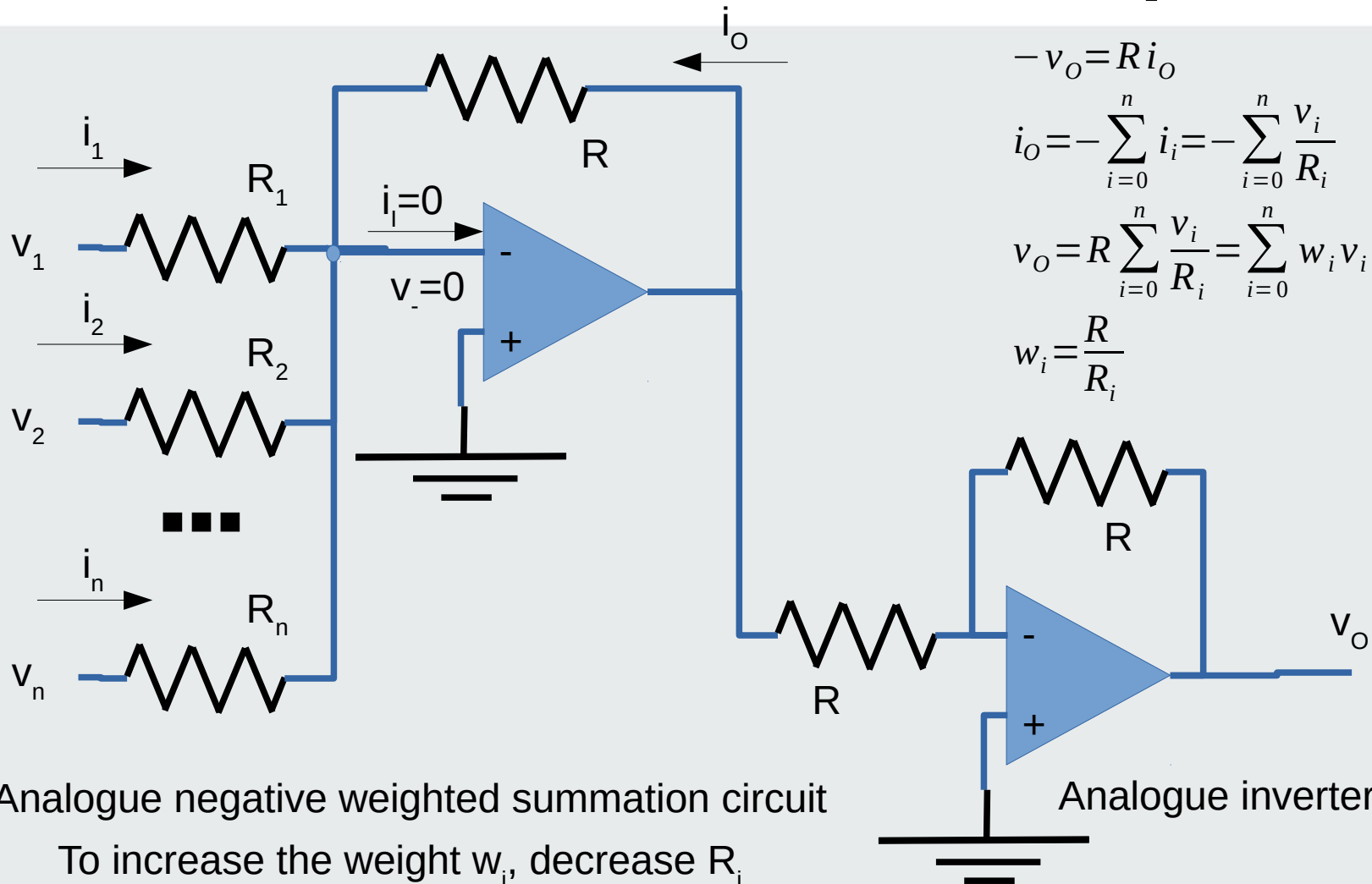
# Compute a weighted summation of the inputs


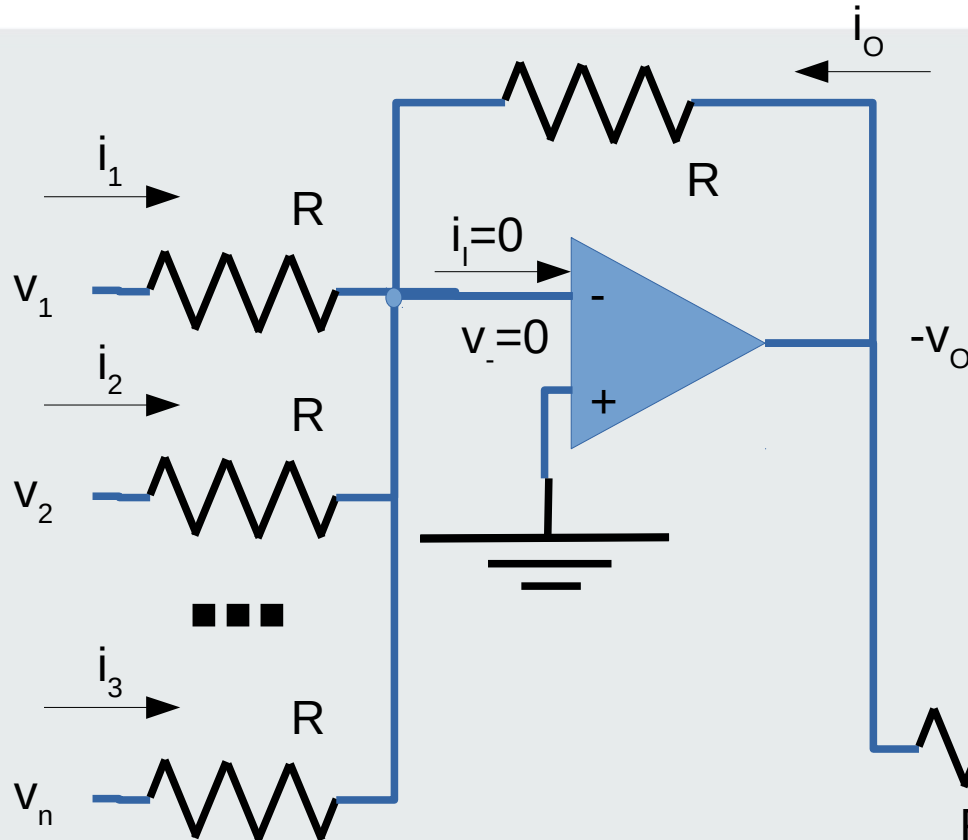
# Compute the summation of the inputs: just make $R_i = R$




$$-v_O = R i_O$$


$$i_O = -\sum_{i=0}^n i_i = -\sum_{i=0}^n \frac{v_i}{R}$$

$$v_O = R \sum_{i=0}^n \frac{v_i}{R} = \sum_{i=0}^n v_i$$

Analogue negative summation circuit

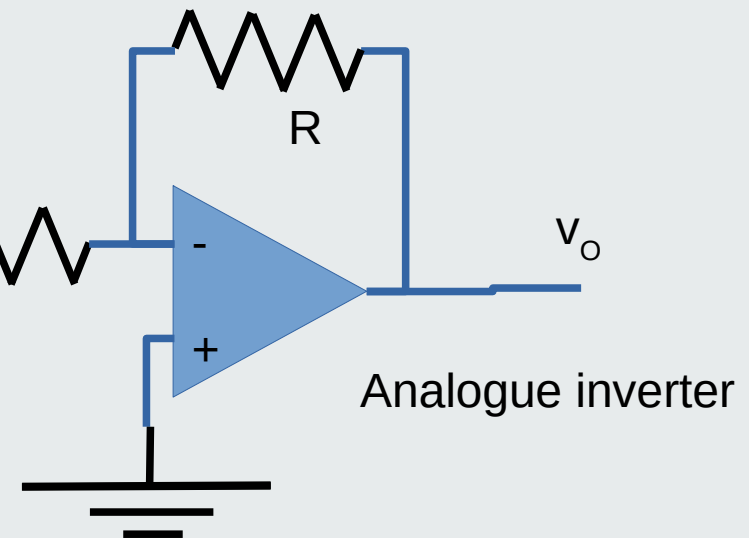
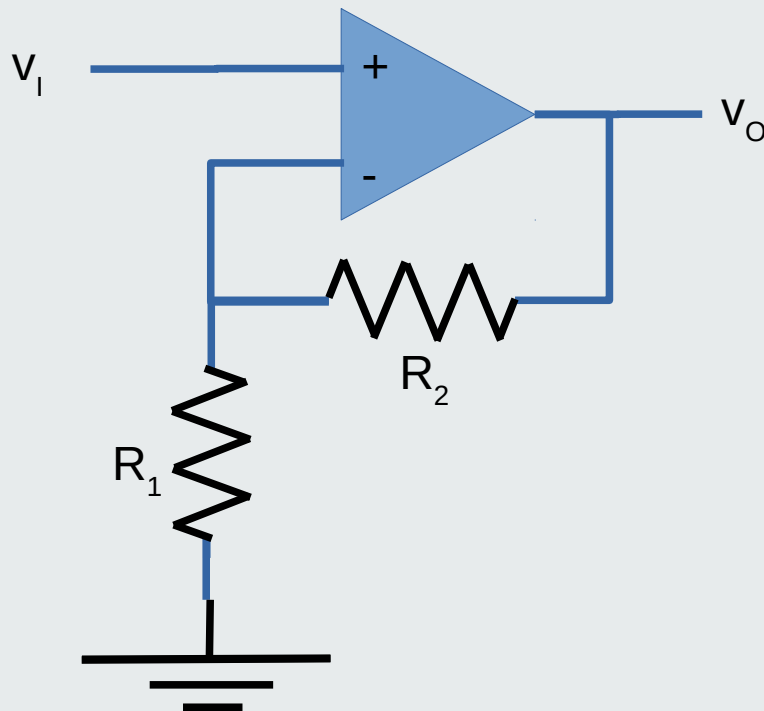
# Compute summation using non-inverting amplifier (1)




$$v_- = \frac{R_1}{R_1 + R_2} v_O$$

$$v_- = v_+ = v_I$$

$$\frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$
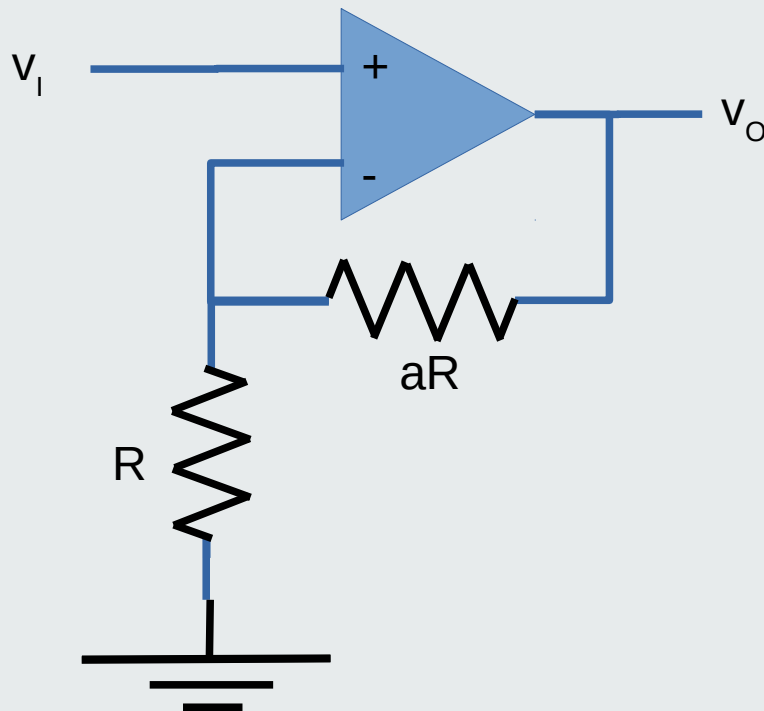
# Compute summation using non-inverting amplifier (2)




**Positive voltage amplifier**

$$\frac{v_O}{v_I} = 1 + \frac{aR}{R} = 1 + a$$

$$k = 1 + a$$

$$v_O = k v_I, k > 1$$
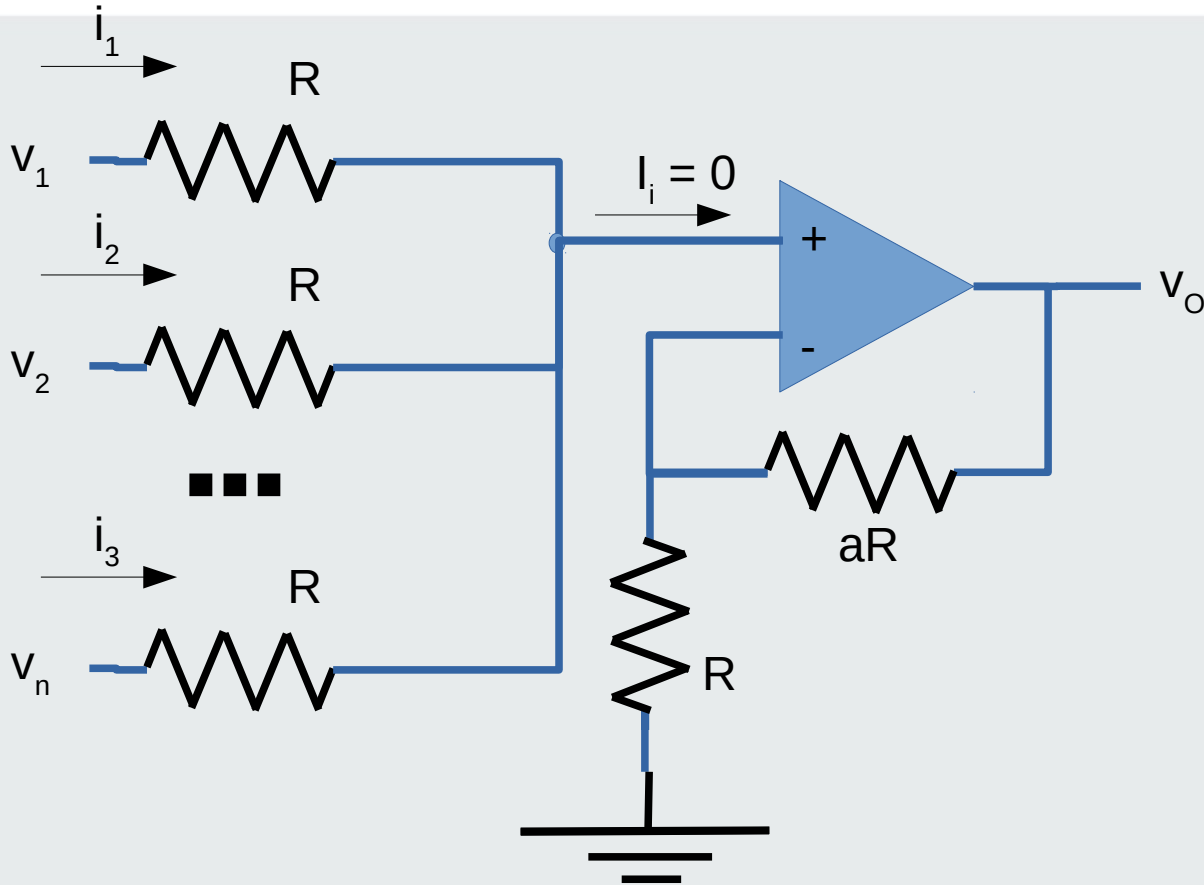
# Compute the summation using non-inverting amplifier (3)



$$v_+ = v_-$$

$$v_- = \frac{R}{R + aR} v_O = \frac{1}{1 + a} v_O = \frac{v_O}{k}$$

$$k = 1 + a > 1$$

$$v_- = \frac{v_O}{k}$$

$$\sum_{i=1}^n \frac{v_i - \frac{v_O}{k}}{R} = 0$$

$$\sum_{i=1}^n v_i - \frac{n}{k} v_O = 0$$


$$v_O = \frac{k}{n} \sum_{i=1}^n v_i$$

$$\frac{k}{n} = 1 \Rightarrow k = n = 1 + a \Rightarrow a = n - 1$$

$$v_O = \sum_{i=1}^n v_i$$


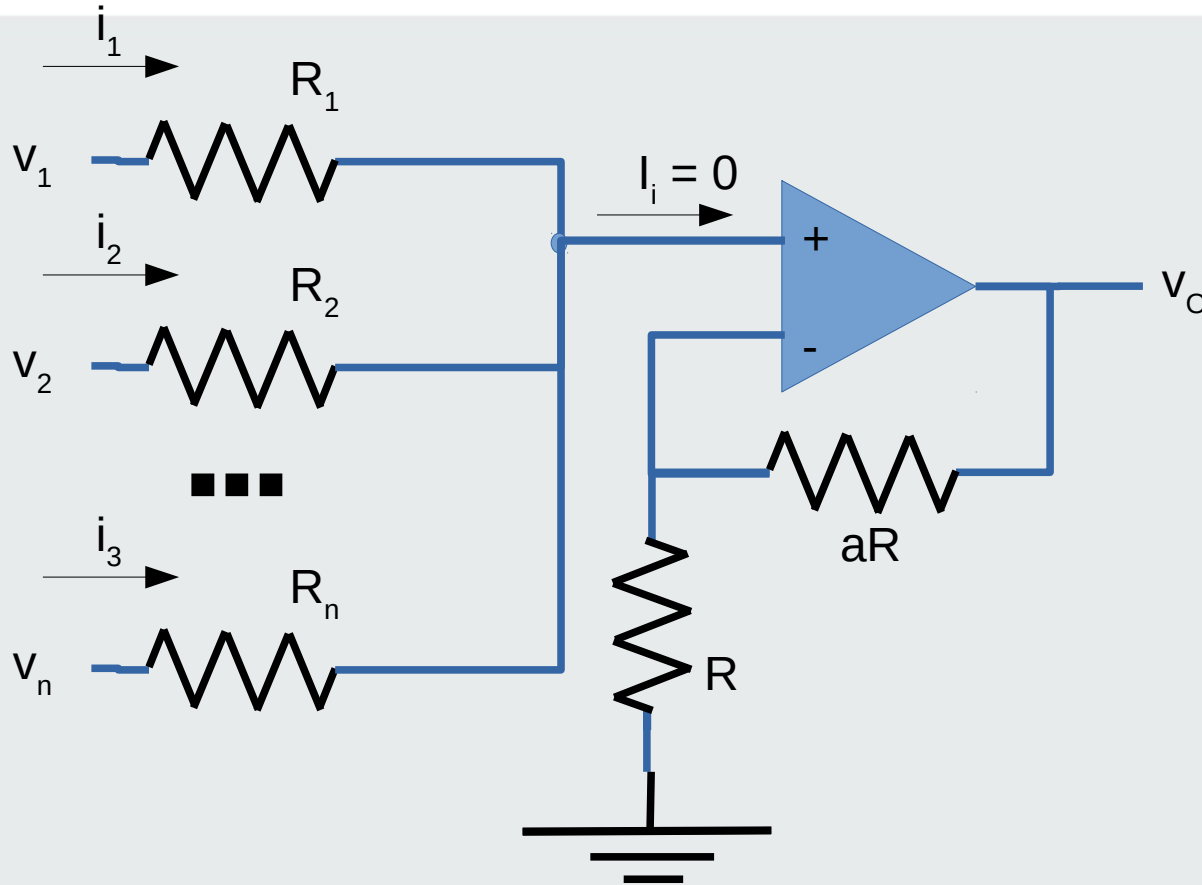
# Compute weighted summation using non-inverting amplifier



$$\sum_{i=1}^n \frac{v_i - \frac{v_o}{k}}{R_i} = 0$$

$$\sum_{i=1}^n \frac{v_i}{R_i} - \left( \frac{1}{k} \sum_{i=1}^n \frac{1}{R_i} \right) v_o = 0$$


$$v_o = \frac{k}{\sum_{i=1}^n \frac{1}{R_i}} \sum_{i=1}^n \frac{v_i}{R_i} = \sum_{i=1}^n w_i v_i$$

$$w_i = \frac{k}{R_i \sum_{i=1}^n \frac{1}{R_i}}$$

$$w_i < k$$

To increase the weight  $w_i$ , decrease  $R_i$
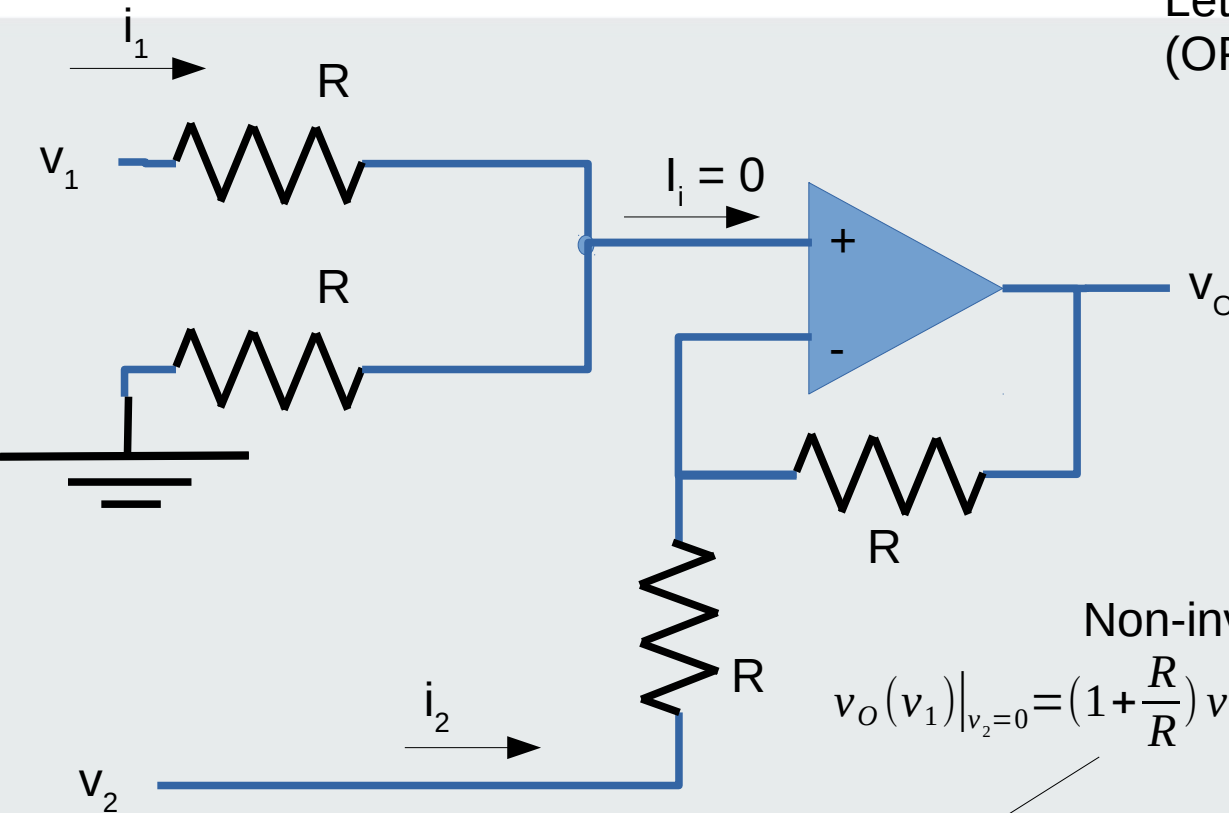
# Compute the subtraction of two voltages



Let's use the superposition theorem  
(OPAMPs make linear circuits!)

$$v_O = v_O(v_1)|_{v_2=0} + v_O(v_2)|_{v_1=0}$$

Non-inverting amp


$$v_O(v_1)|_{v_2=0} = \left(1 + \frac{R}{R}\right) v_+ = \left(1 + \frac{R}{R}\right) \left(\frac{R}{R+R} v_1\right) = v_1$$

Inverting amp


$$v_O(v_2)|_{v_1=0} = -\frac{R}{R} v_2 = -v_2$$

$$v_O = v_1 - v_2$$
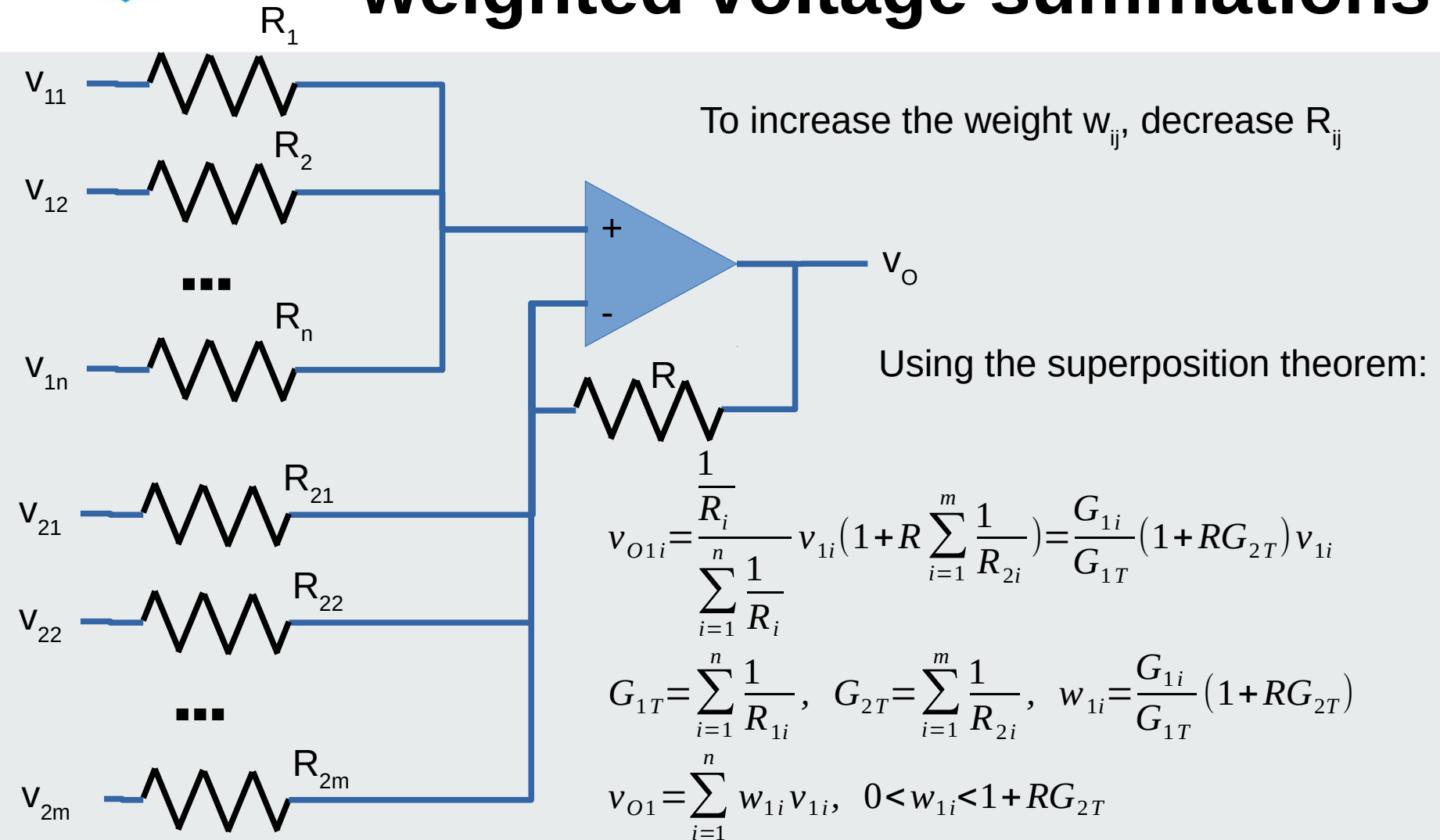
# Compute the subtraction of two weighted voltage summations


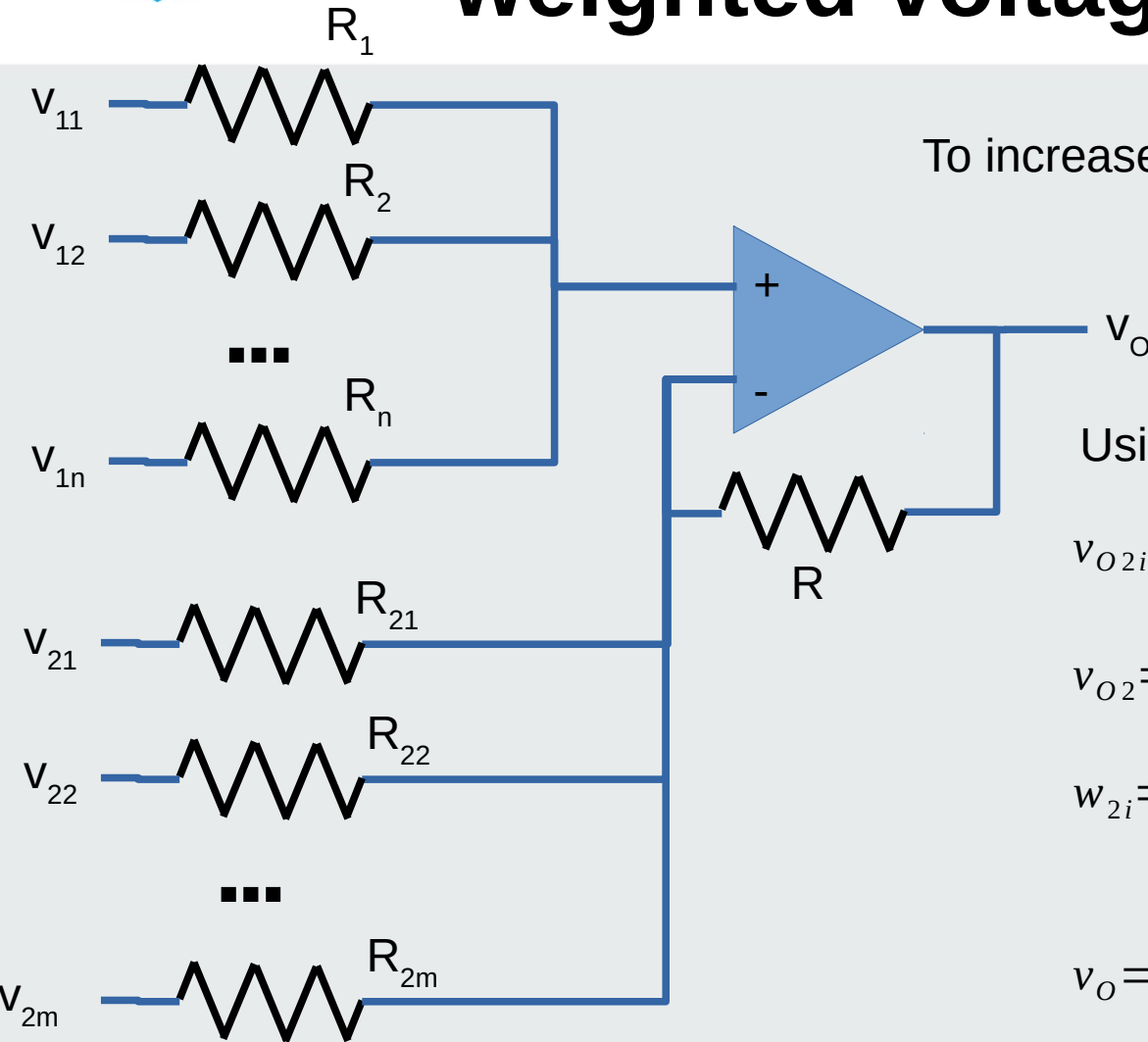
# Compute the subtraction of two weighted voltage summations



To increase the weight  $w_{ij}$ , decrease  $R_{ij}$

Using the superposition theorem:

$$v_{O2i} = -\frac{R}{R_i} v_{2i} \quad \text{Inverting amp}$$

$$v_{O2} = -\sum_{i=1}^m \frac{R}{R_i} v_{2i} = -\sum_{i=1}^m w_{2i} v_{2i}$$

$$w_{2i} = \frac{R}{R_i}, \quad 0 < w_{2i} < \infty$$

$$v_O = \sum_{i=1}^n w_{1i} v_{1i} - \sum_{i=1}^m w_{2i} v_{2i}$$

# Conclusion

- Analogue negation circuit
- The addition circuit
- Summation circuits
- Subtraction circuits
- The subtraction of summations circuit