


# Circuit Theory and Electronics Fundamentals

## Lecture 2: Circuit analysis methods

- Analysis for circuits with resistors and independent I/V sources
- Superposition Theorem
- Thévenin and Norton Theorems
- Dependent or controlled sources
- Circuit mesh and nodal analysis methods
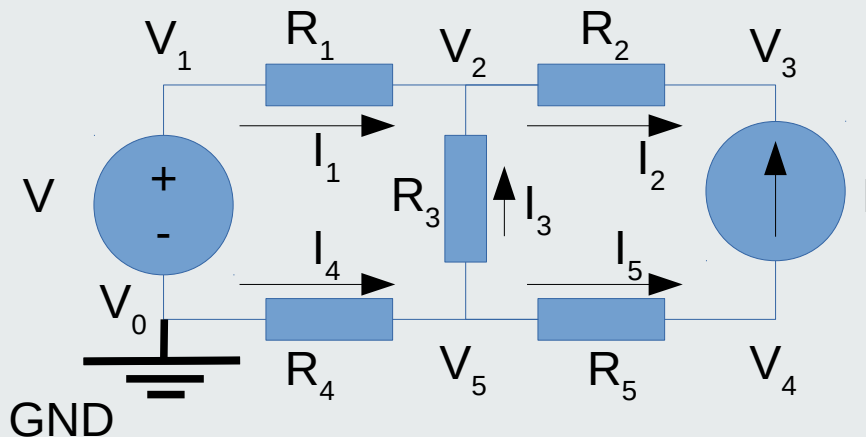
# Analysis of circuits with resistors and independent V/I sources

Analysis: find all node voltages and branch currents




## SETUP

- 1) Number nodes arbitrarily (e.g. 0 to  $n-1$ )
- 2) Assign current names and directions to all branches arbitrarily
- 3) Assign potential 0 to one of the nodes
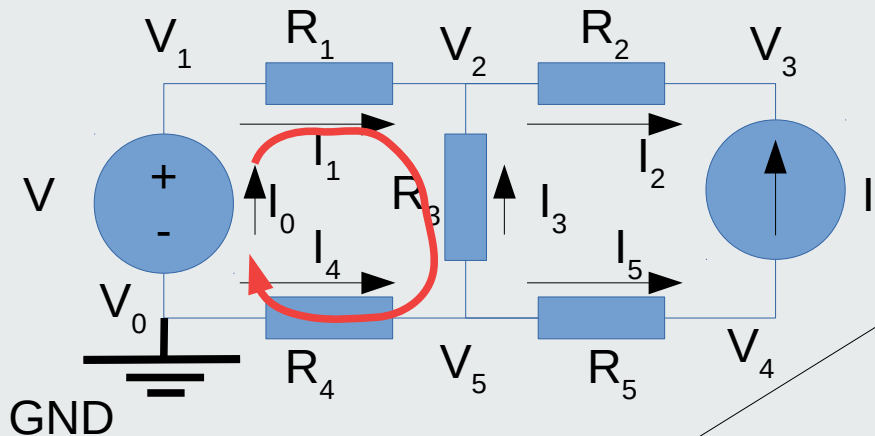
# Solving circuits

Find all node voltages  $V_0$ - $V_5$  and branch currents



$$\begin{aligned} I_0 &= I_1 \\ I_2 &= -I \\ I_4 &= -I_1 \\ I_5 &= I \end{aligned}$$

$$\begin{aligned} I_1 + I_3 - I_2 &= I_1 + I_3 + I = 0 \quad (\text{KCL node 2}) \\ I_3 + I_5 - I_4 &= I_3 + I + I_1 = 0 \quad (\text{KCL node 5}) \\ V &= R_1 I_1 - R_3 I_3 + R_4 I_1 \quad (\text{KVL loop } V, R_1, R_3, R_4) \end{aligned}$$


$$\begin{aligned} I_1 &= \frac{1}{R_1 + R_3 + R_4} V - \frac{R_3}{R_1 + R_3 + R_4} I \\ I_3 &= -\frac{1}{R_1 + R_3 + R_4} V - \frac{R_3 + R_4}{R_1 + R_3 + R_4} I \end{aligned}$$

KCL2 = KCL5 !

This may happen if we are not following a structured method!

# Computing node voltages from branch currents

## Use Ohm's Law

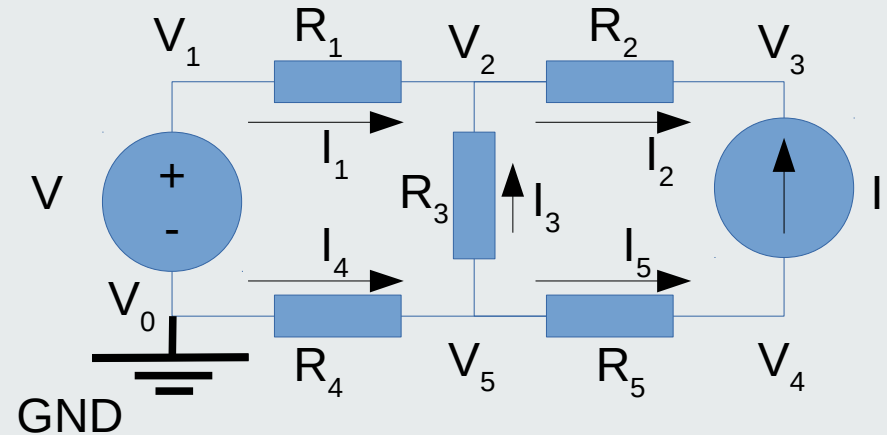

$$V_0 = 0$$

$$V_1 = V$$

$$V_2 = V_1 - R_1 I_1 = \frac{R_3 + R_4}{R_1 + R_3 + R_4} V + \frac{R_1 R_3}{R_1 + R_3 + R_4} I$$

$$V_3 = V_2 - R_2 I_2 = V_1 - R_1 I_1 = \left(1 - \frac{R_1}{R_1 + R_3 + R_4}\right) V + \left(\frac{R_1 R_3}{R_1 + R_3 + R_4} + R_2\right) I$$

$$V_4 = V_5 - R_5 I_5 = \frac{R_4}{R_1 + R_3 + R_4} V - \left(\frac{R_3 R_4}{R_1 + R_3 + R_4} + R_5\right) I$$

$$V_5 = V_0 - R_4 I_4 = \frac{R_4}{R_1 + R_3 + R_4} V - \frac{R_3 R_4}{R_1 + R_3 + R_4} I$$


# Superposition Theorem

Note that the solution for  $V_2$

$$V_2 = \frac{R_3 + R_4}{R_1 + R_3 + R_4} V + \frac{R_1 R_3}{R_1 + R_3 + R_4} I$$

can be expressed as

$$V_2 = V_2|_{V=0} + V_2|_{I=0}$$

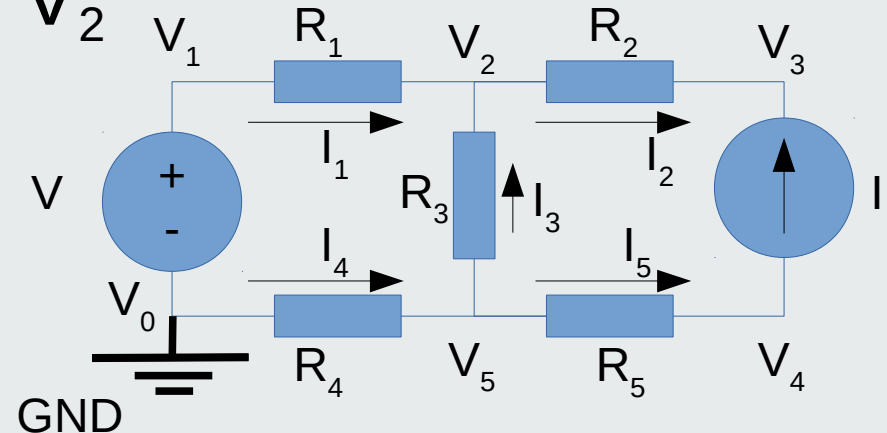

$V_2$  is given by a Linear Superposition of the effects of the independent sources  $V$  and  $I$


This is a consequence of all-linear relationships

# Computing the Effect of $V$ on $V_2$


Switch off current source  $I$

$$I=0 \Rightarrow I_2=I_5=0 \Rightarrow V_2$$

Then use Voltage Divider

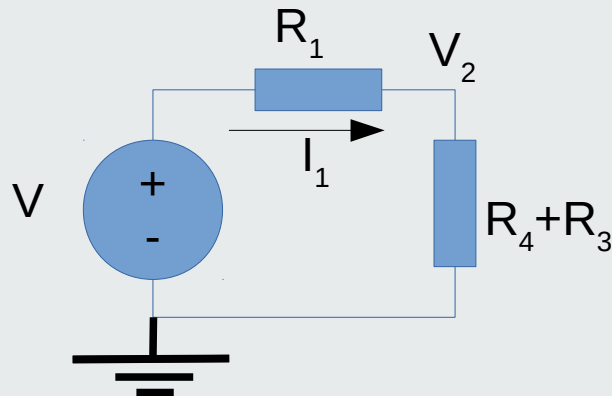
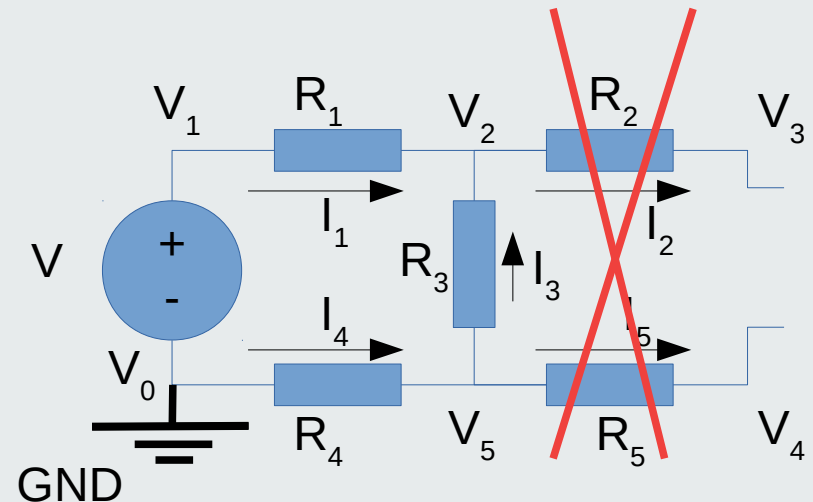
$$V_2 = \frac{R_3 + R_4}{R_1 + R_3 + R_4} V$$



Switching off current source  $I$  leaves an open-circuit between nodes 3 and 4 (internal resistance is infinite).  $R_2$  and  $R_5$  become dead-end branches and may be removed.



# Computing the Effect of $I$ on $V_2$

Switch off voltage source  $V$

$$V=0 \Rightarrow V_1=0 \Rightarrow V_2 = -R_1 I_1$$

Then use Current Divider

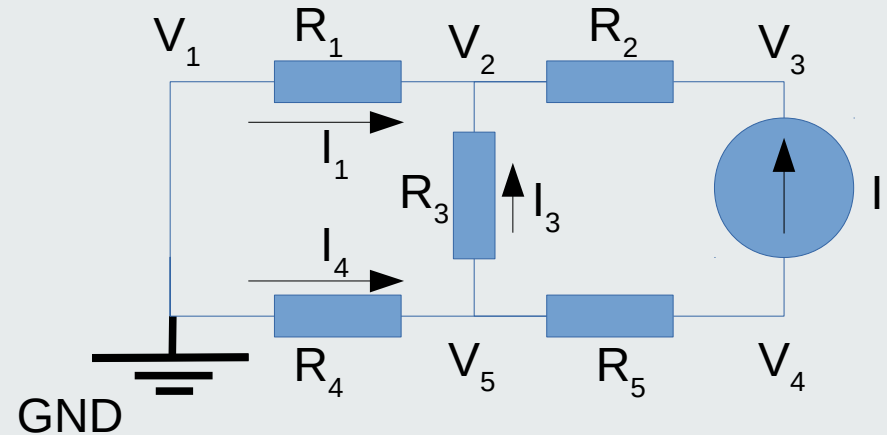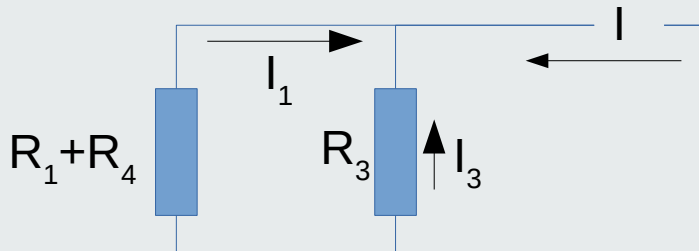
$$-I_1 = \frac{\frac{1}{R_1+R_4}}{\frac{1}{R_1+R_4} + \frac{1}{R_3}} I \Rightarrow V_2 = \frac{R_1 R_3}{R_1+R_3+R_4} I$$



Switching off voltage source  $V$  leaves a short-circuit between nodes 0 and 1 (internal resistance is zero).  $R_1$  and  $R_4$  are now directly connected in a resistor series.


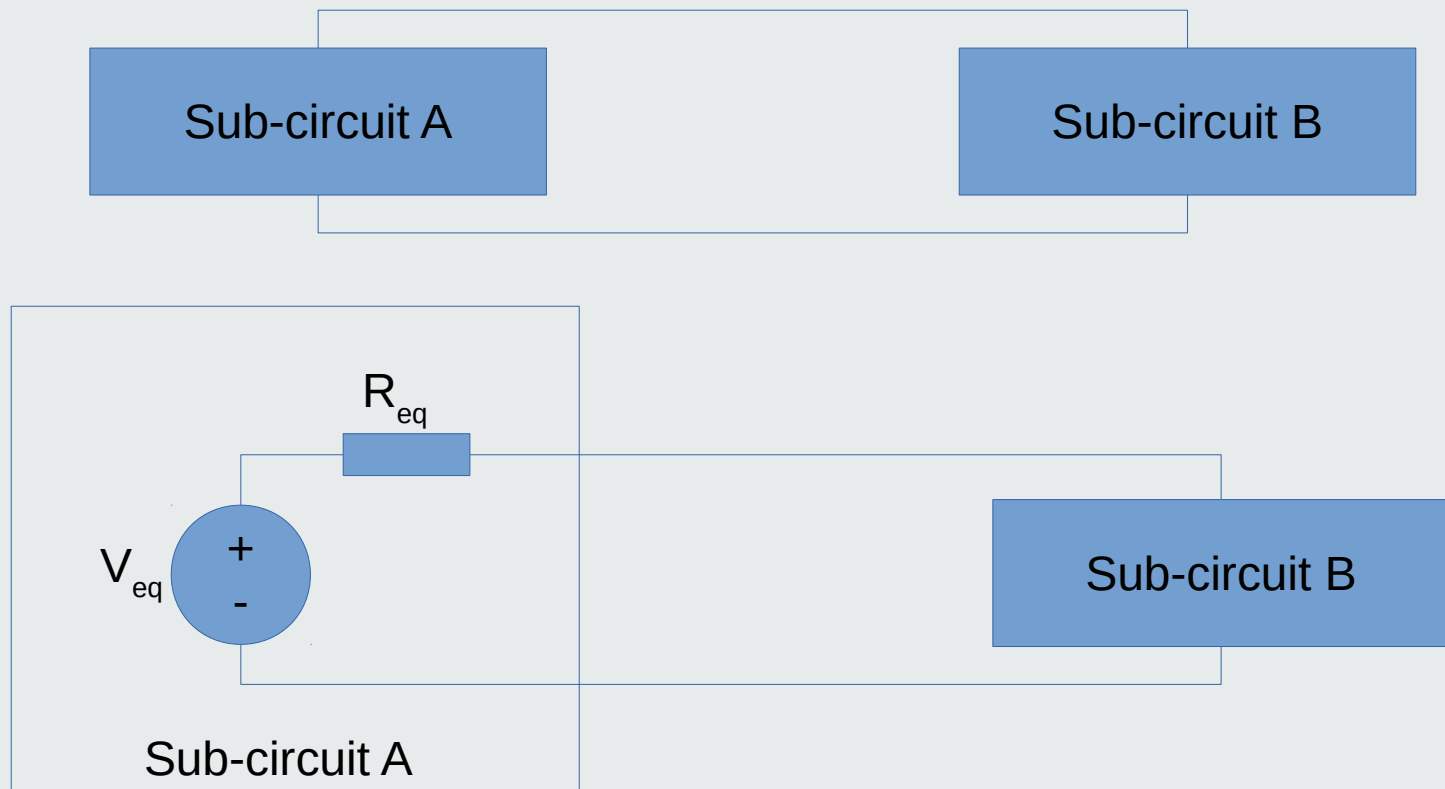
# Thévenin Theorem

Replaces a linear complex 2-port circuit with a simpler 2-port circuit having a voltage source  $V_{eq}$  in series with a resistor  $R_{eq}$





# Thévenin $V_{eq}$ and $R_{eq}$

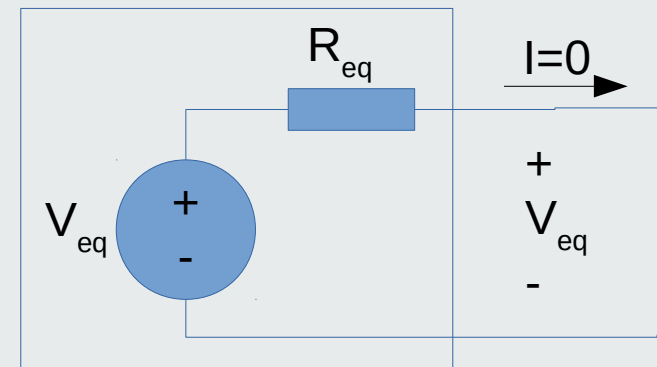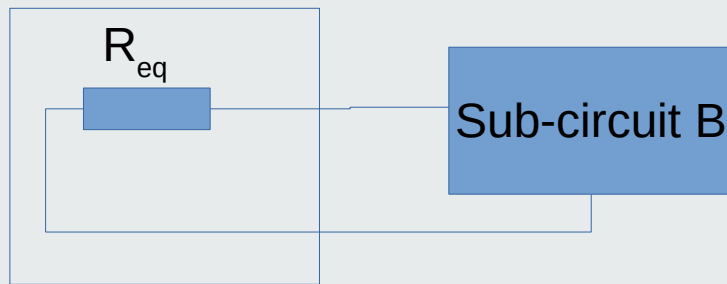


$R_{eq}$  is the equivalent resistor  
when all sources of Sub-circuit A  
are switched off



$V_{eq}$  is the voltage drop between  
the 2 ports if sub-circuit B is  
removed, leaving an open-circuit  
between the ports
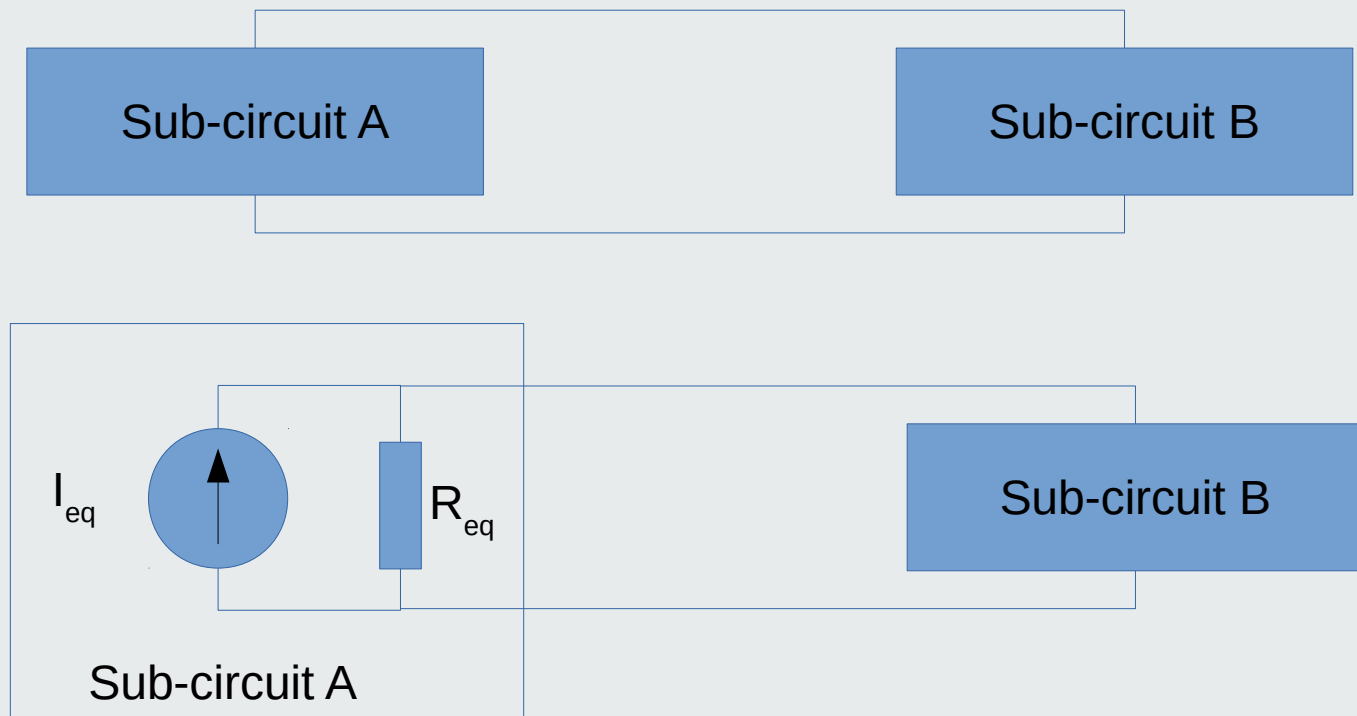
# Norton Theorem


Replaces a linear complex 2-port circuit with a simpler 2-port circuit having a current source  $I_{eq}$  in parallel with a resistor  $R_{eq}$



# Norton $I_{eq}$ and $R_{eq}$

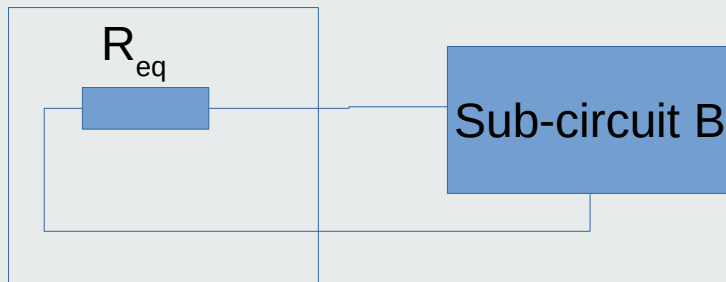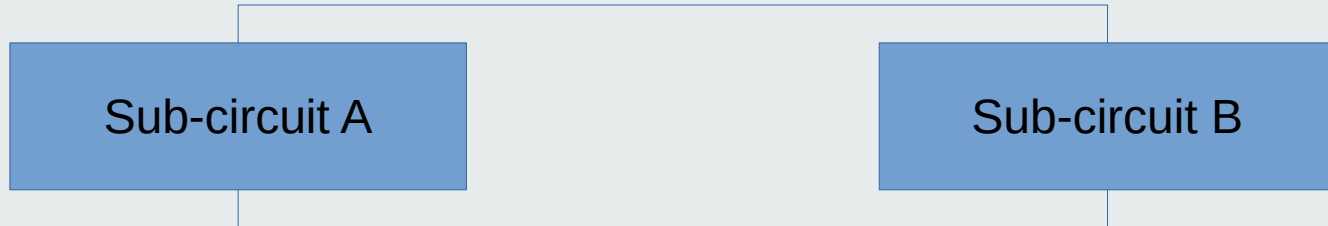

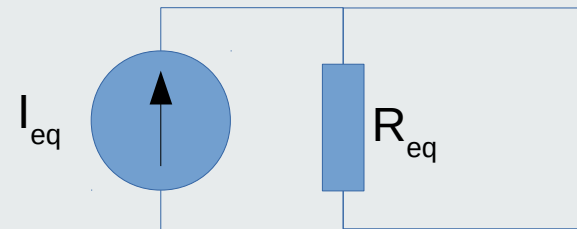$R_{eq}$  is the equivalent resistor  
when all sources of Sub-circuit A  
are switched-off



$I_{eq}$  is the current between the 2  
ports when Sub-circuit B is  
replaced with a shunt (short-  
circuit)


# Relationship between $I_{eq}$ and $V_{eq}$

Applying the Thévenin Theorem to the Norton equivalent (do it as exercise) or


Applying the Norton Theorem to the Thévenin equivalent (do it as exercise) we get the useful relationship:

$$V_{eq} = R_{eq} I_{eq}$$


# Linearly Dependent Sources

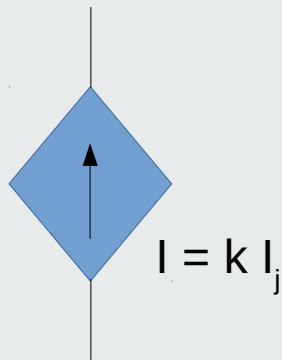

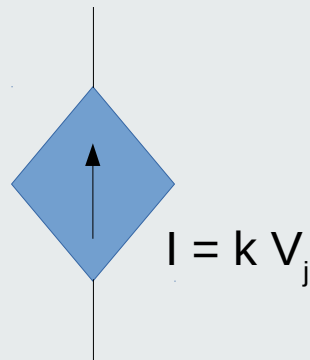
Current  
controlled  
Current  
source  
( $R_i = \infty$ )



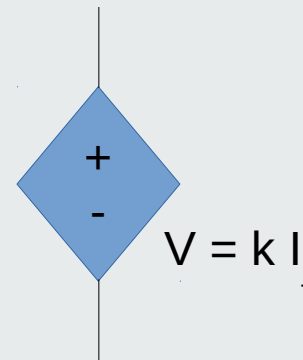Voltage  
controlled  
Current  
source  
( $R_i = \infty$ )



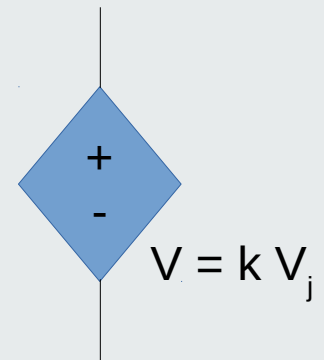Current  
controlled  
Voltage  
source  
( $R_i = 0$ )




Voltage  
controlled  
Voltage  
source  
( $R_i = 0$ )

# Mesh Analysis

A mesh is a loop that contains no other loops

Consider 2 meshes **a** and **b**

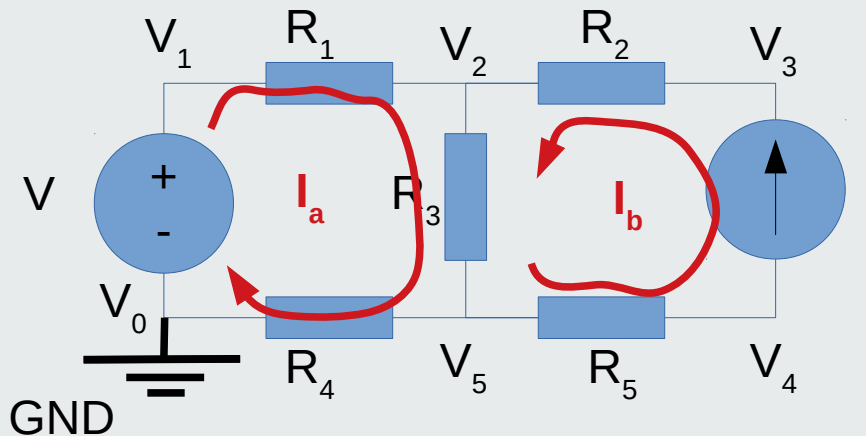

Knowing mesh currents, we can know any node voltages or branch currents, using Ohm's law. For example for  $V_2$ :

$$V = R_1 I_a + R_3 (I_a + I_b) + R_4 I_a \quad (\text{KVL mesh 'a'})$$

$$(R_1 + R_3 + R_4) I_a + R_3 I_b = V$$

$$I_b = I \quad (\text{by inspection})$$

$$\begin{bmatrix} R_1 + R_3 + R_4 & R_3 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \end{bmatrix} = \begin{bmatrix} V \\ I \end{bmatrix}$$

$$I_a = \frac{V - R_3 I}{R_1 + R_3 + R_4}$$


$$V_2 = V - R_1 I_a = V - R_1 \frac{V - R_3 I}{R_1 + R_3 + R_4} = \frac{R_3 + R_4}{R_1 + R_3 + R_4} V + \frac{R_1 R_3}{R_1 + R_3 + R_4} I$$

Same result as before: check
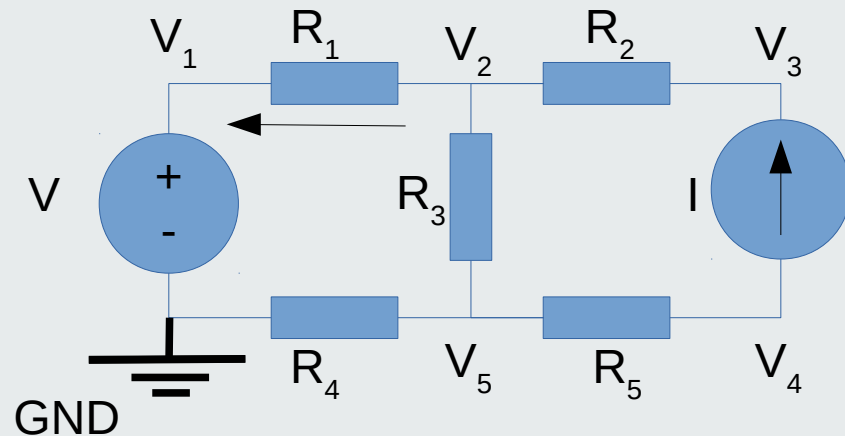
# Node Analysis

Nodes connect components in a circuit. Nodal equations comprise

- KCL in nodes not connected to voltage sources
- Additional equations for nodes related by voltage sources



*KCL equations:*

$$\text{node 2} \rightarrow (V_2 - V_1)G_1 + (V_2 - V_5)G_3 + (V_2 - V_3)G_2 = 0$$

$$\text{node 3} \rightarrow (V_3 - V_2)G_2 - I = 0$$

$$\text{node 4} \rightarrow (V_4 - V_5)G_5 + I = 0$$


$$\text{node 5} \rightarrow (V_5 - V_4)G_4 + (V_5 - V_2)G_3 + (V_5 - V_1)G_1 = 0$$

*Additional equations:*

$$V_1 - V_0 = V$$

$$V_0 = 0$$

# Node Analysis Matrix Form

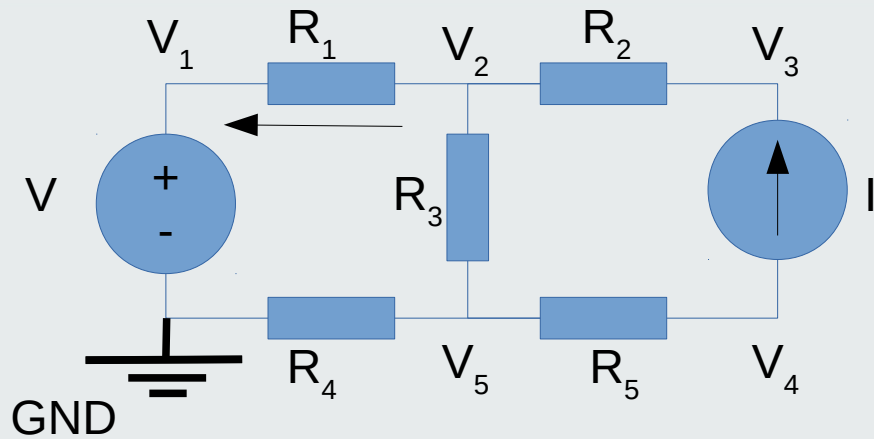

- The nodal method is systematic
- Automatic extraction of nodal equations from circuit description
- Preferred method for circuit simulation
- Solve in Octave!

$$\begin{bmatrix}
 1 & 0 & 0 & 0 & 0 \\
 -G_1 & G_1 + G_3 + G_4 & -G_2 & 0 & -G_3 \\
 0 & -G_2 & G_2 & 0 & 0 \\
 0 & 0 & 0 & G_5 & -G_5 \\
 0 & -G_3 & 0 & -G_5 & G_3 + G_4 + G_5
 \end{bmatrix}
 \begin{bmatrix}
 V_1 \\
 V_2 \\
 V_3 \\
 V_4 \\
 V_5
 \end{bmatrix}
 =
 \begin{bmatrix}
 V \\
 0 \\
 I \\
 -I \\
 0
 \end{bmatrix}$$



# Conclusion

- Analysis for circuits with resistors and independent I/V sources
- Superposition Theorem
- Thévenin and Norton Theorems
- Dependent or controlled sources
- Mesh analysis method
- Nodal Analysis method