

Circuit Theory and Electronics Fundamentals

Lecture 1: Course introduction

- Course introduction
- Circuits: node, branch, loop
- Current and voltage sources
- Resistors, Kirchoff laws, power,
- Resistor series and parallel, voltage and current dividers

About the course

- Basic circuit theory and electronics
- Circuits: components and wires
- Basic components:
 - Voltage and current sources, independent or dependent (controlled)
 - Linear components: resistors, capacitors, inductors, transformers
 - Non-linear components: diodes and transistors
- Basic circuits
 - Circuits containing only linear components
 - Circuits containing linear and non-linear components

About the course (continued)

- Circuit topology: nodes, branches and loops
- Voltage and current signals: static and sinusoidal
- Power and energy
- Analyses: static, time and frequency analysis
- Popular circuits: amplifiers, filters, rectifiers, envelope detectors, logic gates and operational amplifiers

About me: José Teixeira de Sousa

- IST/DEEC: assistant professor
- INESC-ID: researcher
- IObundle: founder
- <https://www.linkedin.com/in/jose-t-de-sou-sa-a34b86/>
- <https://scholar.google.com/citations?user=ai6ekBAAAAAJ&hl=en&authuser=1>

The classes

- Theory lectures
 - 2 x 1h30 per week
- Problems classes
 - 8 sessions x 1h30
- Laboratory sessions
 - 5 sessions x 1h30 per week

Lab sessions

- Groups of 3 students
- 5 lab assignments: 5 circuits to study
- Each assignment: each group shows its work in 10 minutes
- Report:
 - Theoretical analysis: Octave code
 - Simulation analysis: Ngspice code
 - Documentation: report written using Latex
- Marking: very good(4), good(3), ok(2), bad(1), very bad(0)

Lab evaluation criteria

- The lab instructor has 10 minutes to
 - Git clone your group's git repository
 - Run the Makefile, which will
 - Run Octave and generate data and figures for the report
 - Run Ngspice and generate data and figures for the report
 - Compile the Latex report and produce the pdf file
 - Make sure the above works *flawlessly*
 - Check the quality of the work, make sure you don't have obvious mistakes

Software

- Ubuntu 18.4 or 20.4 Linux distribution
 - Real or virtual machine, 40+ GB recommended size
- Linux tools:
 - Bash: Linux terminal command interpreter
 - Useful commands: ls, cd, find, grep, sed
 - Make: (build) procedure automation tool
 - Text editor (Any but Emacs or Vim recommended).
- Ngspice: circuit simulator
- Octave: maths tool
 - Open-source free of charge alternative to Matlab
- Tex Live (full installation): Latex text processor

Evaluation

- Exam or 2 tests:

$$T = \max\{ \text{av}(T1, T2), E1, E2 \}$$

- Lab: L
- Minimum mark on T or L: 8/20
- Mark:

$$\mathbf{M = 0.75T + 0.25L}$$

Tests and exams


- 2 Tests or Exam
- Duration:
 - Tests: 1h30
 - Exam: 3h00
- Check Fénix for dates
- Exam is divided in 2 parts, which may be used to recover one of the tests
 - Each test may only be recovered once

Bibliography

- The Internet: Google it!
- Lecture slides
- Exercises and their resolution
- Lab materials
- Recommended bibliography on Fénix

Let's start: Electric Circuits!

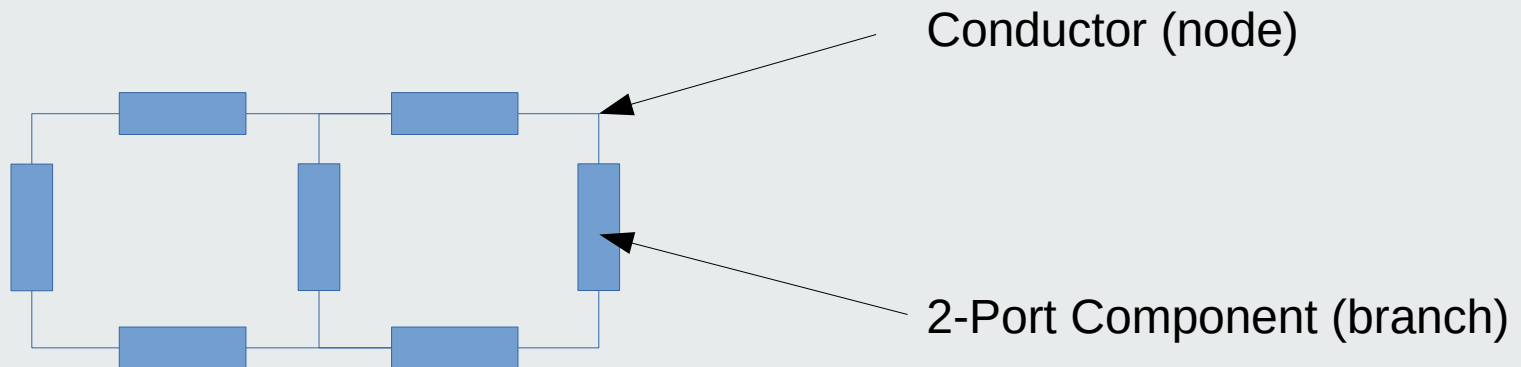2-Port Components (branches)
connected by Conductors (nodes)



Lumped elements approximation: no notion of physical distance => no wave propagation or radiation


Circuits as Graphs

Simplest mathematical model for a circuit:

A graph $G=(V,E)$




V : set of vertices or nodes

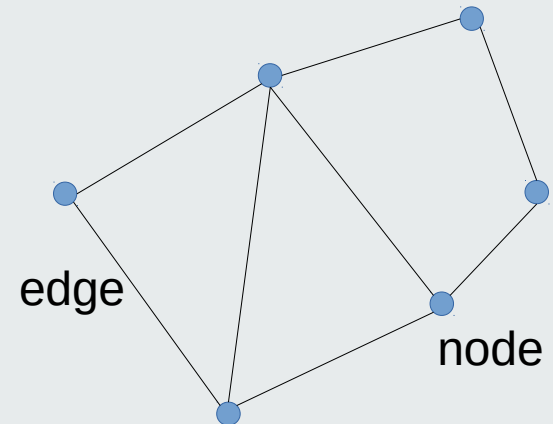E : set of edges or branches (may be labelled to identify function)




Physical quantities

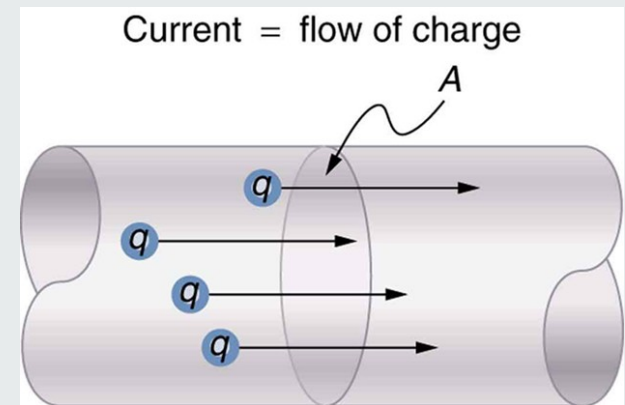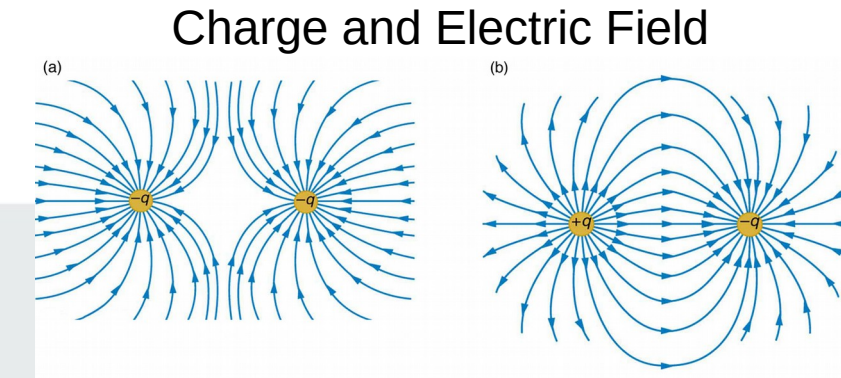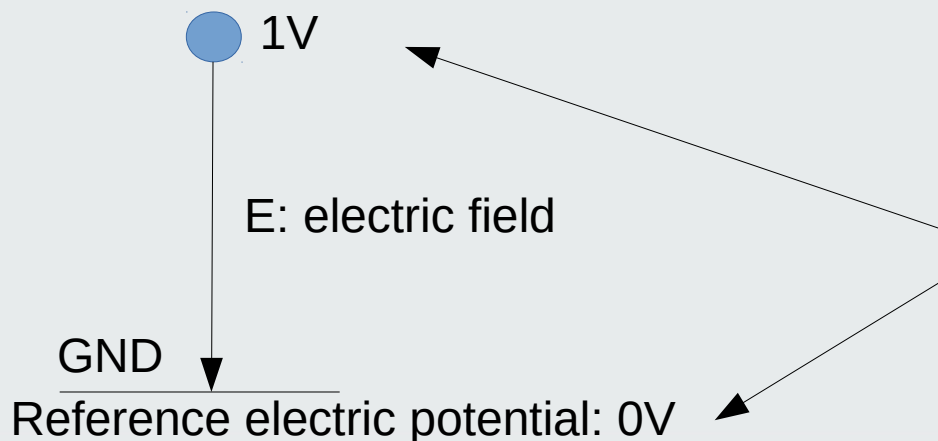- Charge (Q): Coulomb (C)
- Current (I): Ampere ($A = C/s$)
- Voltage (V): Volt ($V = J/C$)




It takes 1 Joule of energy to move a 1 Coulomb charge from GND to 1V Electric Potential


Component: Resistor

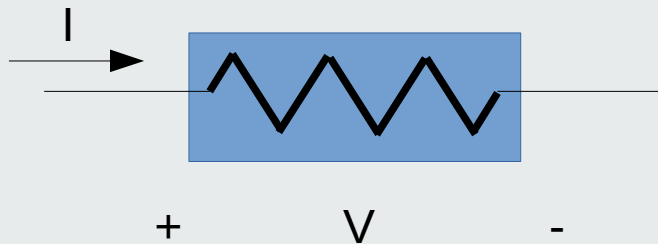

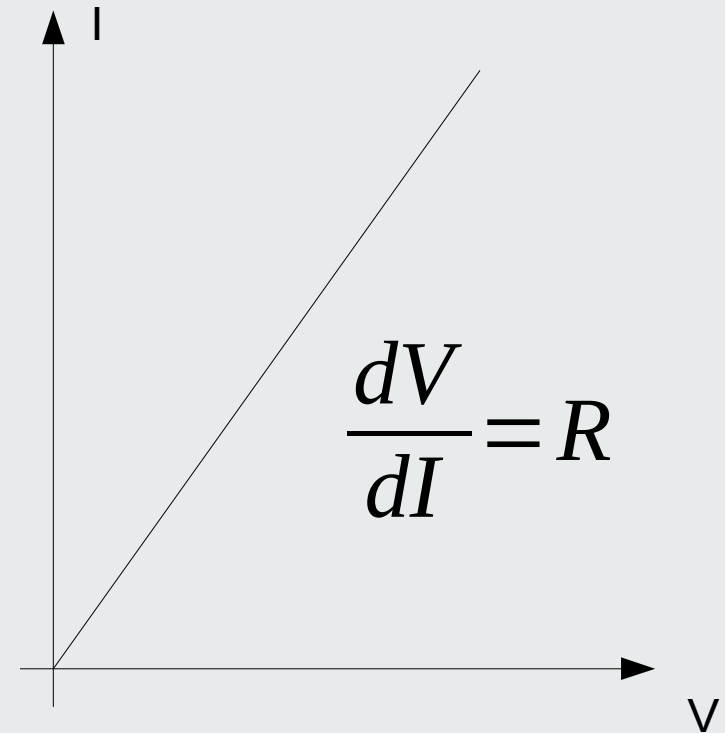
- Linear resistor
- Ohm's law: $V = RI$
- $G = 1/R$ (conductance)
- R is expressed in Ohm: $\Omega = V/A$
- G is expressed in Siemens: $S = \Omega^{-1} = A/V$




Component: Voltage Source

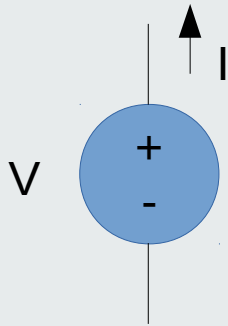

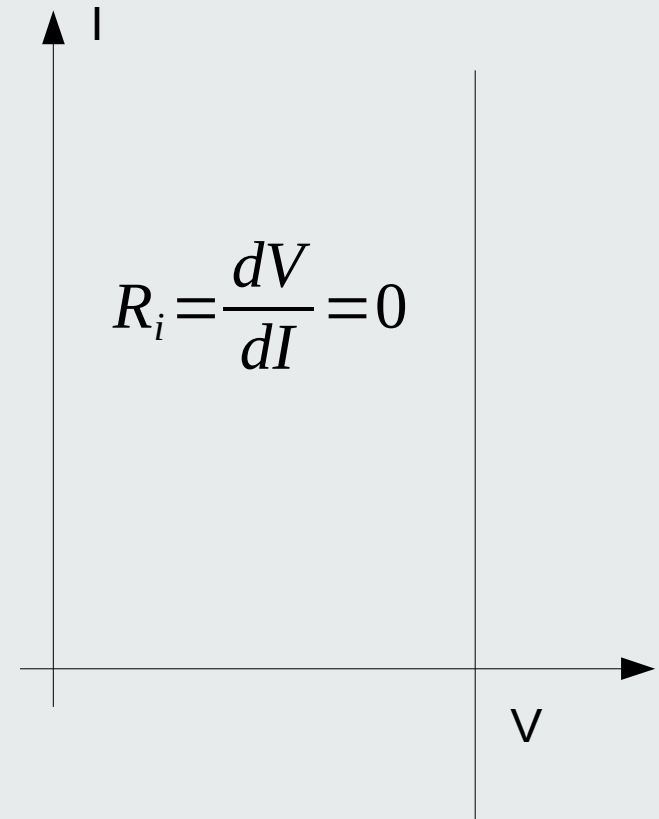
- Imposes voltage V regardless of current I
- Internal resistance is null



Component: Current Source

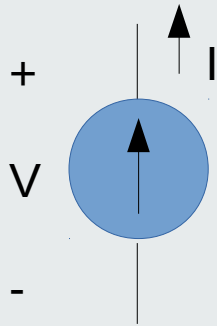

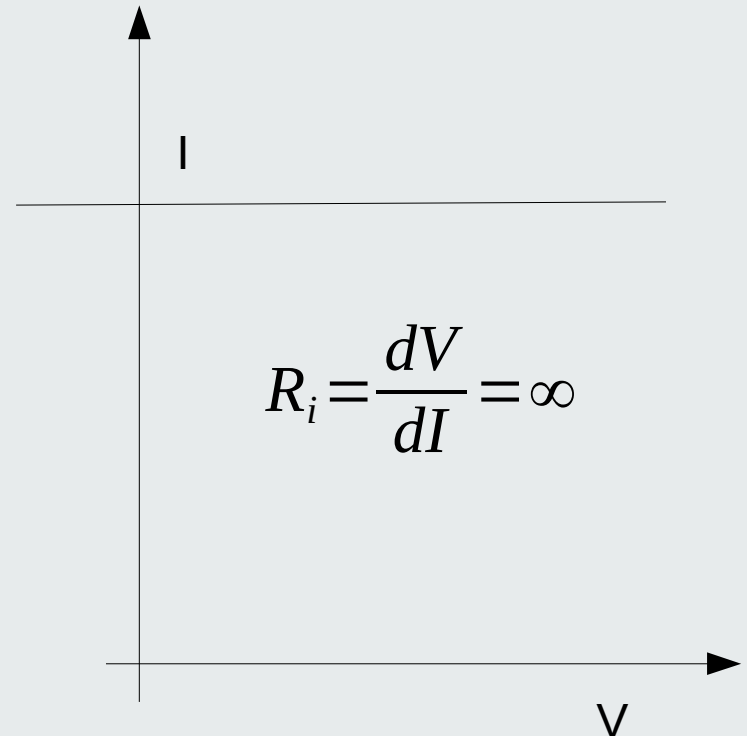
- Imposes current I regardless of voltage V
- Internal resistance is infinite



Kirchhoff Current Law (KCL)

- KCL: sum of currents converging (diverging) in a node is null


$$\sum_{i=1}^n I_i = 0$$

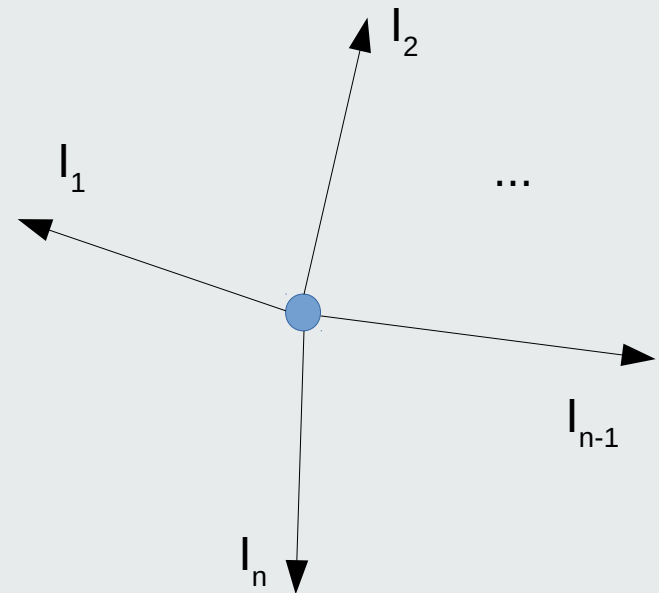

Kirchhoff Voltage Law (KVL)

- KVL: sum of Voltages in a circuit loop is null

$$\sum_{i=1}^n V_i = 0$$

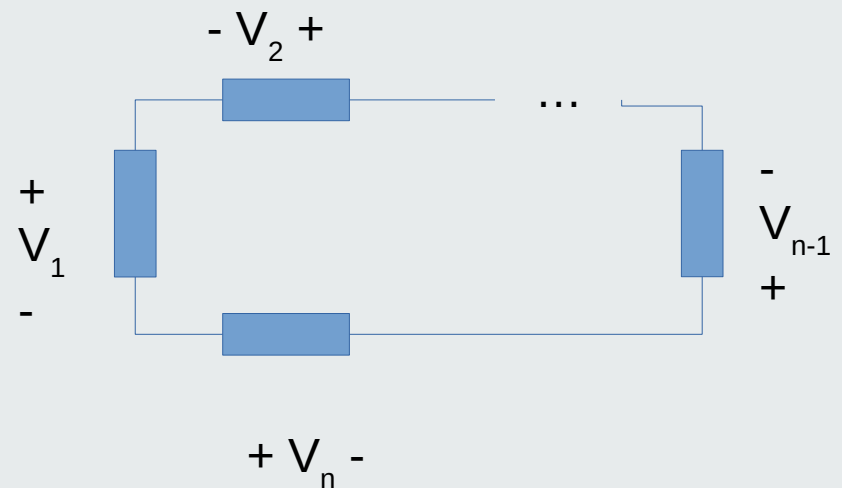


Power

- Power (P) is a measure of Energy (E) per Time (t) unit
- P(t) used to compute the energy supplied or consumed by a component during a time interval
- Power is expressed in Watt units: $W = J / s$
- With the directions for Voltage V and Current I as defined in the figure

$$P = V I$$

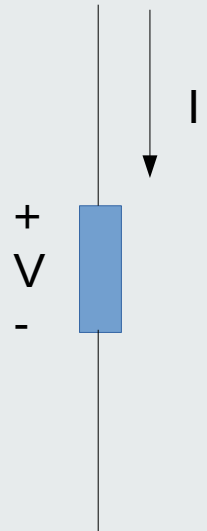- If $P > 0$ the component is consuming energy
- If $P < 0$ the component is supplying energy




Series of Resistors

$$V = \sum_{i=1}^n V_i \quad \text{KVL}$$

$$V = \sum_{i=1}^n R_i I \quad \text{Ohm's Law}$$

$$V = \left(\sum_{i=1}^n R_i \right) I$$

$$R = \sum_{i=1}^n R_i$$

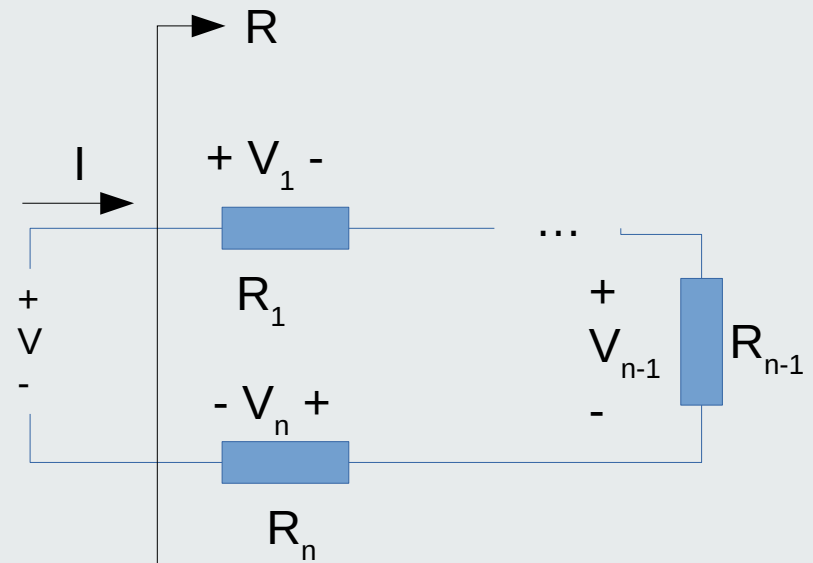


Parallel of Resistors

$$I = \sum_{i=1}^n I_i \quad \text{KCL}$$

$$I = \sum_{i=1}^n \frac{V}{R_i} \quad \text{Ohm's Law}$$

$$I = \left(\sum_{i=1}^n \frac{1}{R_i} \right) V$$
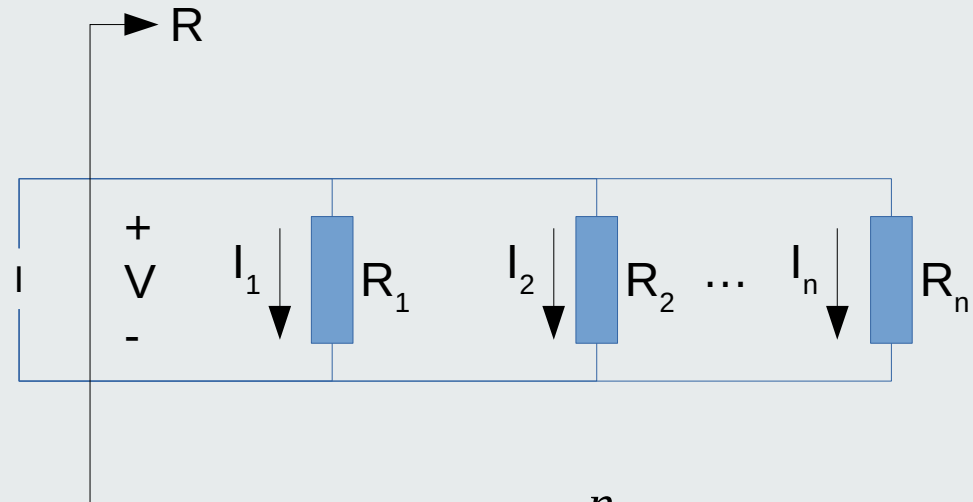
$$R = \frac{1}{\sum_{i=1}^n \frac{1}{R_i}}$$



$$G = \sum_{i=1}^n G_i$$

Voltage Divider

$$V_i = R_i I$$


$$V_i = R_i \frac{V}{R}$$

Ohm's Law

$$R = \sum_{j=1}^n R_j$$

R Series

$$V_i = \frac{R_i}{\sum_{j=1}^n R_j} V$$

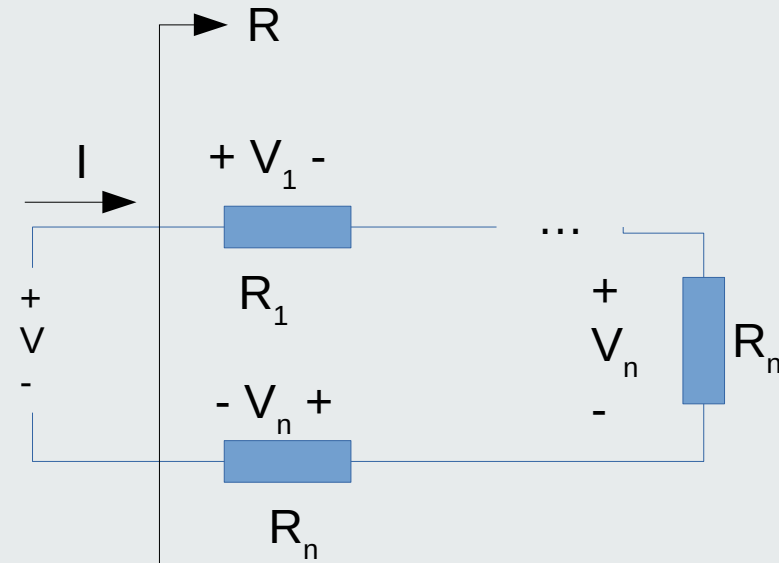

Current Divider

Ohm's Law


$$I_i = \frac{V}{R_i}$$

$$I_i = \frac{(RI)}{R_i}$$

R Parallel

$$R = \frac{1}{\sum_{j=1}^n \frac{1}{R_j}}$$
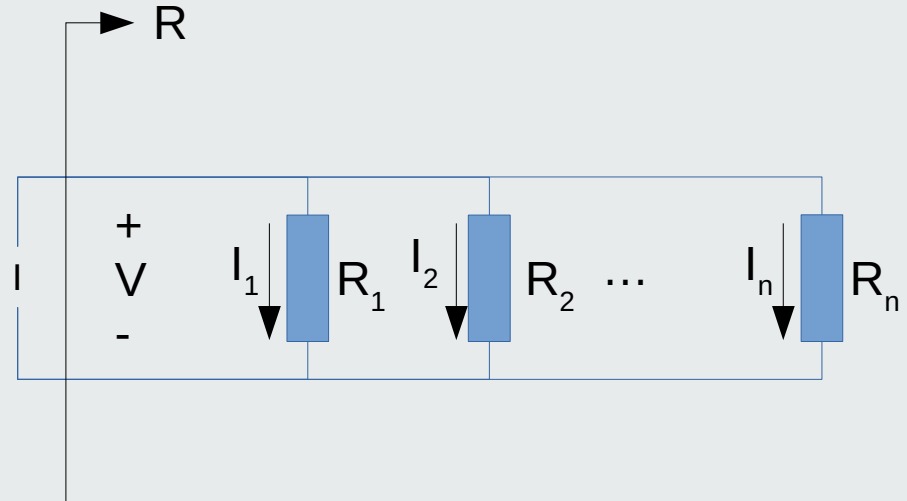
$$I_i = \frac{\frac{1}{R_i}}{\sum_{j=1}^n \frac{1}{R_j}} I$$



$$I_i = \frac{G_i}{\sum_{j=1}^n G_j} I$$

Conclusion

- Circuit, nodes, branches and loops
- Voltage and current sources
- Resistors and Ohm's Law: $V = RI$
- Power and energy: $P = VI$, E is integral of power over time
- Kirchhoff laws:
 - sum of currents $\sum I_i$ diverging in node is null
 - sum of voltages $\sum V_i$ diverging in loop is null
- Series of resistors: sum them up to get equivalent resistor
- Parallel of resistors: sum the conductances up to get equivalent conductance; resistance is the conductance inverse
- Voltage divider: $V_i = (R_i/R) * V$, where V_i is voltage across resistor R_i in series of resistors having total resistance R connected to voltage source V
- Current divider: $I_i = (G_i/G) * I$, where I_i is current through resistor R_i in parallel of resistors having total conductance G connected to current source I