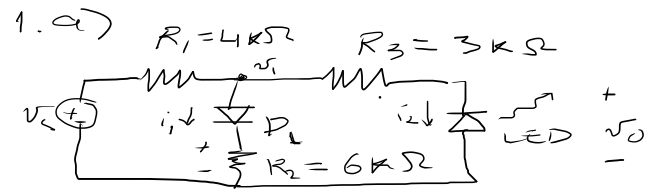


EXAME 8/7/21 - Part 2 resolution



$$V_S = 2 \text{ V} \Rightarrow D_1 \text{ ON, LED OFF}$$

$$i_2 = 0 \Rightarrow V_O = V_1 = V_{R_2} + V_{D_1 \text{ ON}}$$

$$= \frac{R_2}{R_1 + R_2} (V_S - V_{D_1 \text{ ON}}) + V_{D_1 \text{ ON}} = 1.4 \text{ V}$$


(0.5 V)

$$V_S = -3 \text{ V} \Rightarrow D_1 \text{ OFF, LED ON} \Rightarrow V_O = -V_{LED \text{ ON}} = -1 \text{ V}$$

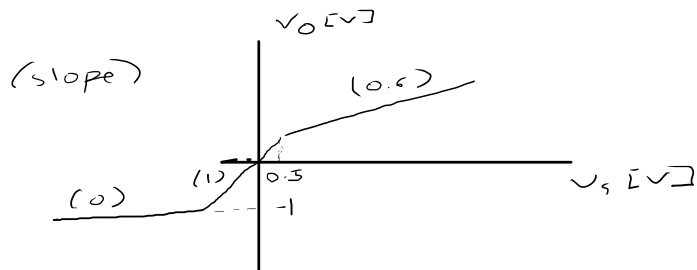b) $V_S < -1 \text{ V} \Rightarrow D_1 \text{ OFF, LED ON} \Rightarrow V_O = -1 \text{ V}$



$$-1 \text{ V} \leq V_S < 0.5 \text{ V} \Rightarrow D_1, \text{ LED OFF} \Rightarrow i_1 = i_2 = 0 \Rightarrow V_O = V_S$$

$$V_S \geq 0.5 \text{ V} \Rightarrow D_1 \text{ ON, LED OFF} \Rightarrow V_O = V_{R_2} + V_{D_1 \text{ ON}} = \frac{R_2}{R_1 + R_2} V_S + \frac{R_1}{R_1 + R_2} V_{D_1 \text{ ON}}$$




$$V_O = 0.6 V_S + 0.2 \text{ V}$$

c) $v_s = 2 \sin(\omega t)$

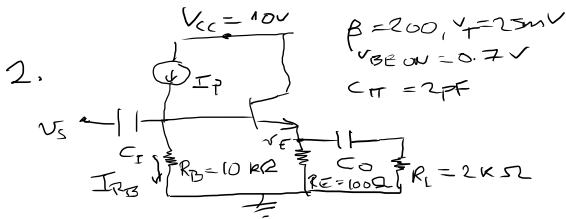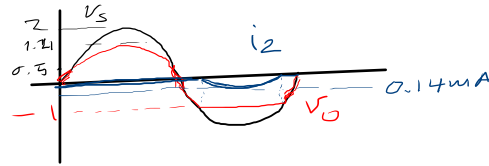

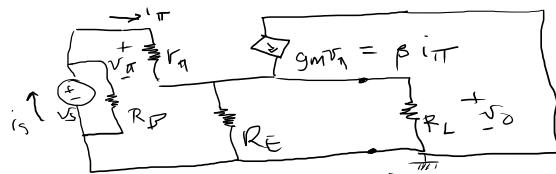b) Incremental circuit for postband

$V_{CC} \equiv GND$
 $I_P \equiv \text{open-circuit}$
 $C_I, C_O \equiv \text{short-circuit}$
 $r_{\pi} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} \approx 83.3 \Omega$



$Z_i = (r_{\pi} + (1+\beta)R_E) \parallel R_B = 6.67 k\Omega$


$A_v = \frac{v_o}{v_s} = \frac{(1+\beta)R_E}{r_{\pi} + (1+\beta)R_E} \approx 1$
 Voltage divider
 $Z_o = r_{\pi} \parallel \frac{1}{g_m} \parallel R_E \approx 0.41 \Omega$

d) Instantaneous power is $p(t) = v(t)i(t)$
 Max occurs where i is max since $v = V_{D(on)}$ is fixed
 $i_{1 \max} = \frac{2 - V_{D(on)}}{R_1 + R_2}$, $-i_{2 \max} = \frac{2 - V_{LED \text{ on}}}{R_1 + R_3}$

$P_{1 \max} = V_{D(on)} i_{1 \max} = 75 \mu W$ $P_{2 \max} = V_{LED \text{ on}} i_{2 \max} = 143 \mu W$

a) $V_E = 6V$ at 0.7, All capacitors open-circuit
 $I_E = \frac{V_E}{R_E} = 60 \text{ mA}$, $I_B = \frac{I_E}{\beta + 1}$, $I_{RB} = \frac{V_E + 0.7}{R_B}$
 $I_P = I_B + I_{RB} = 0.97 \text{ mA}$

c)

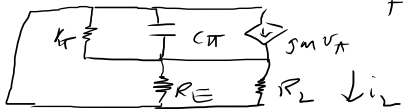Find equivalent resistor seen from C_{π}


$$R_{eq} = r_{\pi} \parallel R_E \parallel \frac{1}{g_m} \parallel R_L \approx \frac{1}{g_m} \approx Z_o$$


$$f_{high} = \frac{1}{2\pi C_{\pi} R_{eq}} \approx 192 \text{ GHz}$$

This is a low-pass filter from the perspective of $T(s) = -\frac{i_L(s)}{i_s(s)}$

Note that this voltage follower circuit has $A_{v\pi} \approx 1$ and its purpose is to amplify current to give to the load

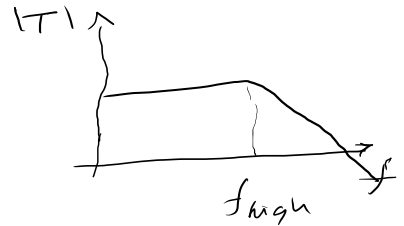When C_{π} becomes a short-circuit $g_m v_{\pi} = 0$
 \Rightarrow no more current gain!



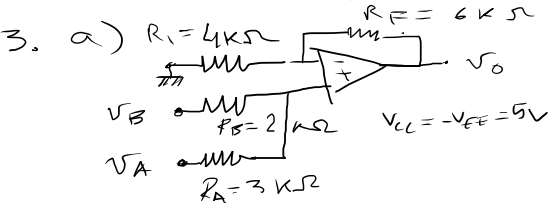


Superposition

$$V_O = \left(\underbrace{\frac{R_B}{R_A + R_B}}_{\text{voltage divider}} V_A + \underbrace{\frac{R_A}{R_A + R_B}}_{\text{voltage divider}} V_B \right) \underbrace{\left(1 + \frac{R_F}{R_1} \right)}_{\text{non-inverting amp.}} \quad (1)$$

$V_A = -0.5 \text{ V}$, $V_B = 5 \text{ V} \Rightarrow V_O = 7 \text{ V}$ but the OP-AMP saturates and

$$\boxed{V_O = 5 \text{ V}}$$

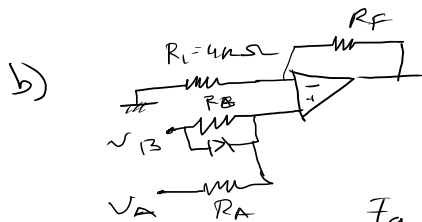

$$V_A = 1 \text{ V}, V_B = -4 \text{ V}, V_D = - \frac{R_B}{R_A + R_B} (V_A - V_B) < 0$$

Diode is OFF



Eq. (1) applies and $V_O = -5 \text{ V}$

c) $V_A = -2 \cos(\omega t)$, $V_B = 2 \text{ V}$

$\frac{I_f (V_B - V_A)}{R_A + R_B} = 0.7 \Leftrightarrow V_A = 0.25$ the diode is at conduction threshold

$$V_A \leq 0.25 \rightarrow D \text{ ON} \rightarrow V_O = (V_B - 0.7) \left(1 + \frac{R_F}{R_1} \right) = 3.25 \text{ V}$$
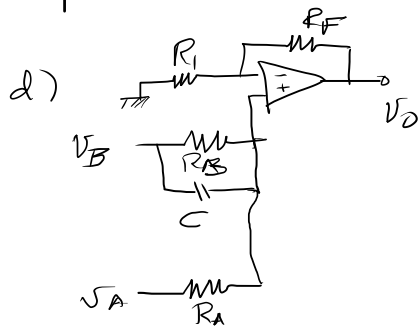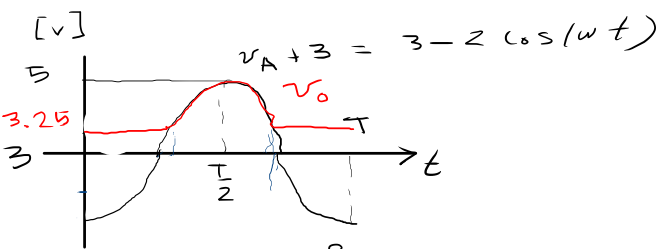
$$V_A > 0.25 \rightarrow D \text{ OFF, eq. (1) applies} \rightarrow V_O = 3 + V_A$$



$$Z_B = R_B \parallel \frac{1}{sC} = \frac{R_B}{1 + sCR_B}$$

$$f = 1 \text{ kHz} \Rightarrow Z_B = \frac{R_B}{1 + j2\pi fCR_B}$$

$$v_A = \cos(\omega t) \text{ V}$$

$$v_B = -1 \text{ V}$$

$$v_0 = \underbrace{\left(\frac{Z_B}{R_A + Z_B} v_A \right)}_{\substack{v_A \text{ contribution} \\ \text{varies with } f}} + \underbrace{\left(\frac{R_A}{R_A + R_B} v_B \right)}_{\substack{v_B \text{ contribution} \\ \text{is static}}} \left(1 + \frac{R_F}{R_1} \right)$$

non-inverting amp form.

$$v_0 = v_{0A} + v_{0B}$$

$$v_{0B} = \frac{R_A}{R_A + R_B} \left(1 + \frac{R_F}{R_1} \right) (-1) = -1.5 \text{ V}$$

$$\tilde{v}_{0A} = \frac{Z_B}{Z_B + R_A} \left(1 + \frac{R_F}{R_1} \right) = 0.40728 - j0.49133 \text{ V}$$

$$v_{0A}(t) = |\tilde{v}_{0A}| \cos(\omega t + \angle \tilde{v}_{0A})$$

$$v_0(t) = 0.64 \cos(\omega t - 0.88) - 1.5 \text{ V}$$