

# Circuit Theory and Electronics Fundamentals


## Lecture 18: The Metal Oxide Semiconductor Field Effect Transistor

- Field Effect Transistors
- The Metal Oxide Semiconductor Field Effect Transistor (MOSFET):
  - Operation regions
  - Large signal model (DC)
  - Small signal model (AC)
  - Spice model
  - Comparison with BJT


# The Field Effect Transistor

- The Field Effect Transistor (FET) is another way to realize a controlled current source
- Unipolar device: only one type of carrier (hole or electron) contributes electric current
- FET types:
  - Junction FET (JFET)
  - Metal Oxide Semiconductor FET (MOSFET)
- 4-pin device: Gate, Source, Drain and Body

# The JFET

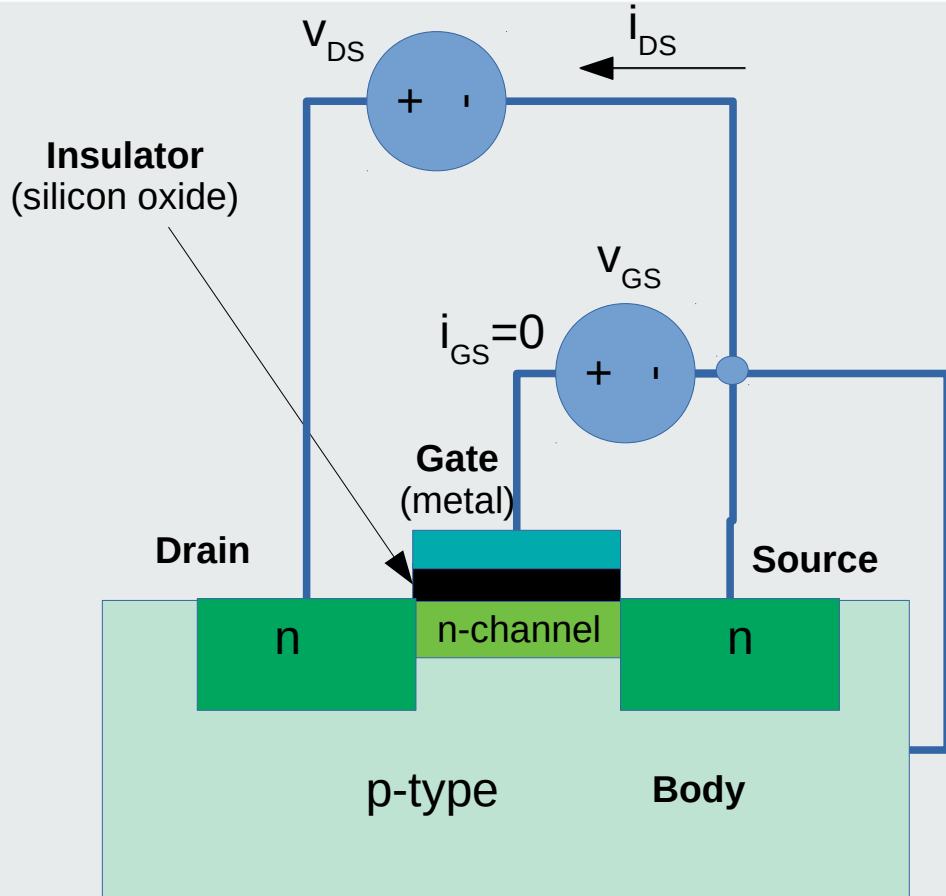


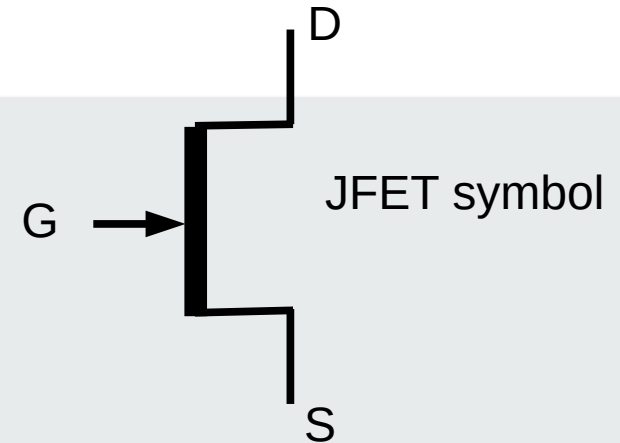
The Body is always always connected to lowest voltage in chip



## How the JFET works

- Channel physically present
- Current flows when positive  $v_{DS}$  applied
- A negative  $v_{GS}$  will deplete the channel and decrease the current until cut off
- For constant  $v_{GS}$  the current saturates with increasing  $v_{DS}$

# The MOSFET

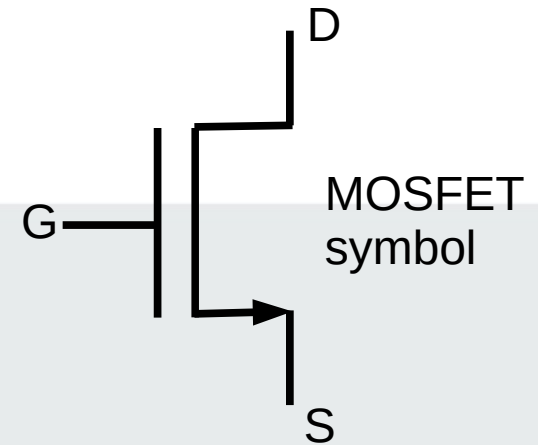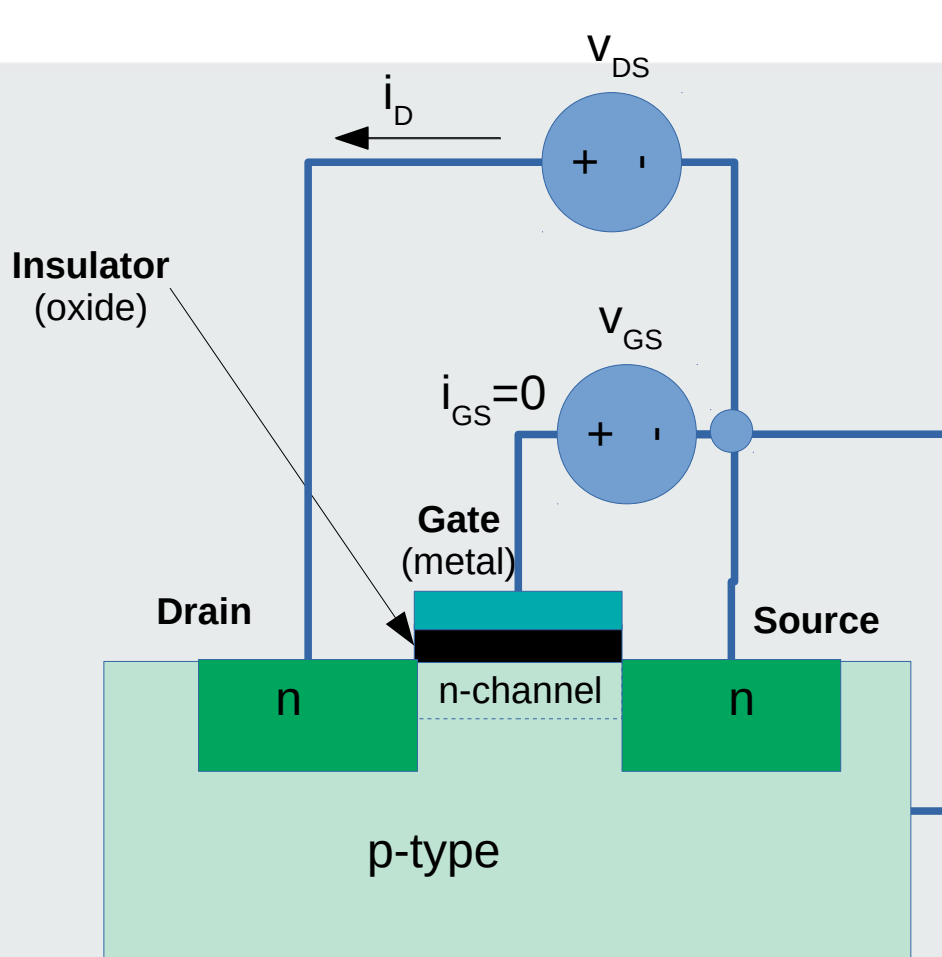

## How the MOSFET works

- Channel **not** physically present
- Channel is created when high enough  $v_{GS}$  applied
- Current flows when channel present and positive  $v_{DS}$  applied
- A negative or insufficient  $v_{GS}$  will cut off the device
- For a constant  $v_{GS}$  the current saturates with increasing  $v_{DS}$

# The MOSFET operation regions

- **Source** and **drain** are physically indistinguishable if no electric field applied
- When an electric field is applied
  - the **drain** is the higher potential terminal
  - The **source** is the lower potential terminal
  - Electrons move from source to drain (current flows from drain to source)
- The **gate** controls the amount of current that flows
- If  $v_{GS} < V_T$  the MOSFET is in the **CUT-OFF region** – no current
  - $V_T$  is the threshold voltage for MOSFETs (not to be confused with Diode's and BJT's thermal voltage  $V_T$ !)
- If  $v_{GS} \geq V_T$  and  $v_{DS} \leq v_{GS} - V_T$  the MOSFET is in the **OHMIC** or **TRIODE region** and behaves like a  $v_{GS}$  controlled resistor
- If  $v_{GS} \geq V_T$  and  $v_{DS} \geq v_{GS} - V_T$  the MOSFET is in the **SATURATION region** and behaves like a  $v_{GS}$  controlled current source

# The MOSFET large signal model

$$i_D = 0$$

Cut-off region

$$I_D = k[2(v_{GS} - V_T)v_{DS} - v_{DS}^2]$$

Triode or Ohmic region


$$I_D = k(v_{GS} - V_T)^2$$

Saturation region


$$v_{DS} = (v_{GS} - V_T)$$

$$k = \frac{1}{2} \mu C_{ox} \frac{W}{L} \quad [AV^{-2}]$$

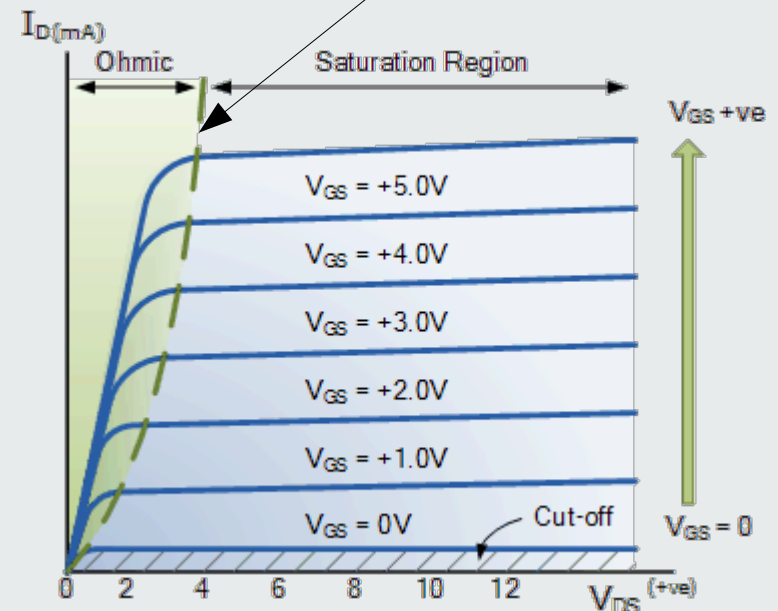$\mu$ : Carrier mobility  
 $C_{ox}$ : Oxide layer capacity  
 $W$ : Channel effective width  
 $L$ : Channel effective length




# The p-channel MOSFET

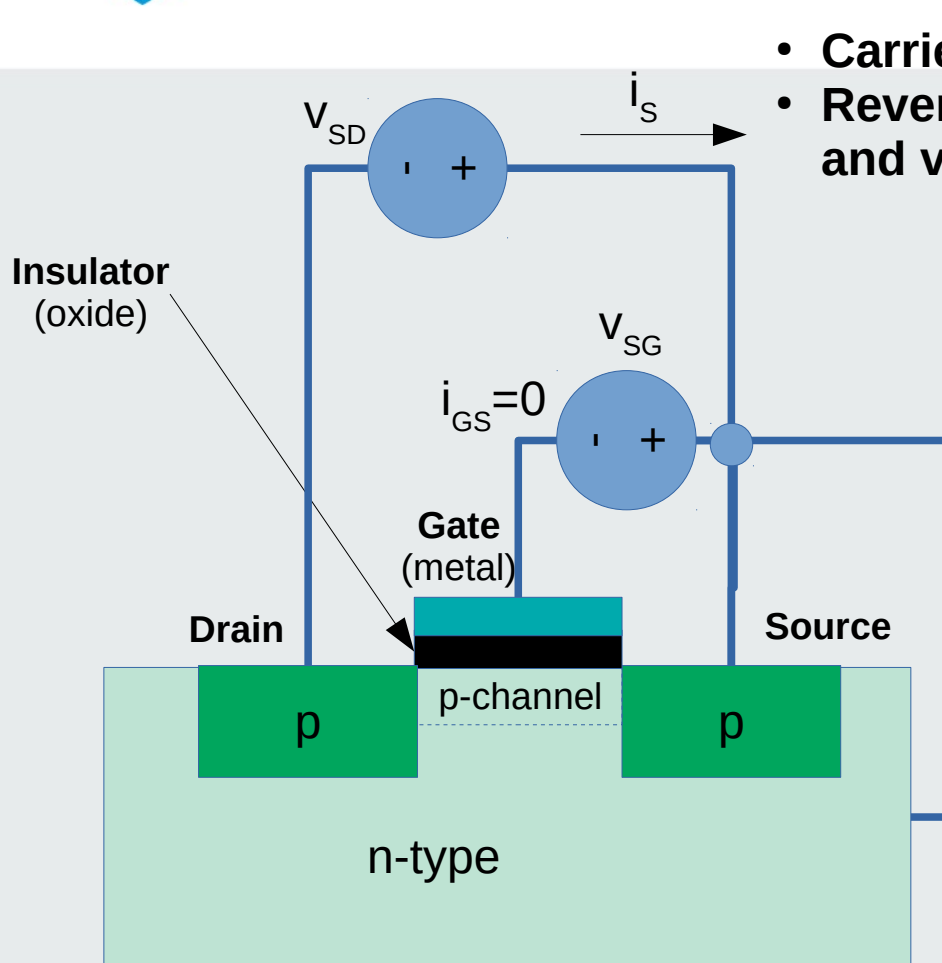

- Carriers are holes
- Reverse all currents and voltages
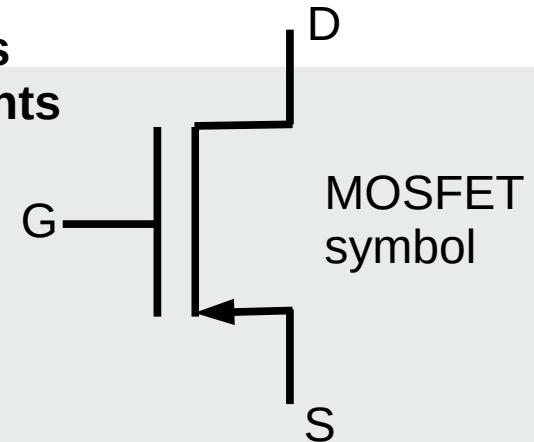
$$\begin{aligned} i_D &\rightarrow i_S \\ v_{GS} &\rightarrow v_{SG} \\ v_{DS} &\rightarrow v_{SD} \end{aligned}$$



$$I_S = 0$$

Cut-Off

$$I_S = k [2(v_{SG} - V_T)v_{SD} - v_{SD}^2]$$


Triode

$$I_S = k (v_{SG} - V_T)^2$$

Saturation


$$k = \frac{1}{2} \mu C_{ox} \frac{W}{L} [AV^{-2}]$$

# The MOSFET cut-off region – no channel

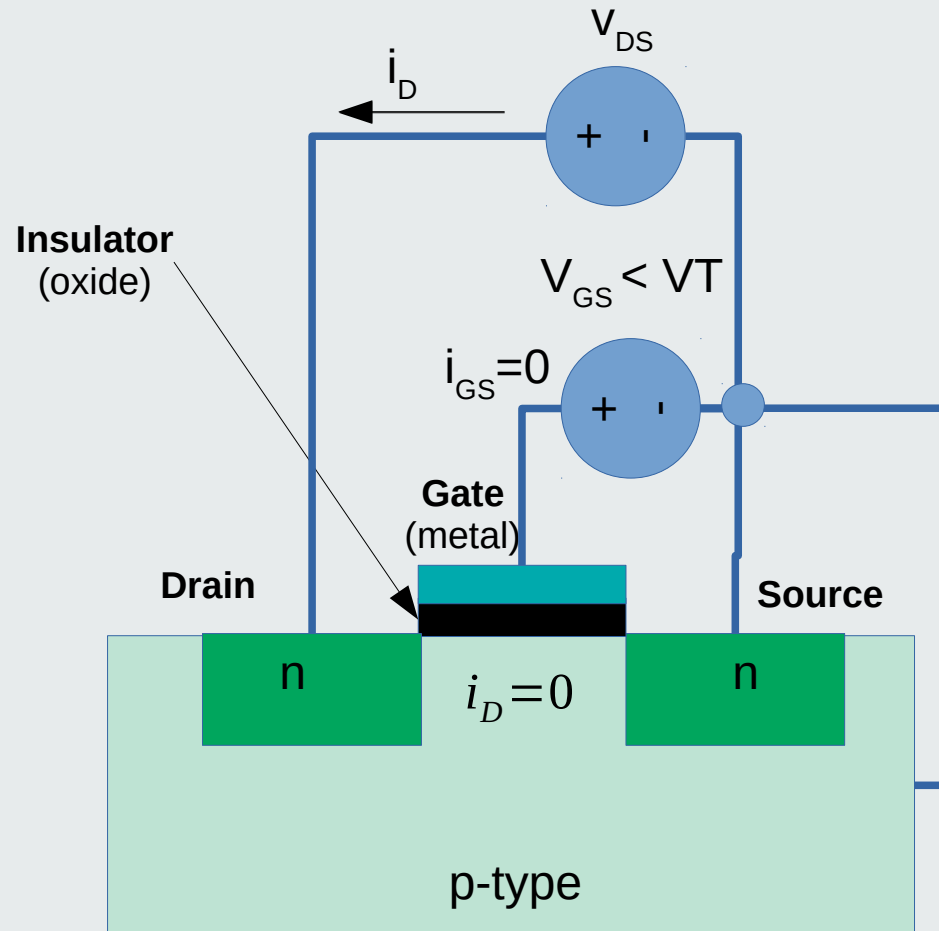




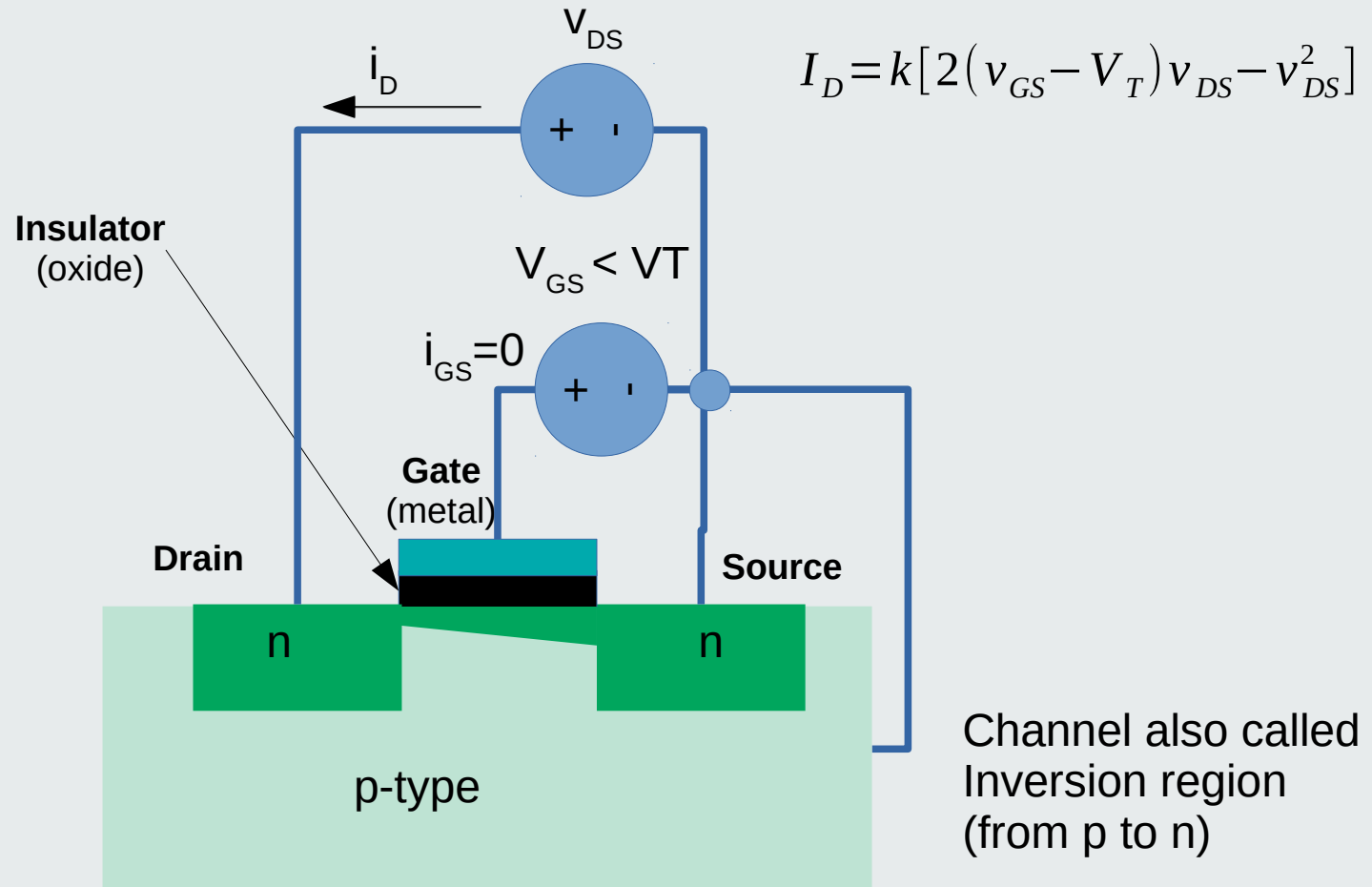
# The MOSFET triode region – channel present


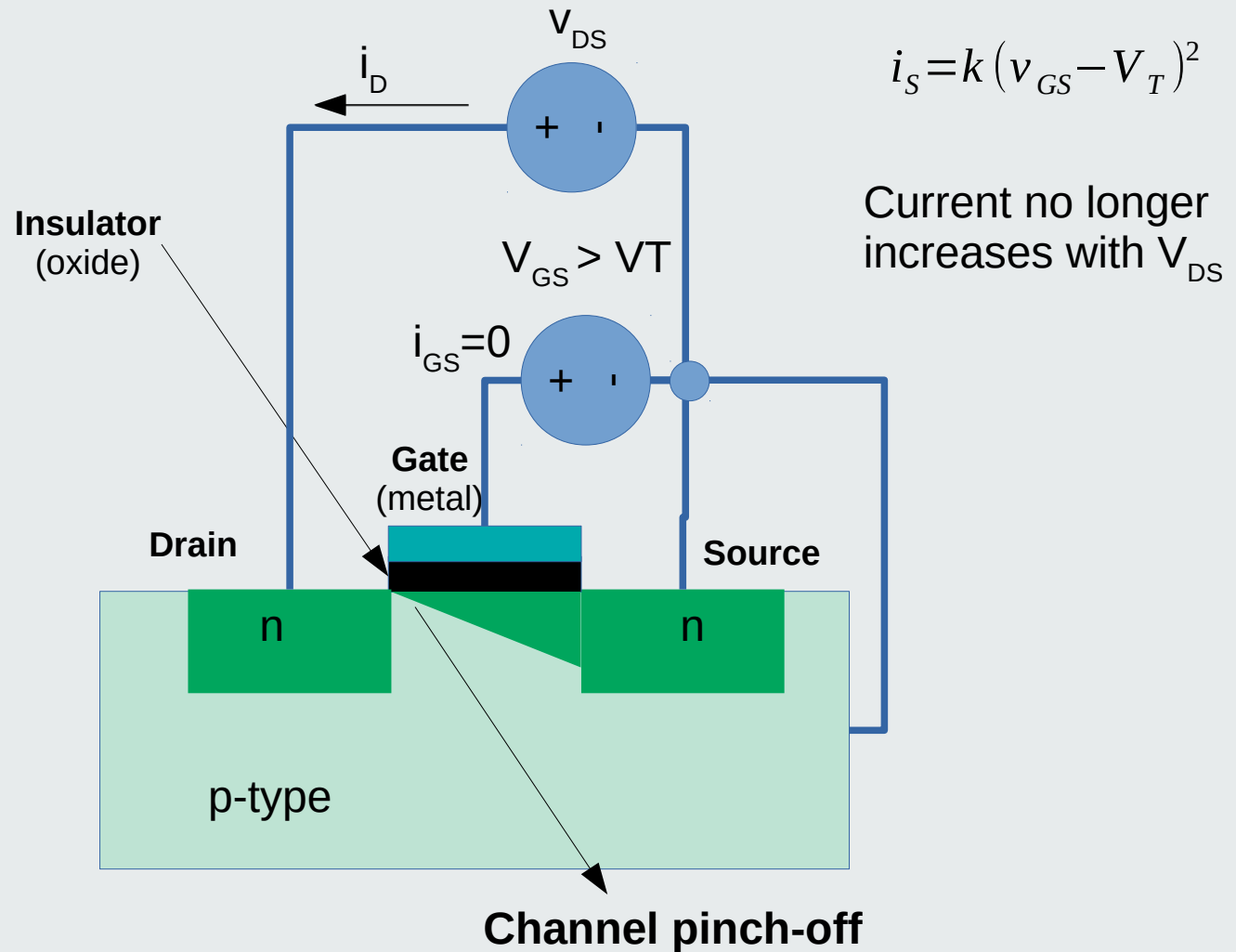
# The MOSFET saturation region – channel pinch-off



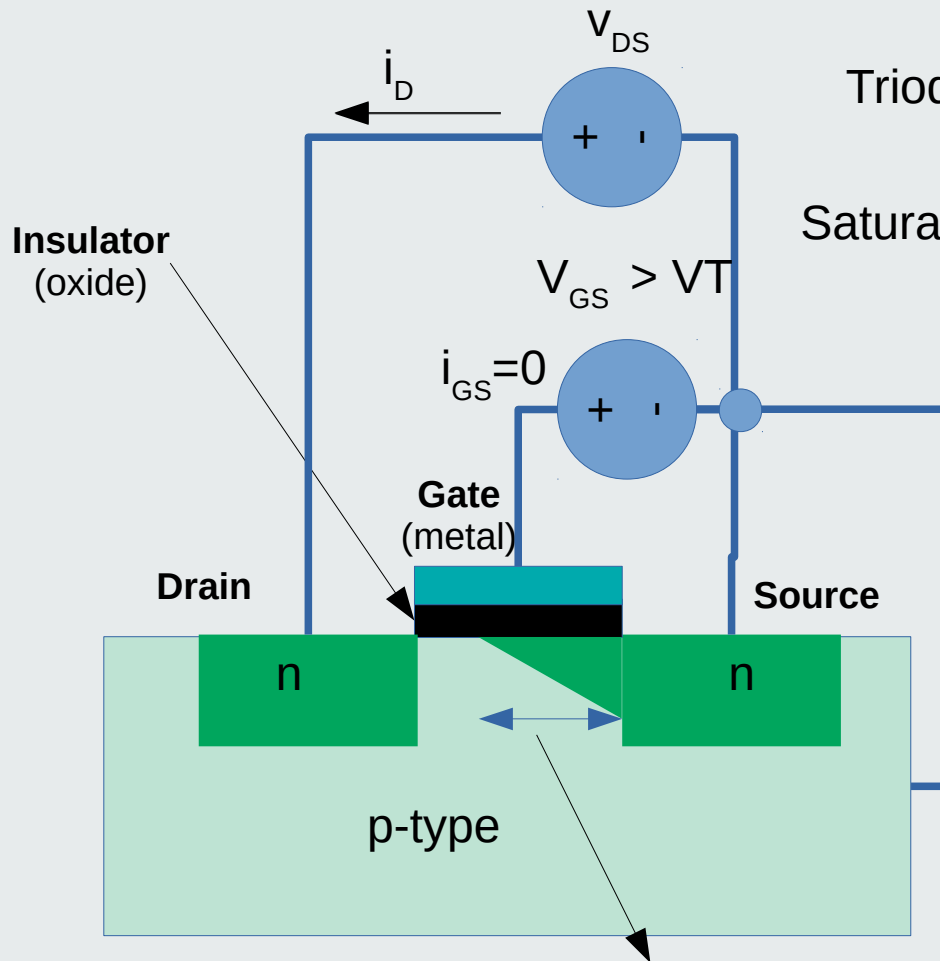
# The MOSFET in saturation – channel length modulation



Triode  $I_D = k[2(v_{GS} - V_T)v_{DS} - v_{DS}^2](1 + \lambda V_{DS})$

Saturation  $I_D = k(v_{GS} - V_T)^2(1 + \lambda V_{DS})$

$\lambda$ : Channel modulation parameter

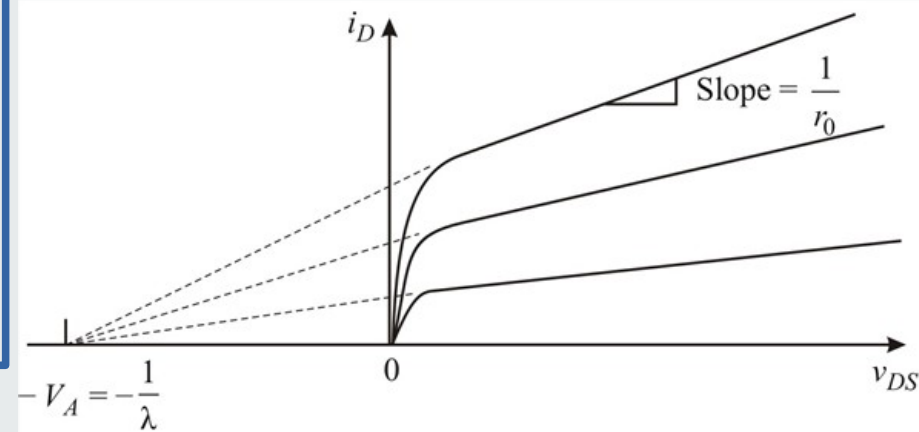


Similar to Early effect in BJTs:  $V_A \leftrightarrow \lambda^{-1}$

Channel effective length shortens with  $V_{DS}$

# MOS transistor small signal model (AC)

Saturation region ONLY

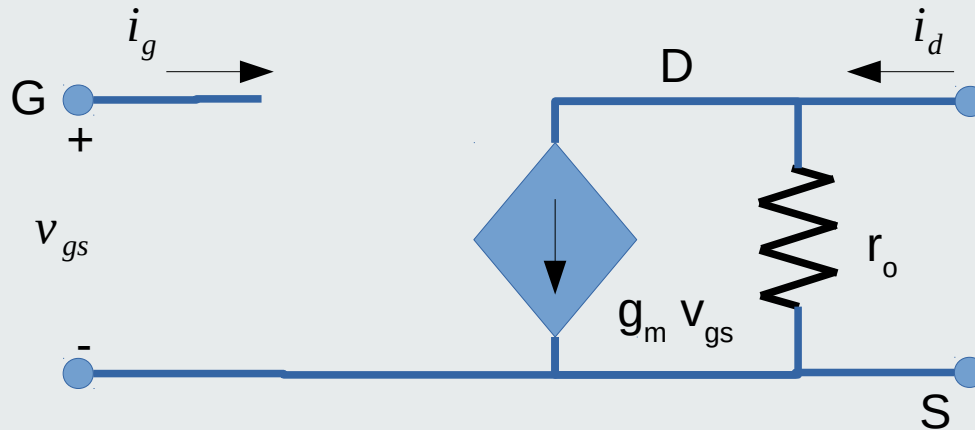

$$g_m = \frac{\partial i_D}{\partial v_{GS}} = \frac{2 I_D}{V_{GS} - V_T}$$

$$r_o = \frac{\partial v_{DS}}{\partial i_D} = \frac{1 + \lambda V_{DS}}{\lambda I_D} \approx \frac{V_A}{I_D}$$

## Incremental parameters

$g_m$  Transconductance  
 $r_o$  Output impedance

Nice feature:  
*Infinite* input impedance!

# Spice's MOS model

- Ngspice has very sophisticated MOS models
- Let's consider a reduced parameter set one
  - Level=1
  - Gamma= 0
  - Xj=0
  - Tox=1200n
  - Phi=.6
  - Rs=0
  - Kp=111u
  - Vto=1.4
  - Lambda=0.01
  - Rd=0
  - Cbd=2.0p
  - Cbs=2.0p
  - Pb=.8
  - Cgso=0.1p
  - Cgdo=0.1p
  - Is=16.64p N=1
- Check out l18.net: simulates  $I_D(v_{DS})$  for constant  $v_{GS}$  using DC analysis (DC sweep) for a real commercial discrete MOS transistor: the CD4007

# BJT versus MOS

Parameter	BJTs	MOS
Gain	High *	Medium
Input impedance	Low	High * (no gate current)
Output impedance	Low *	Medium
Size	Large	Small *
Cost	High	Low *
Power consumption	High	Low*

\* is advantage

The table explains  
why MOS rules!

- Field Effect Transistors
- The Metal Oxide Semiconductor Field Effect Transistor (MOSFET):
  - Operation regions
  - Large signal model (DC)
  - Small signal model (AC)
  - Spice model
  - Comparison with BJT