 


# Circuit Theory and Electronics Fundamentals

## Lecture 17: Presenting the Audio Amplifier Lab Assignment

- Audio amplifier lab assignment presentation
- Bias circuit
- Coupling capacitors
- Bypass capacitor
- Incremental circuit and gain
- Output stage
- Incremental circuit, input and output impedances

# Audio Amplifier Circuit



Based on Lectures 16 and 17, choose the architecture of the Gain and Output amplifier stages. Provided the output has no visible distortion in the output sine waves, the merit  $M$  of your work is given by

$$M = \frac{\text{voltageGain} * \text{bandwidth}}{\text{cost} * \text{lowerCutoffFreq}}$$

cost = cost of resistors + cost of capacitors + cost of transistors

cost of resistors = 1 monetary unit (MU) per kOhm

cost of capacitors = 1 MU/ $\mu\text{F}$

cost of transistors = 0.1 MU per transistor


# Simulation Analysis

- Write an Ngspice script to simulate the audio amplifier. Start with the provided script
- Use the provided transistor models: the gain stage must use the NPN transistor and the output stage must use the PNP transistor
- Measure the output voltage gain in the passband, the lower and upper 3dB cut off frequencies (the difference between them is the bandwidth), the input and output impedances
- Perform incremental modifications to improve the merit figure
  - Make sure the BJTs operate in the F.A.R. ( $V_{CE} > V_{BE}$ ) by means of a suitable O.P. (For the PNP,  $V_{EC} > V_{EB}$ )
  - Understand the purpose of the coupling capacitors and their effect on the bandwidth
  - Understand the purpose of the bypass capacitor and its effect on the gain
  - Understand the effect of resistor  $R_C$  on the gain

# Theoretical Analysis

- 1) Compute the OP using the theoretical DC model studied. Compare it to Ngspice's OP and explain.
- 2) Compute the gain, input and output impedances separately for the 2 stages, and explain why they can be connected without significant signal loss.
- 3) Compute the frequency response  $V_o(f)/V_i(f)$ , using the incremental circuit, solving the circuit for a frequency vector in log scale with 10 points per decade, from 10Hz to 100MHz.
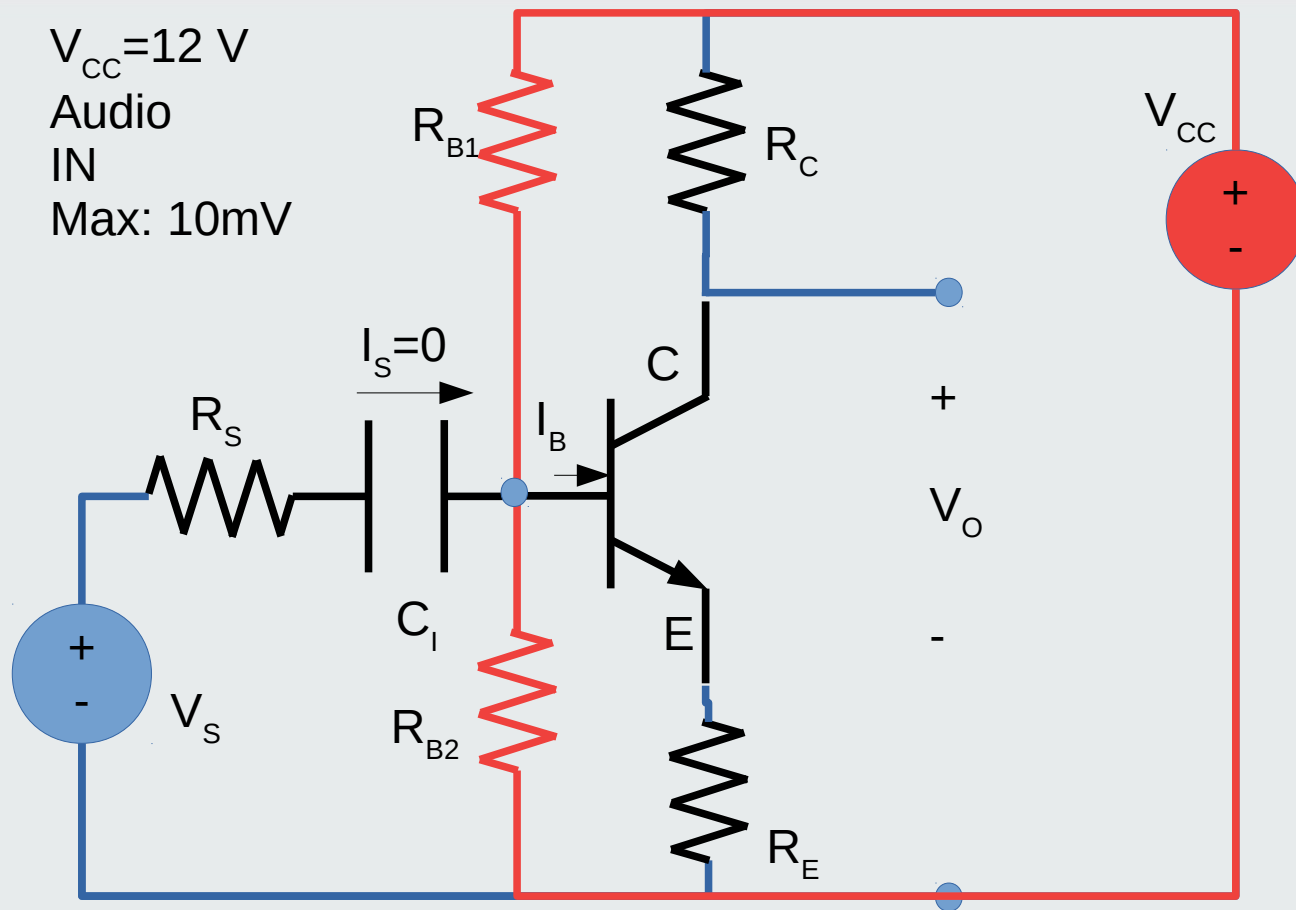
# Gain stage: degenerated common emitter amp; OP(1)



Can't connect source to base directly:

Source has 0V DC value and base needs a different DC value

Source can't bias the BEJ forwardly


We need a coupling capacitor and a bias circuit

$C_i$  blocks the 0V DC component of  $V_s$  (open-circuit at low freq.)

The **bias circuit**  $V_{CC}, R_{B1}, R_{B2}$  will determine the base voltage  $V_B$  and ensure the BEJ is ON!
 
# Gain stage: degenerated common emitter amp; OP(2)

Thévenin's equivalent of bias circuit makes it easier to analyse



OP complete: all static voltages and currents computed!

$$R_{B1} = 80 \text{ k}\Omega$$

$$R_{B2} = 20 \text{ k}\Omega$$

$$R_B = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 16 \text{ k}\Omega$$

$$-V_{eq} = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} = 2.4 \text{ V}$$

$$V_{eq} + R_B I_B + V_{BEON} + R_E I_E = 0$$

$$V_{BEON} \approx 0.7 \text{ V}, \beta_F = 178.7$$

$$I_E = (1 + \beta_F) I_B$$

$$I_B = \frac{V_{eq} - V_{ON}}{R_B + (1 + \beta_F) R_E} = 50.04 \mu\text{A}$$

$$I_C = \beta_F I_B = 8.24 \text{ mA}$$


$$I_E = 8.99 \text{ mA}$$

$$V_O = V_{CC} - R_C I_C = 3.06 \text{ V}$$

$$V_E = R_E I_E = 0.90 \text{ V}$$

$$\text{Confirms FAR: } V_{CE} = V_O - V_E = 2.16 \text{ V} > V_{BEON}$$
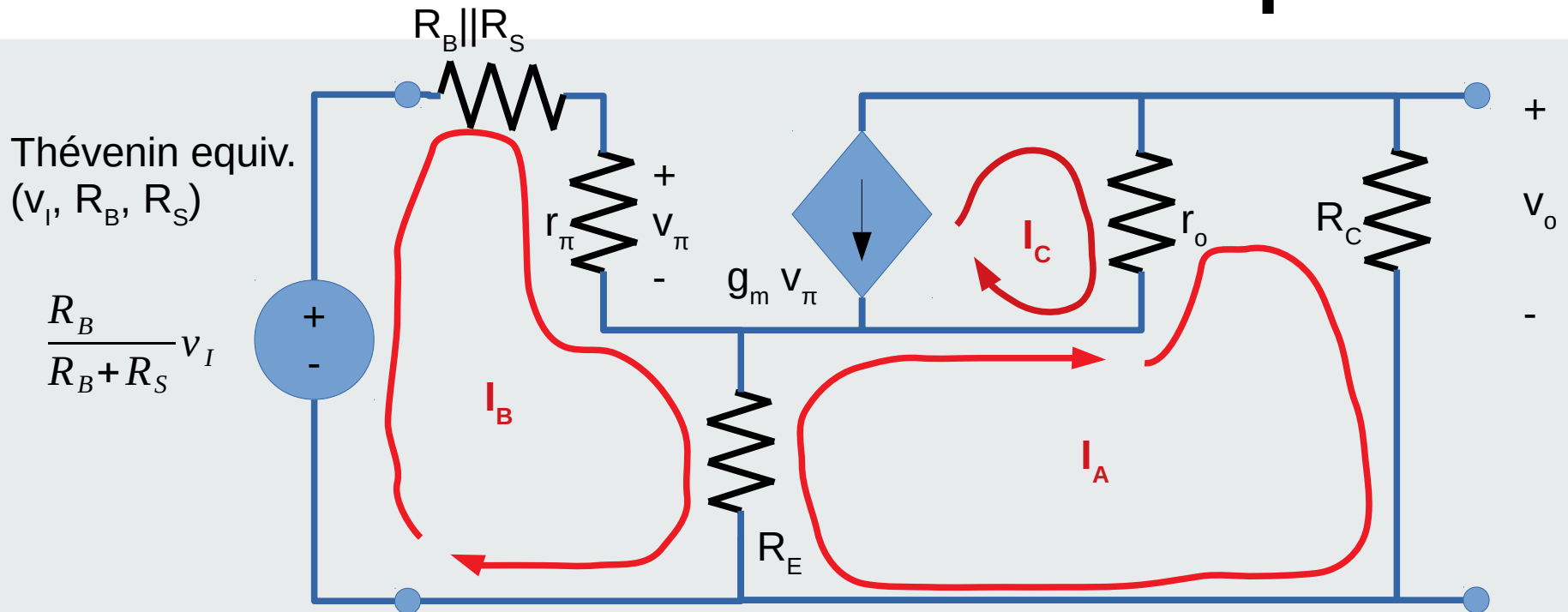
# Gain stage: incremental circuit for medium frequencies



From BC547A model

$$V_A = 69.7 \text{ V}$$

$$\beta_F = 178.7$$


Incremental parameters:

$$g_m = \frac{I_C}{V_T} = 358 \text{ mS}$$

$$r_\pi = \frac{\beta_F}{g_m} = 500.0 \Omega$$

$$r_o \approx \frac{V_A}{I_C} = 7.79 \text{ k}\Omega$$

# Gain stage: incremental circuit gain

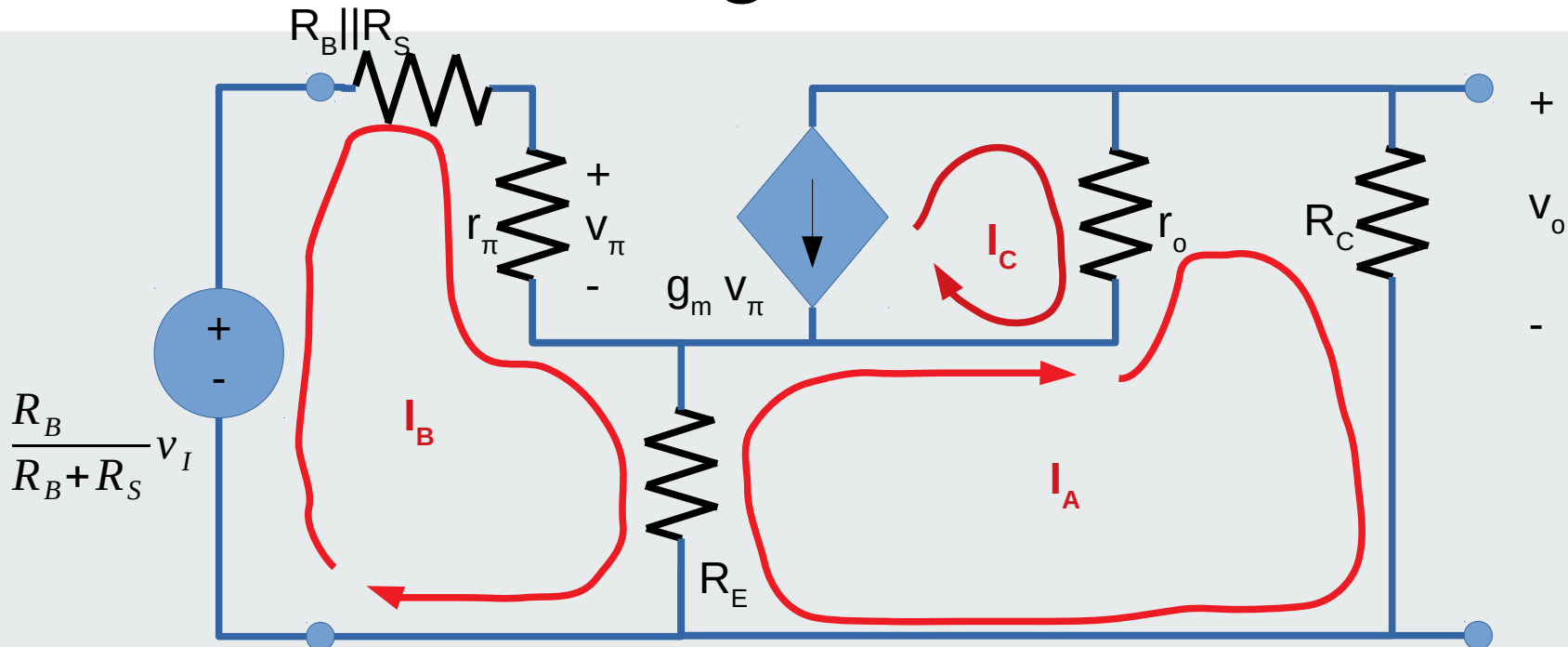


From previous lecture


$$\frac{v_o}{v_i} = \frac{R_B}{R_S + R_B} R_C \frac{R_E - g_m r_\pi r_o}{(r_o + R_C + R_E)(R_B || R_S + r_\pi + R_E) + g_m R_E r_o r_\pi - R_E^2} = -9.51$$


 
# Gain stage: effect of the input coupling capacity




 Input capacitance too low!  
Lower cutoff frequency too high!




Input capacitance good enough!  
Lower cutoff frequency close to 20Hz.

# Gain stage: bypass capacitor

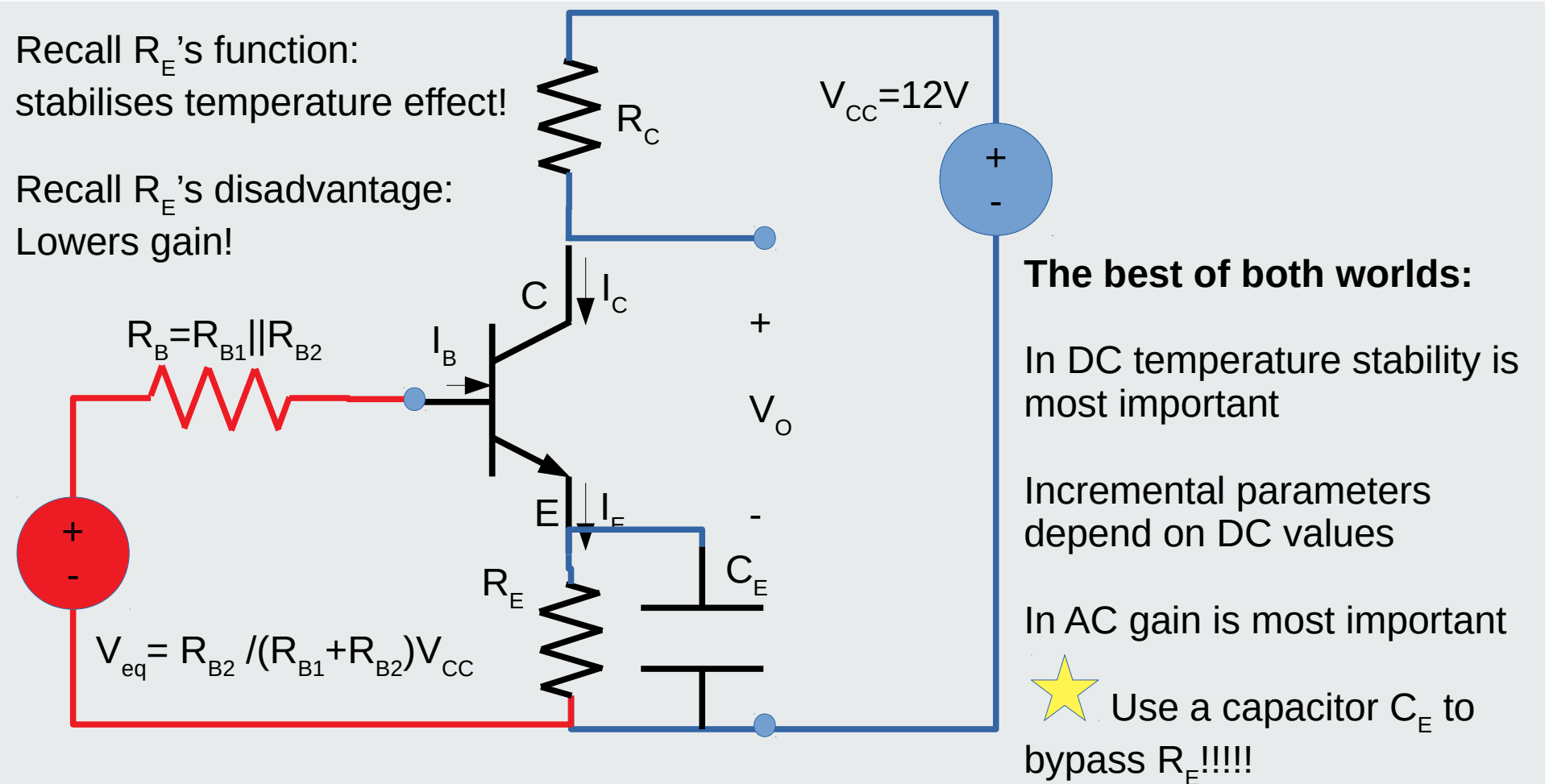


$C_E$  is an open-circuit for low frequency (DC) and a short-circuit for higher frequencies (AC)
 
# Gain stage: effect of the bypass capacitor




 Bypass capacitance too low!  
Gain is low in part of the bandwidth!



Bypass capacitance good enough!  
Gain is stable in desired passband.
 
# Gain stage: incremental circuit gain with bypass C



With  $R_E = 0$ :

$$\frac{v_o}{v_i} = -g_m (R_C \parallel r_o) v_{\pi}$$

$$v_{\pi} = \frac{r_{\pi} \parallel R_{B1} \parallel R_{B2}}{R_S + r_{\pi} \parallel R_{B1} \parallel R_{B2}} v_S$$

$$\frac{v_o}{v_i} = -g_m (R_C \parallel r_o) \frac{r_{\pi} \parallel R_{B1} \parallel R_{B2}}{R_S + r_{\pi} \parallel R_{B1} \parallel R_{B2}} v_S$$

# Gain stage: input and output impedances

$$Z_I = R_{B1} \parallel R_{B2} \parallel r_{\pi} = 484.43 \, \Omega$$

Not very compatible with  $R_S = 100 \, \Omega$


$$Z_O = R_C \parallel r_o = 886.28 \, \Omega$$

Certainly cannot be connected to an  $8 \, \Omega$  load!!

An output stage is in demand!!

# Output stage: common collector amplifier OP

PNP transistor!

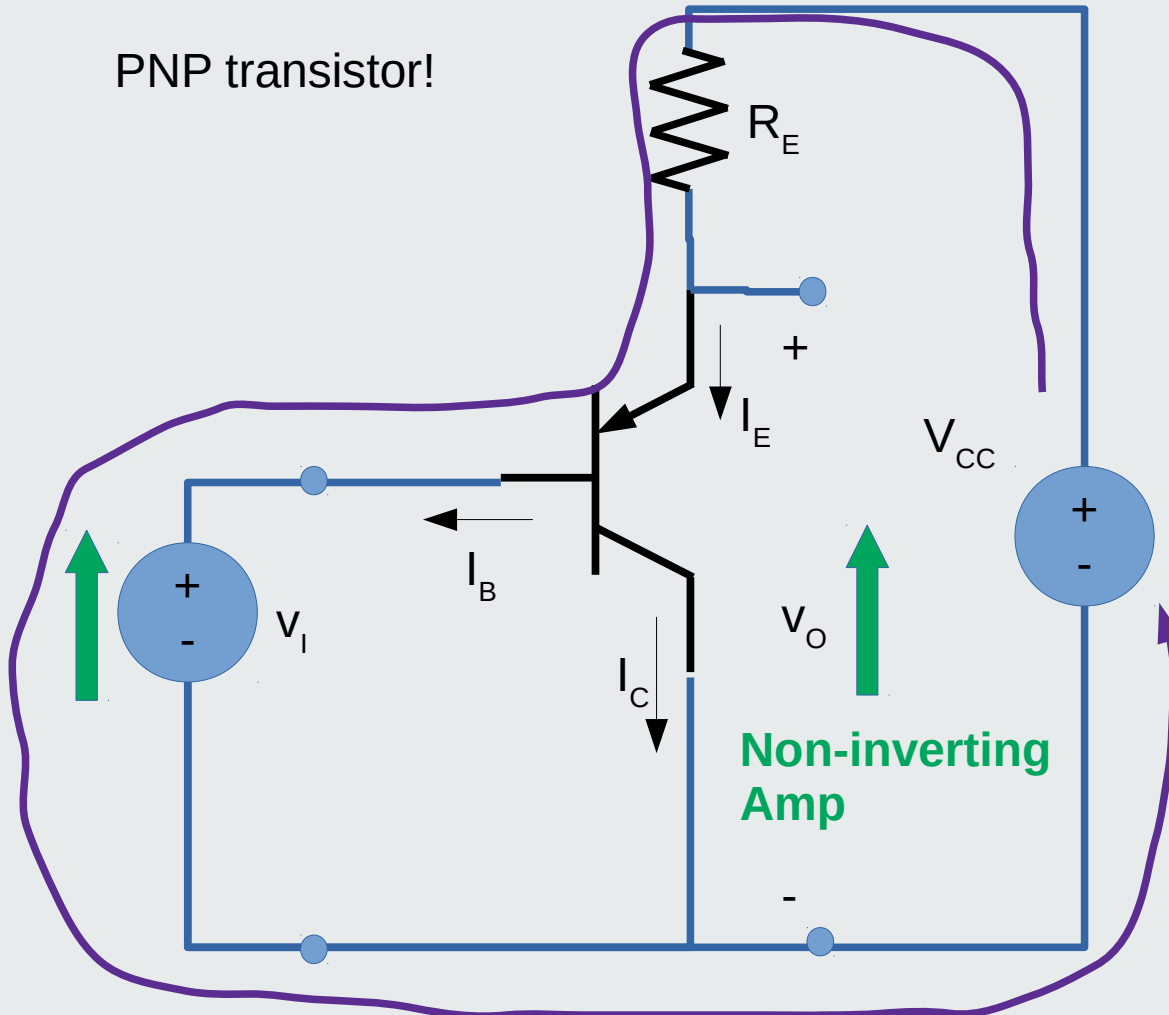

$$V_{CC} = 12\text{ V}$$

$$V_{EBON} \approx 0.7\text{ V}$$

$$R_E = 100\Omega$$

$$R_E I_E + V_{EBON} + V_I - V_{CC} = 0$$

$$I_E = \frac{V_{CC} - V_{EBON} - V_I}{R_E} = 82.24\text{ mA}$$


$$V_O = V_{CC} - R_E I_E = 3.76\text{ V}$$

$$V_O = V_I + V_{EBON}$$

Output current  $I_E$  much stronger than in Gain Stage!

Part of this current will feed the Load!
 
# The common collector amplifier: voltage gain



Convenient  
to work with  
admittances

$$g_{\pi} = \frac{1}{r_{\pi}}$$

$$g_E = \frac{1}{R_E}$$

$$g_o = \frac{1}{r_o}$$

KCL:  $\left(\frac{1}{R_E} + \frac{1}{r_o}\right)v_o + \frac{v_o - v_i}{r_{\pi}} - g_m v_{\pi} = 0$

$v_{\pi} = v_i - v_o$



$$\frac{v_o}{v_i} = \frac{g_m}{g_{\pi} + g_E + g_o + g_m} = 0.99$$

From BC557A model

$V_A = 37.2 \text{ V}$   
 $\beta_F = 227.3$

Almost unitary gain as predicted!

# Output stage: input and output impedances

From previous lecture:

$$Z_I = \frac{g_\pi + g_E + g_o + g_m}{g_\pi(g_\pi + g_E + g_o)} = 8.6 \text{ k}\Omega$$

Quite compatible with gain stage  $Z_o = 886.28 \Omega$

$$Z_o = \frac{1}{g_\pi + g_E + g_o + g_m} = 0.3 \Omega$$

Amazingly low output impedance!

Very good to connect to an  $8\Omega$  load!

The output stage is doing its job!!

Another coupling capacitor between the Output stage and the load is also needed.



# Lab report

- 1) Produce all tables and plots required in the simulation and analysis sections
- 2) Compare Octave and Ngspice results side by side looking for accuracy or discrepancy, and explaining both. Read the repository's README file.
- 3) The results of interest are, obviously,
  - the gain's frequency response
  - input /output impedances to support the driver (input audio source) and load (speaker), respectively, adequately
  - the cost of the components used

# Evaluation criteria

- 1) The instructor should *git pull* your repo, and run *make flawlessly*
- 2) The report should not have obvious mistakes in figures, tables, formulae, section titles or main sentences
- 3) 1 bonus point (mark can be 5 offsetting previous grade losses) for the 5% best merit figures
  - if your work is in the top 5%, expect a more thorough review