

Circuit Theory and Electronics Fundamentals

Lecture 22: Operational Amplifiers

- What are operational amplifiers (OP-AMPs)
- Design once reuse many times
- The famous μ A741 OP-AMP design
- OP-AMP operation with and without feedback
- Inverting amplifier
- Non-inverting amplifier
- Amplifiers with resistive and complex feedback loops

What is an Operational Amplifier

- An OPerational AMPlifier (OP-AMP) is transistor-based amplifier used often as a subcomponent in analogue designs
- OP-AMP main features
 - High gain
 - High input impedance
 - Low output impedance
 - Differential input
- OP-AMP main limitations
 - Frequency response
 - Complexity (due to its generality)
 - Power consumption (due to its generality)

OP-AMP: package and reuse

- A considerable effort goes into designing good analogue circuits:
 - Extensive hand calculations needed
 - Extensive simulations needed
 - Silicon prototyping and validation needed
- It may take years before the circuit is stable
- Unfortunately, if the underlying semiconductor technology changes or evolves, the circuit needs to be redesigned...
- Nevertheless, it is important to have building blocks such as the OP-AMP to speed up development


OP-AMP: symbol and pins

Differential input!
Only the difference
 $v_+ - v_-$ matters


So v_+ and v_- may
have any common
DC offset!

No coupling capacitors needed, as in single-ended designs!

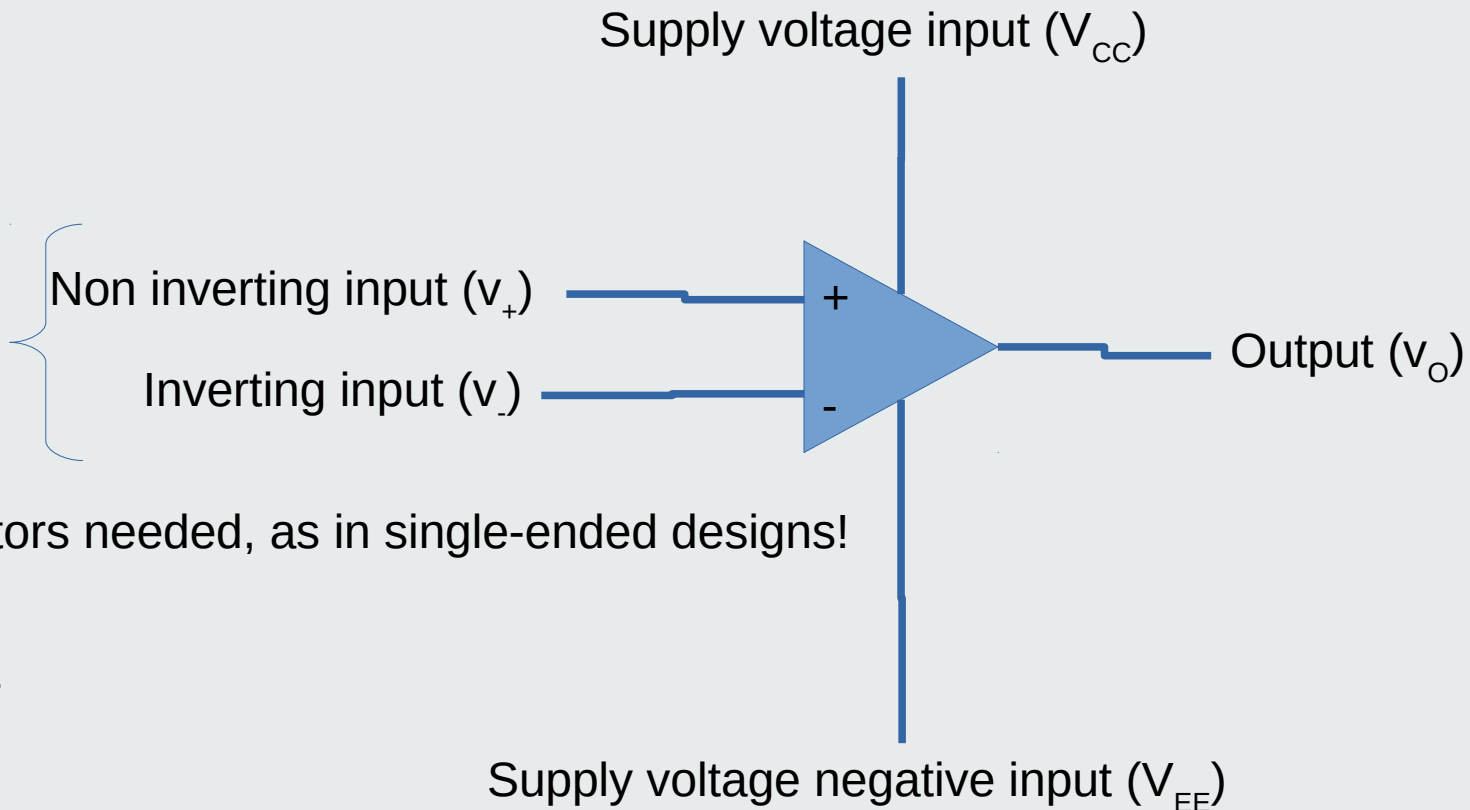Examples: signal
from microphone or
antenna



The famous μ A741 OP-AMP

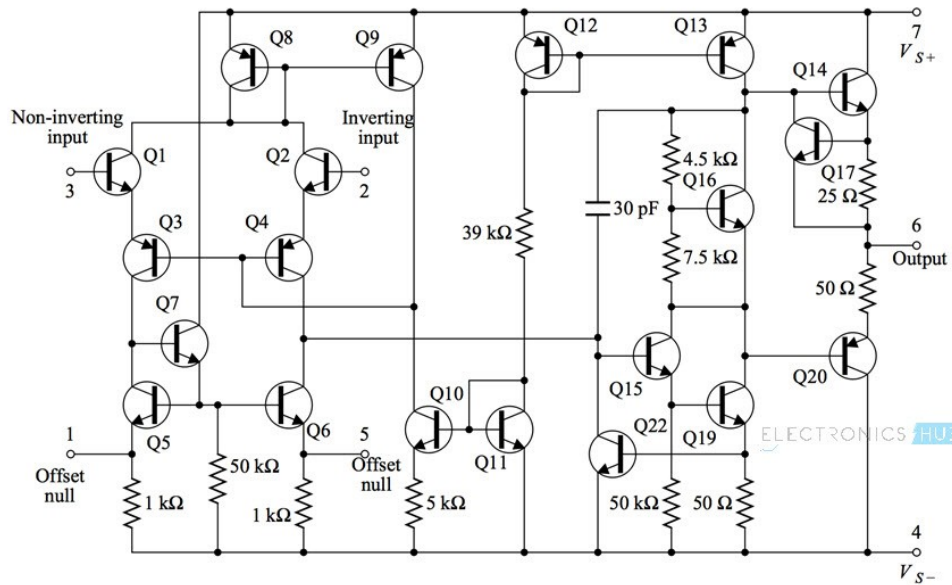

Internal Circuitry of 741 Op-Amp IC

- In 1963 Robert Widlar's μ A702 design for Fairchild Semiconductor at age 26
- Widlar later designed an improved version, the LM101
- Widlar also has a current source design named after him
- David Fullagar (also Fairchild's) improved the LM101 design, called it μ A741, and took it to the head of R&D – Gordon Moore (the legend)


The 20-transistor μ A741 circuit became the OP-AMP world standard!

Original price in 1963: US\$300
Price now: 60 cents!



electronicsarea.com


OP-AMP: model

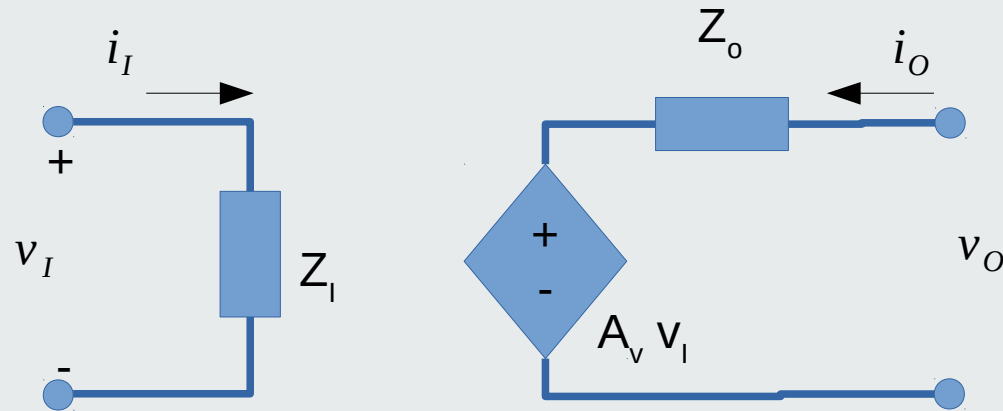


Differential input amplifier model

Ideally, $A_v = \infty$, $Z_I = \infty$, $Z_o = 0$

OP-AMP: operation

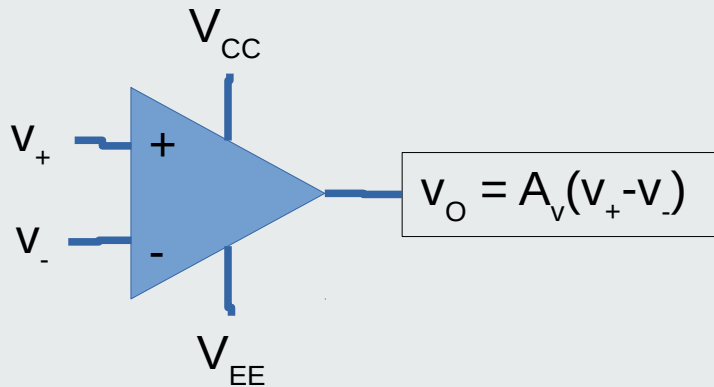

OP-AMP used as a comparator

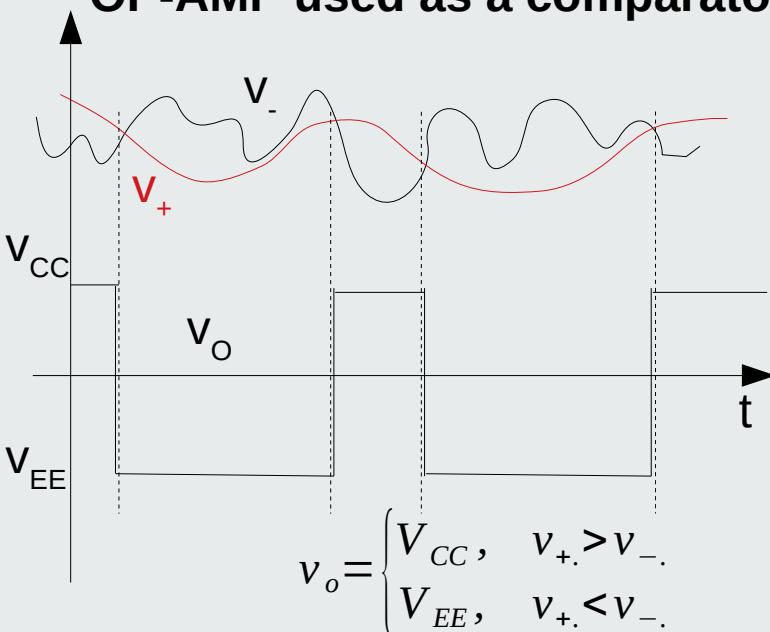


Feature	Ideal	Practical (typical)
Gain	∞	$10^4 - 10^6$
Input impedance	$\infty \Omega$	1-10 M Ω
Output impedance	0 Ω	10 – 100 Ω
Bandwidth	∞ Hz	10 Hz
Power efficiency	100%	50%
Slew rate*	∞ V/s	0.5 V/ μ s
Output limits	$[V_{EE}, V_{CC}]$	$[V_{EE} + \delta_e, V_{CC} - \delta_c]$

*max output voltage variation rate

OP-AMP: feedback operation

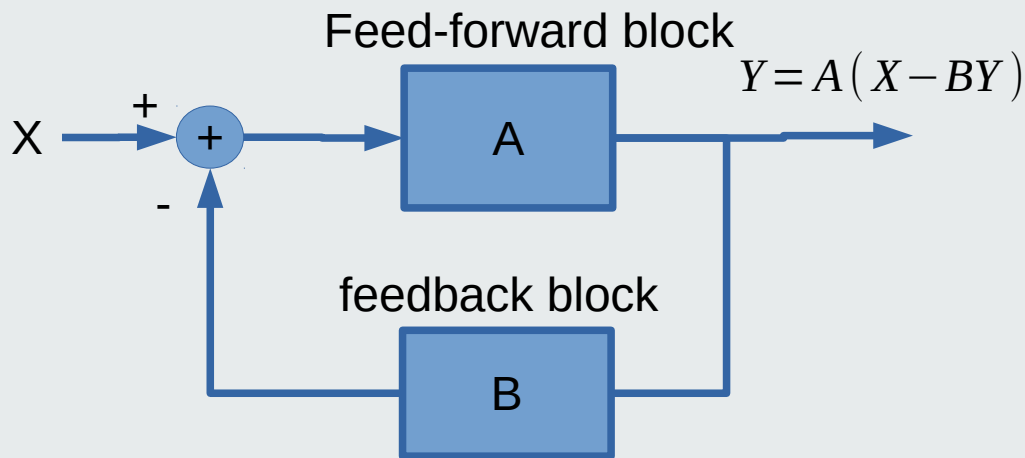- Question: What can a device with very high gain used for, besides the comparator circuit
- Answer: for many different uses provided a technique called **feedback** is used




$$Y = \frac{A}{1 + AB} X$$

The feedback equation!

$$A \rightarrow \infty \Rightarrow Y \approx \frac{1}{B} X$$

- Gain depends on feedback block only!
- Normally B is made with passive components (less sensitive to temperature, humidity, fabrication variations than active components)
- High gain still possible as we take the inverse of B!

OP-AMP: inverting amplifier

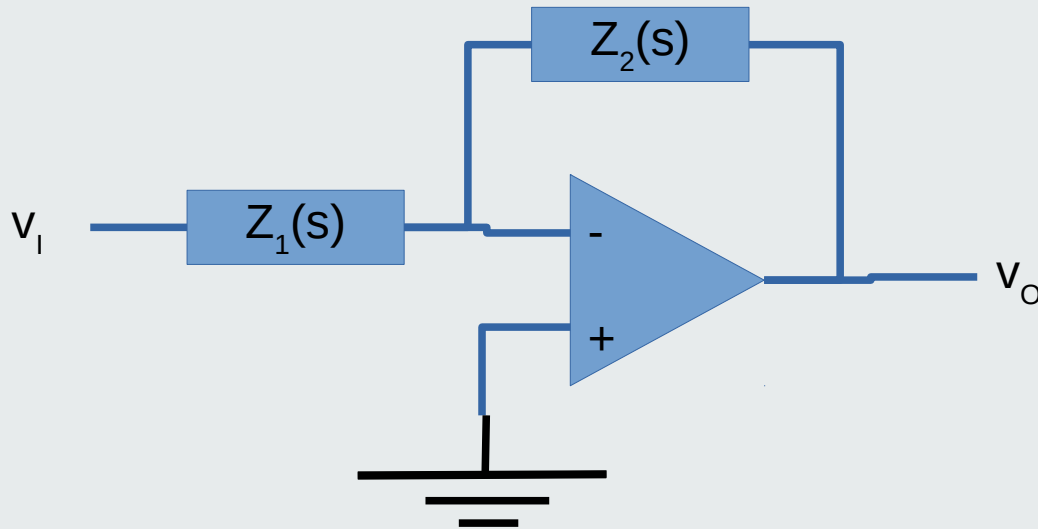

Negative feedback using inverting input:

$$v_O = A_v (v_+ - v_-)$$

$$v_O = A_v \left(0 - \frac{Z_2}{Z_1 + Z_2} v_I - \frac{Z_1}{Z_1 + Z_2} v_O \right)$$

$$v_O = -\frac{Z_2}{Z_1 + Z_2} \frac{A_v}{1 + A_v \frac{Z_1}{Z_1 + Z_2}} v_I$$

$$v_+ = 0$$

Connected to ground


$$v_- = \frac{Z_2}{Z_1 + Z_2} v_I + \frac{Z_1}{Z_1 + Z_2} v_O \quad \text{superposition}$$

$$\frac{Y}{X} = \frac{A}{1 + AB}$$

$$B = \frac{Z_1}{Z_1 + Z_2} \quad \text{Feedback gain}$$

$$A_v \rightarrow \infty \Rightarrow \frac{v_O}{v_I} = -\frac{Z_2(s)}{Z_1(s)}$$

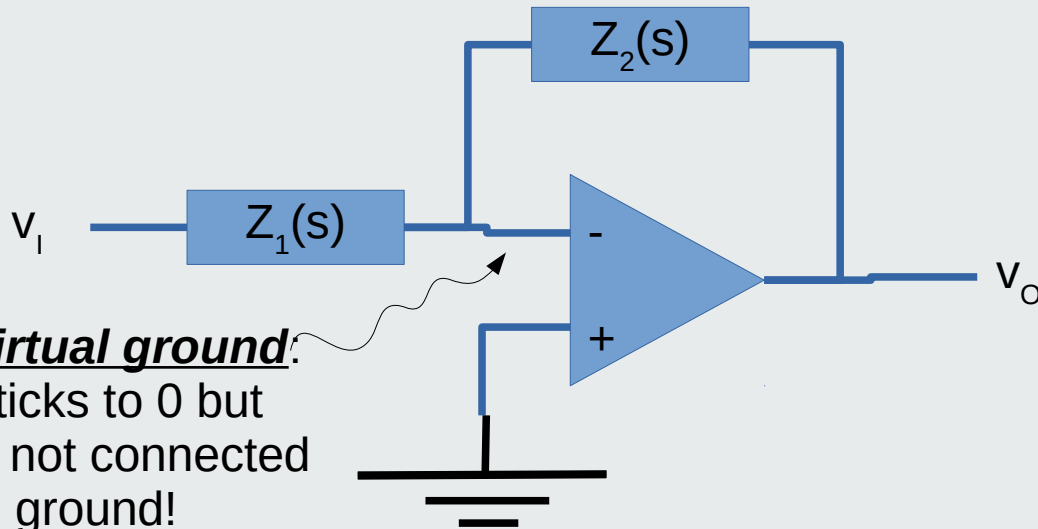OPAMP: inverting amplifier – the effect of negative feedback



$$v_{+} = 0$$

$$v_{-} = \frac{Z_2}{Z_1 + Z_2} v_I + \frac{Z_1}{Z_1 + Z_2} v_O$$


$$\frac{Y}{X} = \frac{A}{1 + AB}$$

$v_I \uparrow \Rightarrow v_{-} \uparrow \Rightarrow v_O \downarrow \Rightarrow v_{-} \downarrow$ If v_I raises v_{-} won't raise!
 $v_I \downarrow \Rightarrow v_{-} \downarrow \Rightarrow v_O \uparrow \Rightarrow v_{-} \uparrow$ If v_I lowers v_{-} won't lower!

$v_O = A_v (v_{+} - v_{-})$ If A_v is infinite the only way v_O can be finite is if $v_{+} - v_{-} = 0$
 $\infty \times 0 = \text{something}$

$v_{-} = v_{+}$ **v_{-} sticks to v_{+} with negative feedback!!!**

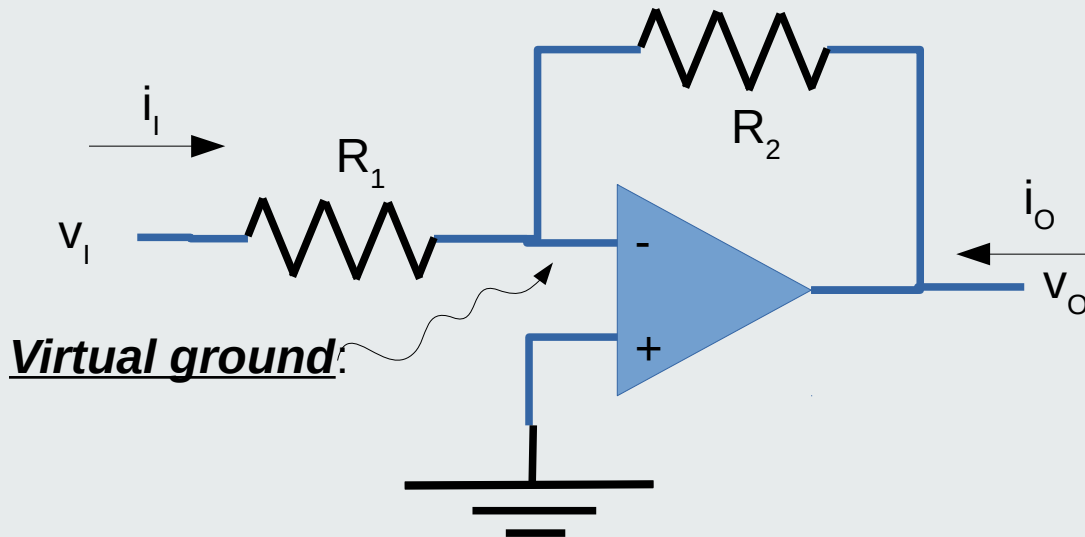OPAMP: inverting amplifier with resistive feedback loop



$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} \quad \text{Gain}$$


$$Z_I = \frac{v_I}{i_I} \Big|_{Z_L = \infty} = \frac{v_i - 0}{\frac{v_i - 0}{R_1}} = R_1$$

$$Z_O = \frac{v_O}{i_O} \Big|_{v_I = 0} = R_2 \parallel 0 = 0$$

Very stable **negative** gain amplifier

R_1 and R_2 also vary with the temperature but if they vary proportionally the gain is kept

OPAMP: non-inverting amplifier

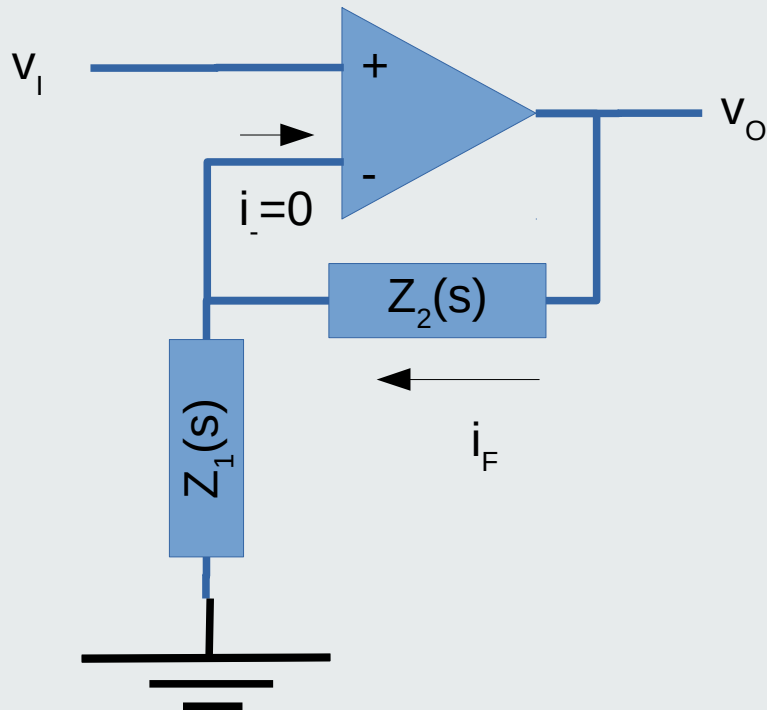

$$\begin{aligned} v_I \uparrow &\Rightarrow v_+ \uparrow \Rightarrow v_O \uparrow \Rightarrow v_- \uparrow \Rightarrow v_O \downarrow \Rightarrow v_- \downarrow \\ v_I \downarrow &\Rightarrow v_+ \downarrow \Rightarrow v_O \downarrow \Rightarrow v_- \downarrow \Rightarrow v_O \uparrow \Rightarrow v_- \uparrow \end{aligned}$$

$$v_O = A_v (v_+ - v_-)$$

$$v_- = v_+ = v_I$$

$$v_O = v_- + Z_2 i_F = v_I + Z_2 i_F$$


$$i_F = \frac{v_-}{Z_1}$$

$$\frac{v_O}{v_I} = 1 + \frac{Z_2(s)}{Z_1(s)}$$

Another Negative Feedback Amplifier: feedback through inverting input

Gain is positive if Z_2 and Z_1 are positive

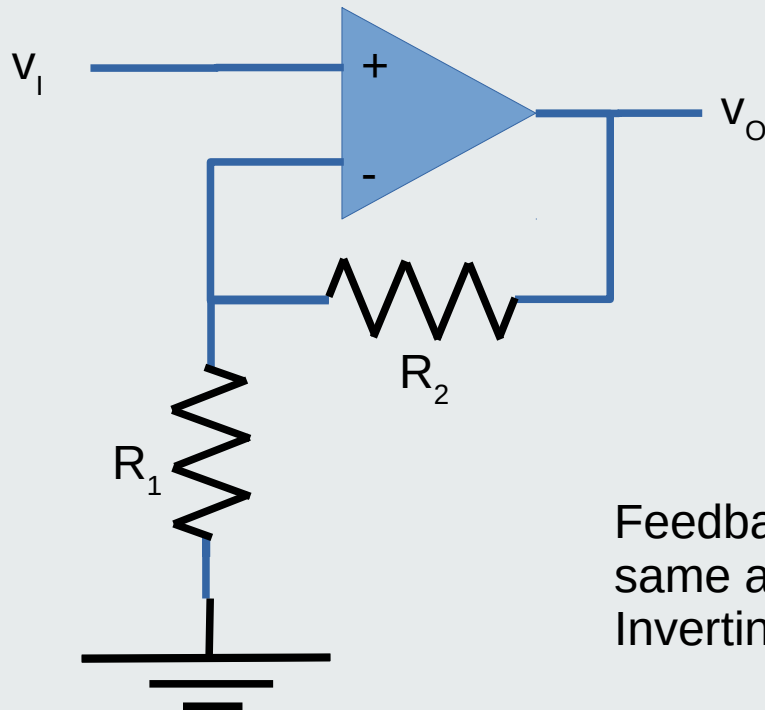OPAMP: non-inverting amplifier with resistive feedback loop



Feedback gain B is the same as the Inverting amplifier:

$$\frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$

$$v_O = A_v \left(v_I - \frac{R_1}{R_1 + R_2} v_O \right)$$

$$\frac{v_O}{v_I} = \frac{A_v}{1 + A_v \frac{R_1}{R_1 + R_2}}$$


$$B = \frac{R_1}{R_1 + R_2}$$

Very stable **positive** gain amplifier

R_1 and R_2 also vary with the temperature but proportionally so the gain keeps

OPAMP: non-inverting amplifier

– gain, input and output impedance

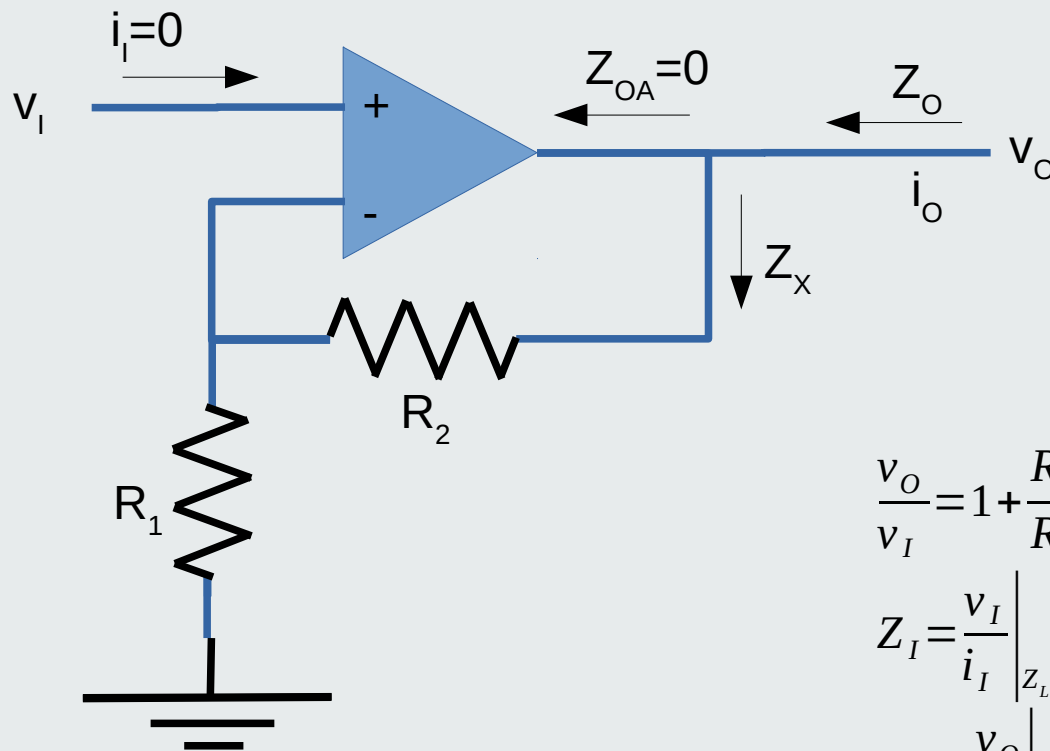


$$\frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$

$$Z_I = \left. \frac{v_I}{i_I} \right|_{Z_L = \infty} = \frac{v_i - v_-}{0} = \infty$$

$$Z_O = \left. \frac{v_O}{i_O} \right|_{v_I = 0} = Z_X \parallel Z_{OA} = R_2 \parallel 0 = 0$$

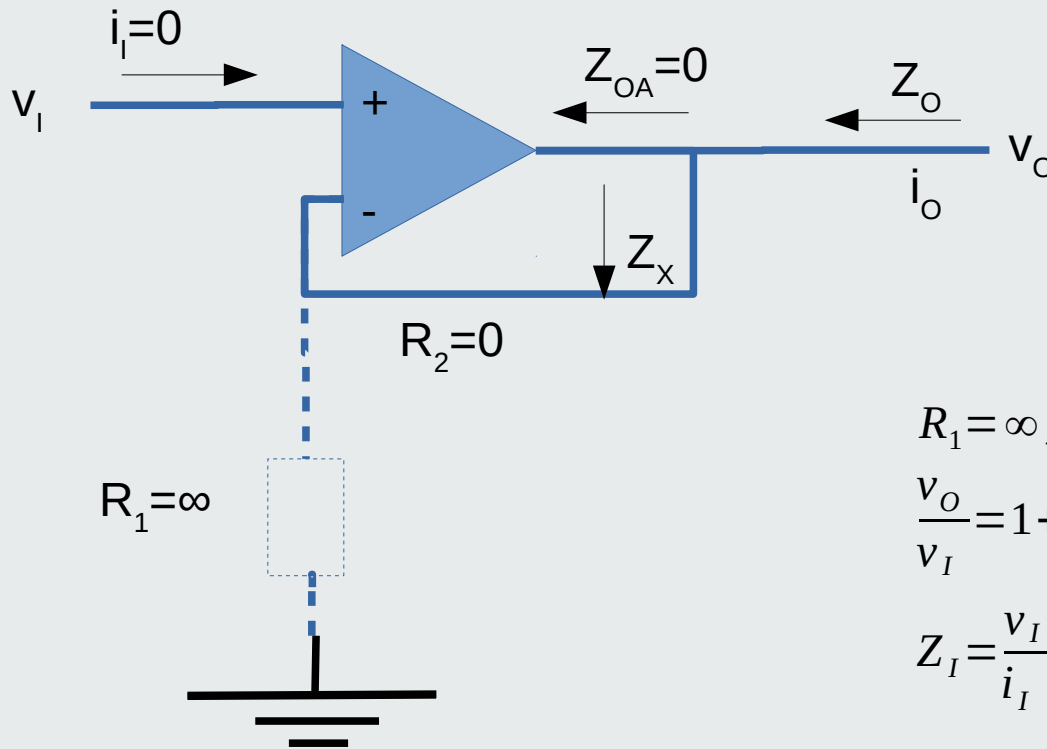OPAMP: non-inverting amplifier as current buffer




$$R_1 = \infty, R_2 = 0$$

$$\frac{v_O}{v_I} = 1 + \frac{R_2}{R_1} = 1$$

$$Z_I = \frac{v_I}{i_I} \bigg|_{Z_L = \infty} = \frac{v_i - v_-}{0} = \infty$$

$$Z_O = \frac{v_O}{i_O} \bigg|_{v_I = 0} = Z_X || Z_{OA} = R_2 || 0 = 0$$

OPAMP: amplifiers complex feedback loop

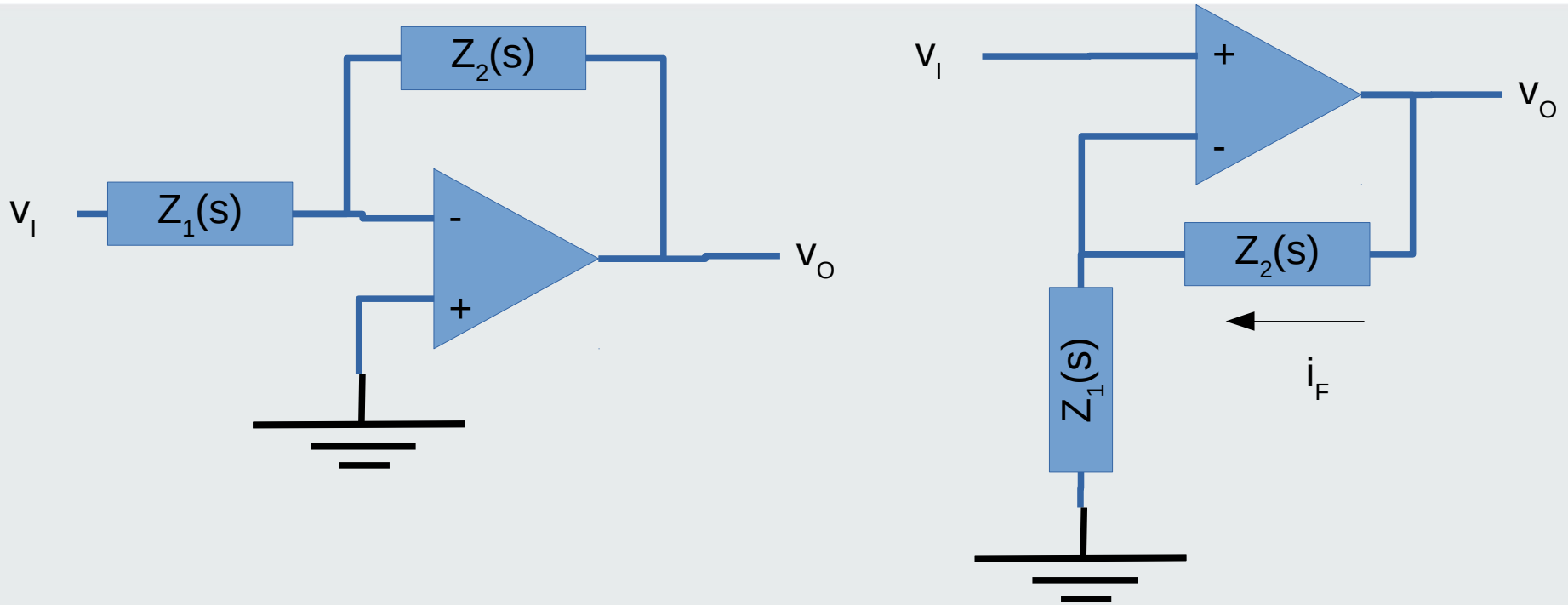

If $Z_1(s)$ and $Z_2(s)$ are complex impedances then interesting **filters** and other operations can be realized

This is what we will in next classes and is done in lab assignment number 5...

Conclusion

- What are operational amplifiers (OP-AMPs)
- Design once reuse many times
- The famous μ A741 OP-AMP design
- OP-AMP operation with and without feedback
- Inverting amplifier
- Non-inverting amplifier
- Amplifiers with resistive and complex feedback loops