

Circuit Theory and Electronics Fundamentals

Lecture 12: Non-Linear Components: piecewise linear and incremental models




- Ideal diode model
- Voltage source diode model
- Voltage source plus resistor diode model
- Piecewise linear diode model
- Incremental analysis
- Incremental diode model
- Exercise

Diode I-V Plots

$$i = I_S \left(e^{\frac{v}{\eta V_T}} - 1 \right)$$

$$I_S = 1 \text{ nA}$$

$$\eta = 2 \quad (\text{Silicon})$$

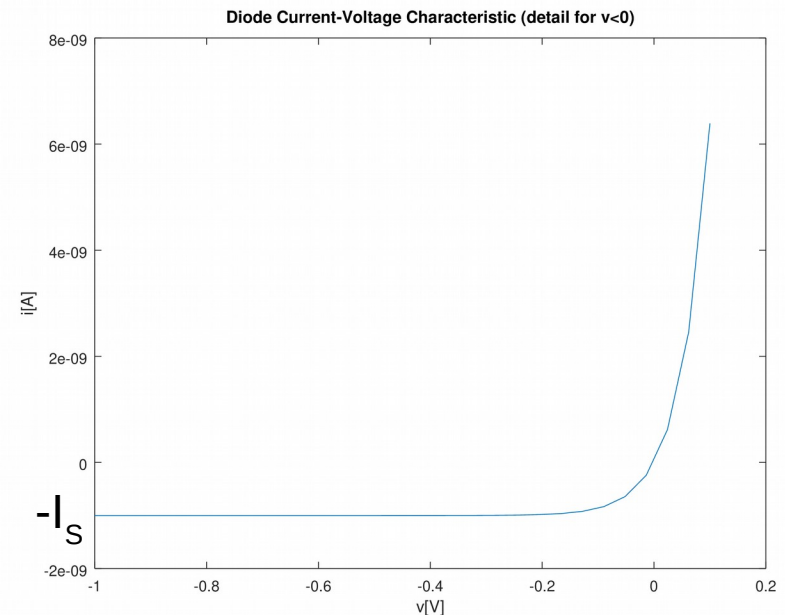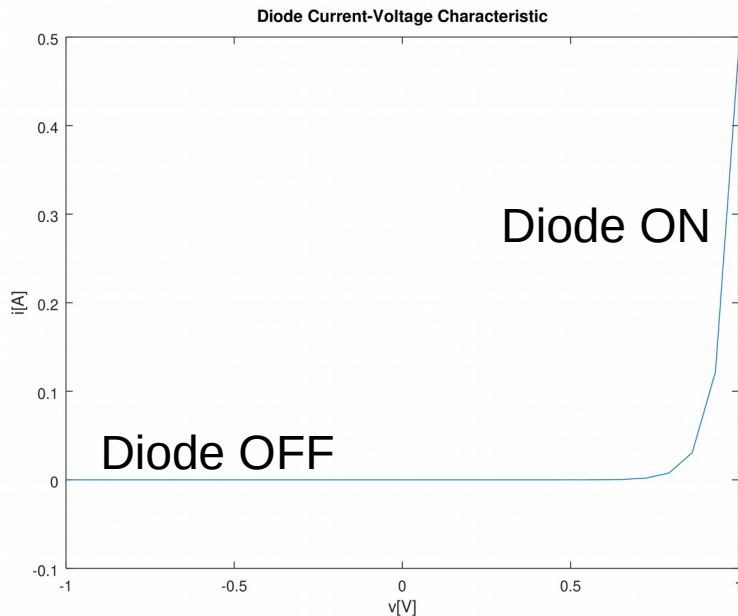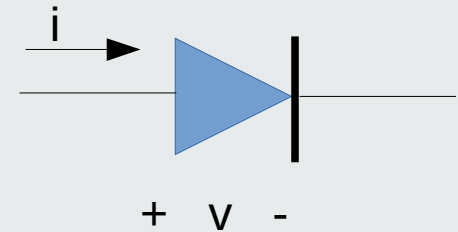

Example diode circuit

$$v + Ri - v_s = 0 \quad \text{KVL}$$

$$v + R I_S \left(e^{\frac{v}{\eta V_T}} - 1 \right) - v_s = 0$$

**Non-Linear
Equation!**

$$f(v) = v + R I_S \left(e^{\frac{v}{\eta V_T}} - 1 \right) - v_s \quad \text{Define error function}$$

$$f(v) = 0$$


Solve non-linear equation for v

$$x_{n+1} = x_n - \frac{f(x_n)}{f'(x_n)}$$

Use **Newton Raphson's** iterative method

$$|x_{n+1} - x_n| < \delta$$

Stop condition: δ is the desired error

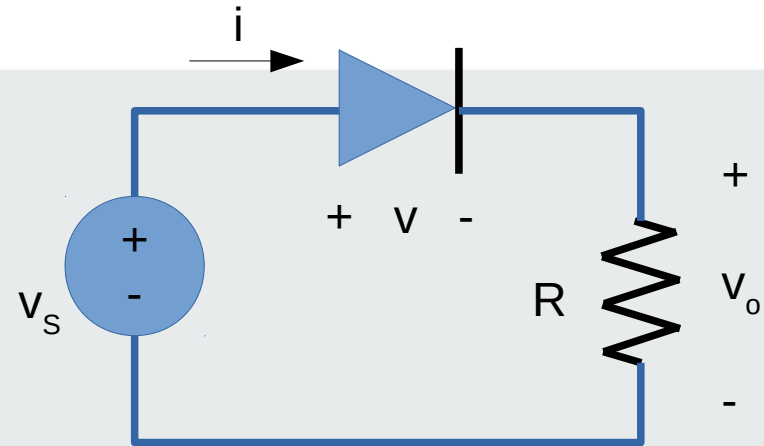

Example diode circuit solution

$$v_s(t) = 2 \cos(2\pi f t)$$

$$I_S = 1 \text{ nA}$$

$$R = 1 \text{ k}\Omega$$



$$f = 1 \text{ kHz}$$

$$v_o = v_s - v; v_o = 0$$

$$i = \frac{v_o}{R}; i = 0 \quad (\text{ON; OFF})$$

Octave script l11.m solves 1 non-linear equation for v , for each time instant t




HALF WAVE RECTIFIER CIRCUIT

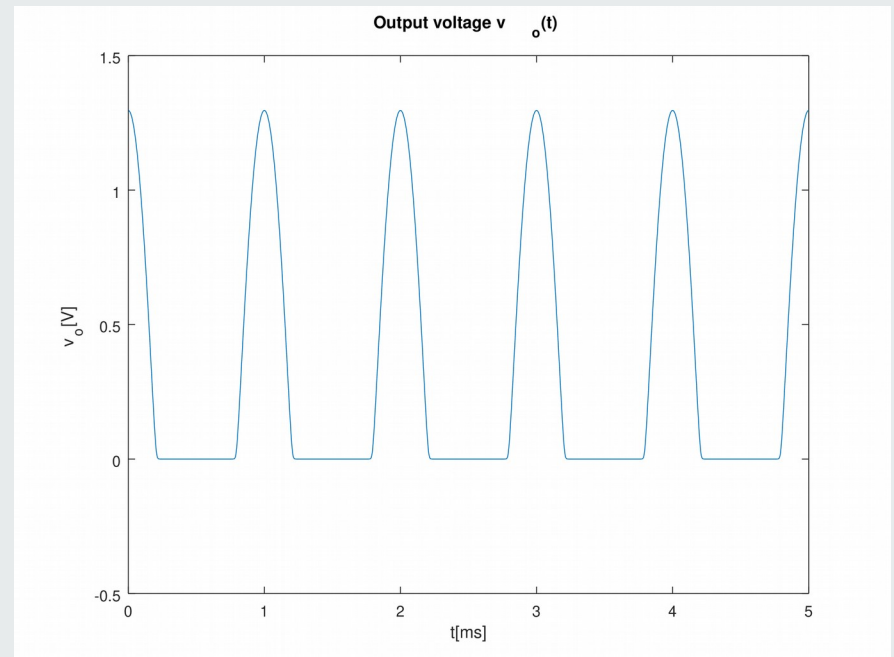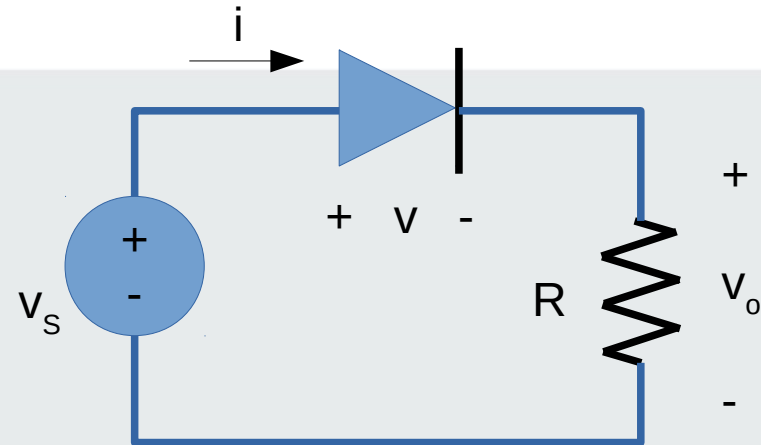

Ideal diode model

$$\begin{cases} i = 0, & v < 0 \\ v = 0, & i \geq 0 \end{cases}$$


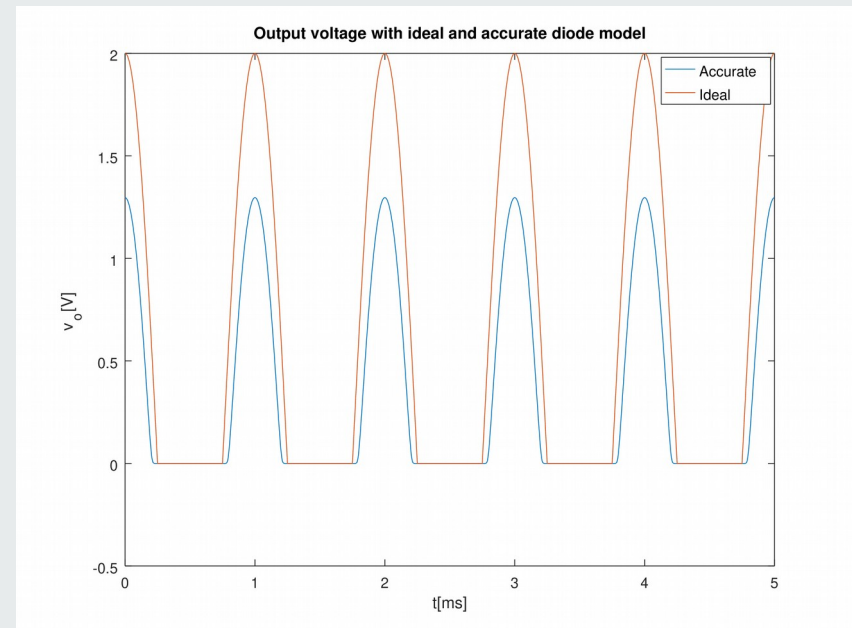
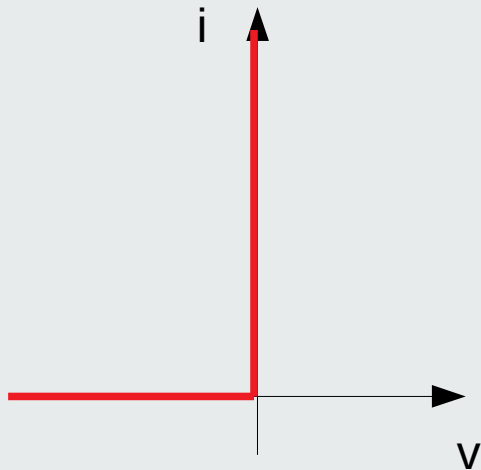
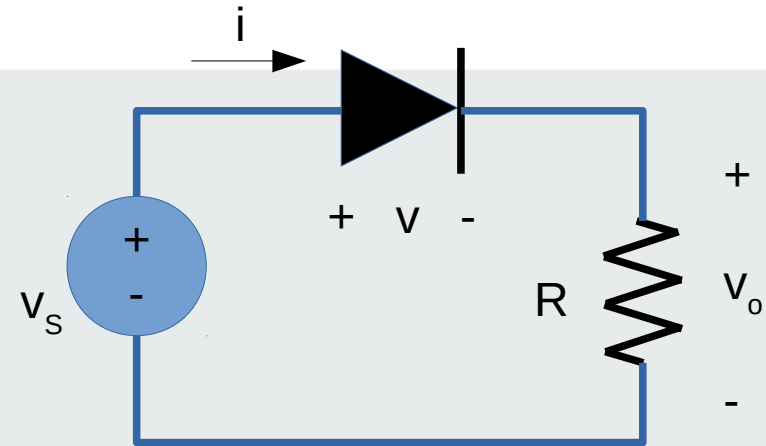
$$\begin{cases} v_o = 0, & v_s < 0 \\ v_o = v_s, & v_s \geq 0 \end{cases}$$



Diode model with ideal diode+ voltage source




$$\begin{cases} i=0, & v < V_{ON} \\ v = V_{ON}, & i \geq 0 \end{cases}$$
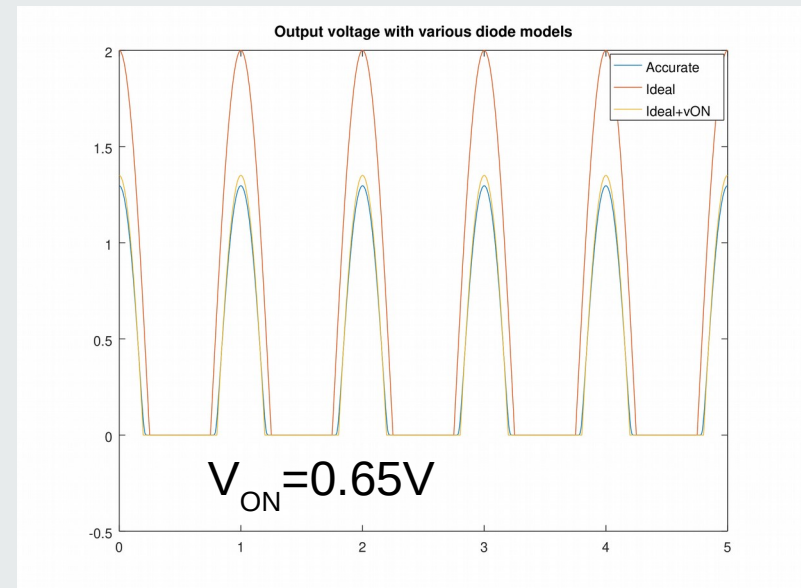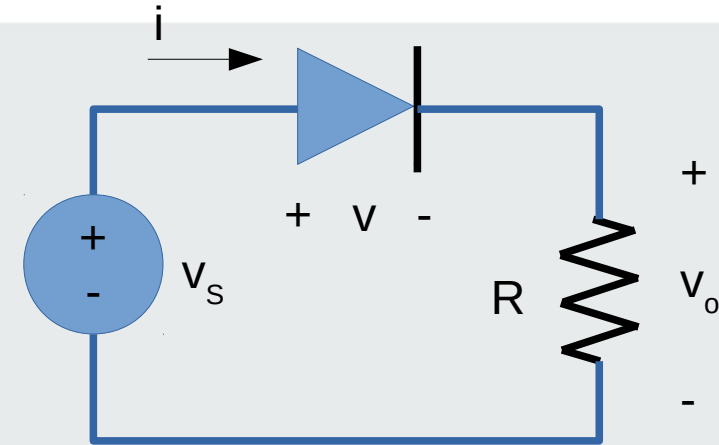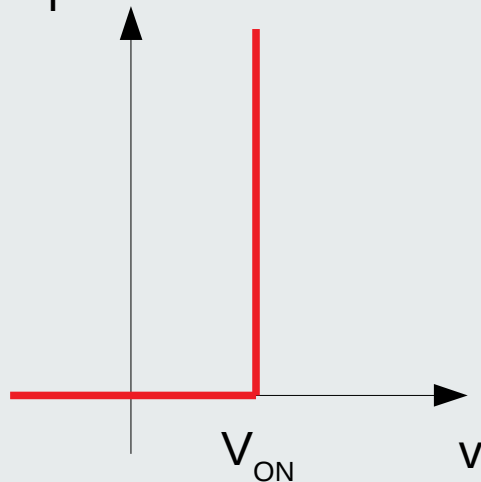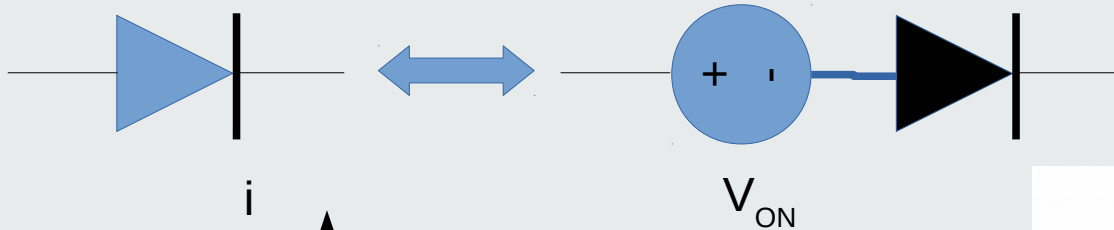
$$\begin{cases} v_o = 0, & v_s < V_{ON} \\ v_o = v_s - V_{ON}, & v_s \geq V_{ON} \end{cases}$$





Diode model with ideal diode + voltage source + resistor
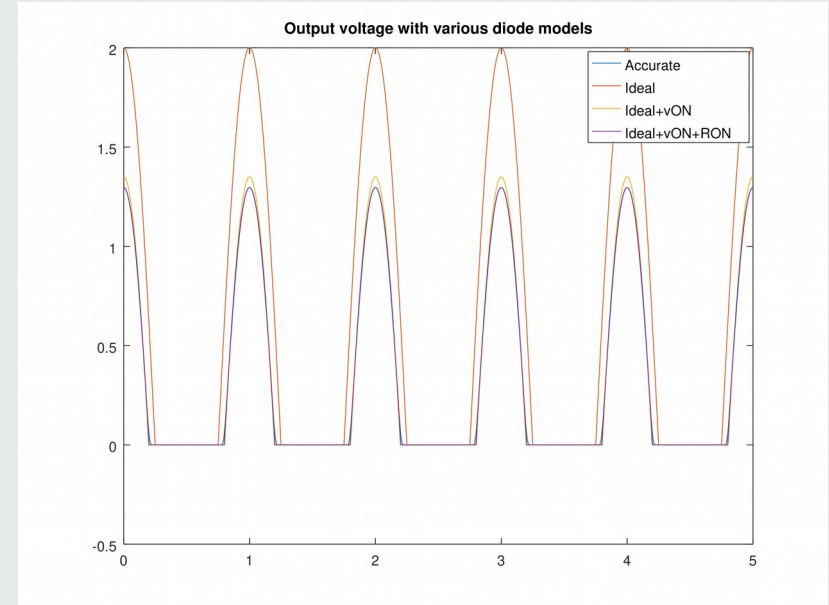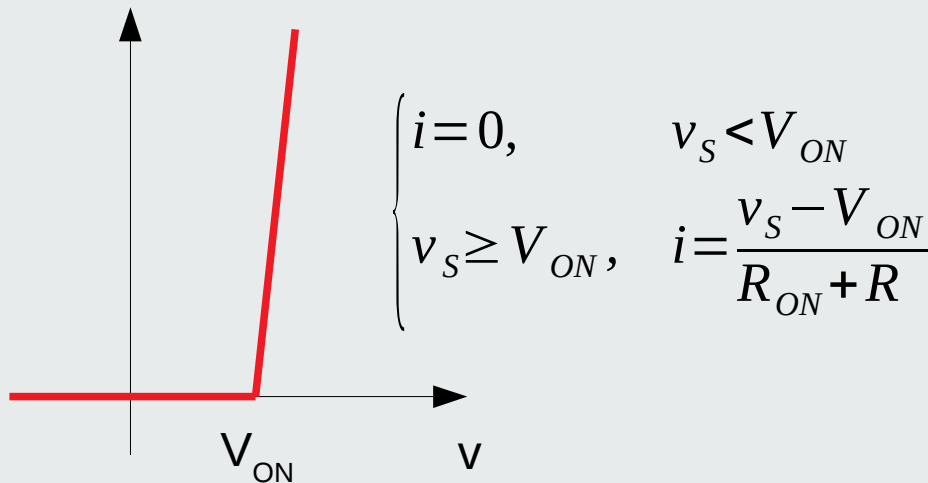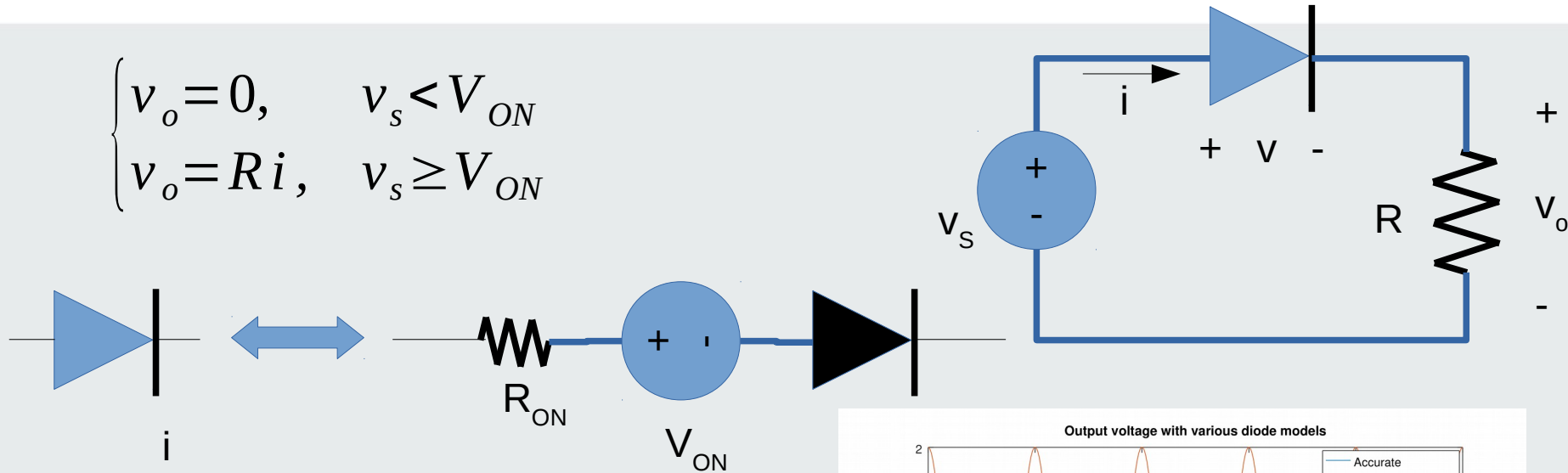
$$\begin{cases} v_o = 0, & v_s < V_{ON} \\ v_o = Ri, & v_s \geq V_{ON} \end{cases}$$



Piece-Wise Linear Diode Model

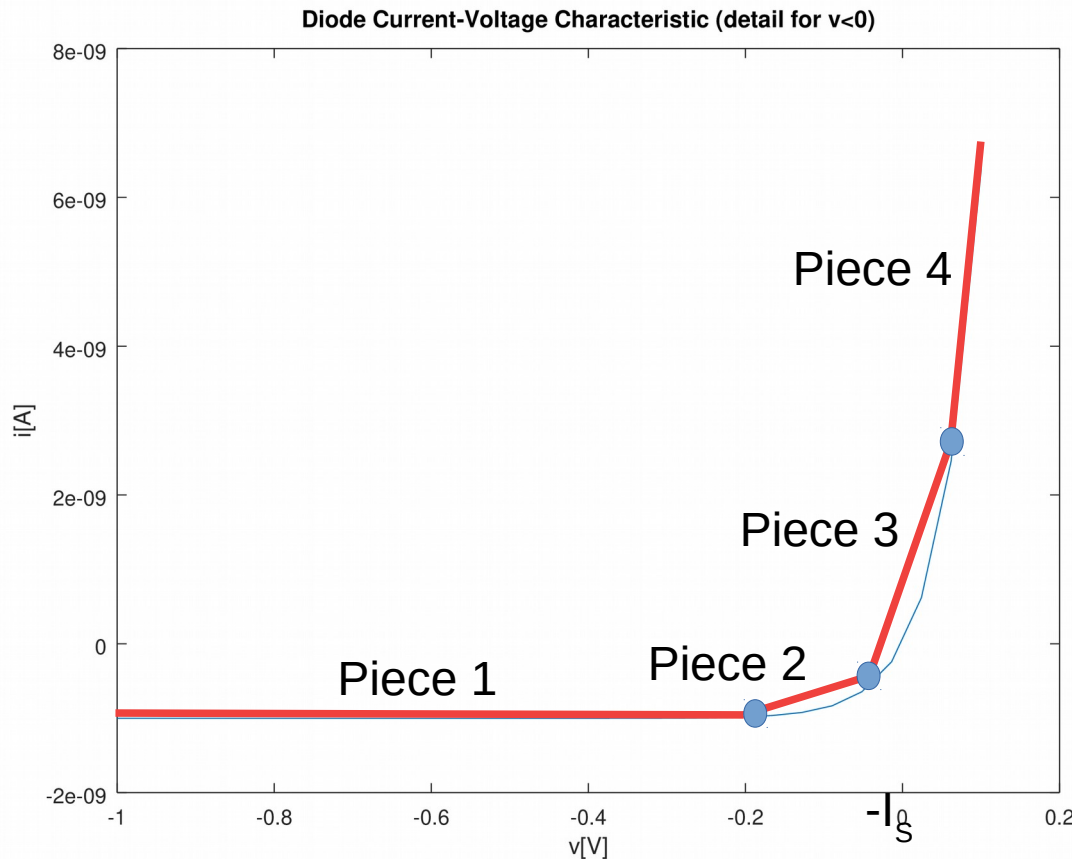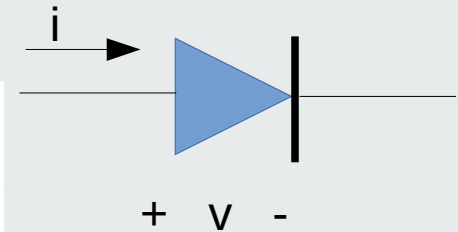

This example model needs:


- I_s
- Three (I,V) points
- Slope for piece 4

8-parameter model...

Is this faster than non-linear model? Maybe...

Incremental Analysis

- In many practical situations, the input voltage has a DC component and an AC component
- The DC component dictates the circuit **operating point**
- The AC component contains the energy or information (the message) delivered
- If the DC component has no information, only the AC component needs to be analysed
- If the amplitude of the AC component is small, the distortion caused by non-linear components such as diodes is small ...
- This is incremental analysis

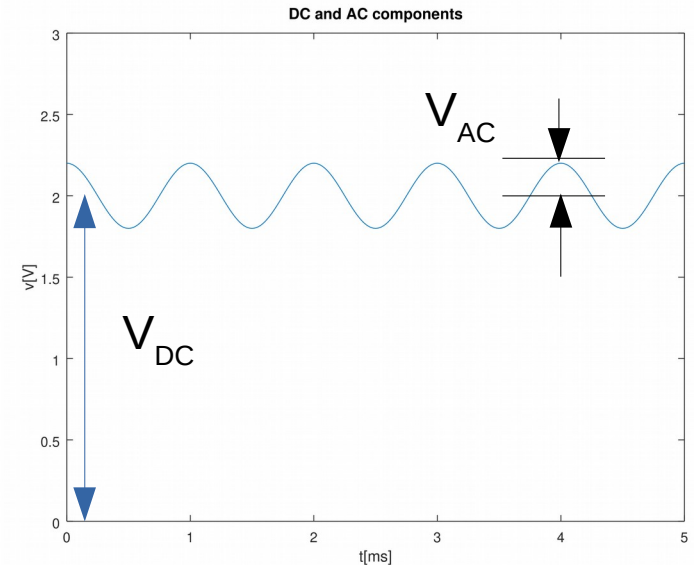

$$v_s(t) = V_{DC} + V_{AC} \cos(2\pi f t)$$

$$v_s(t) = V_{DC} \cos(0t) + V_{AC} \cos(2\pi f t)$$

V_{DC} is zero frequency component
 V_{AC} is frequency f component

Incremental Analysis Notation


$$v_s(t) = V_{DC} + V_{AC} \cos(2\pi f t)$$

$$v_s(t) = V_s + v_s(t)$$

AC increment:
variable and index
lower case

DC: variable and
index upper case

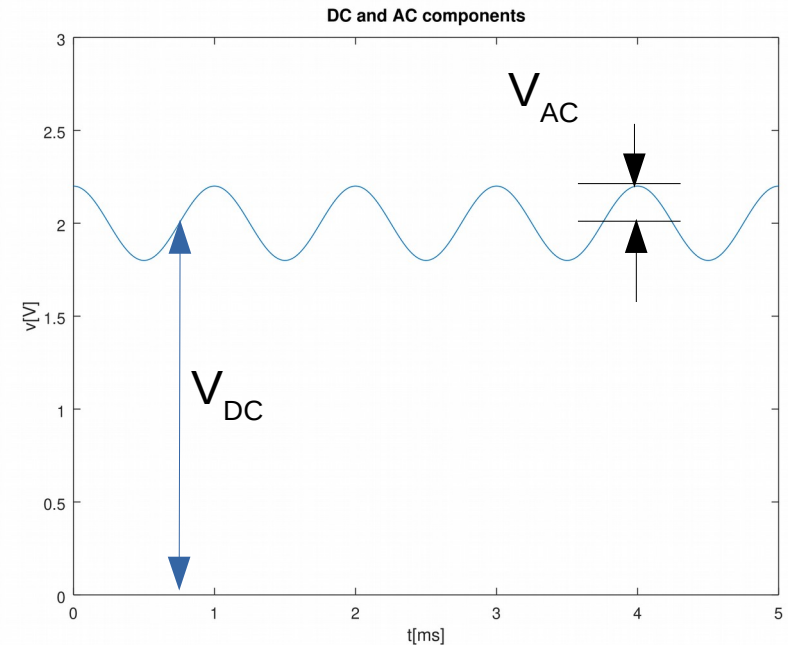Total DC+increment:
variable lower case and
index upper case



$$v_s = \Delta v_s$$

v_s is considered an infinitesimal increment
in incremental analysis.

DC and incremental components be
analysed separately!

Operating point

$$v_D + Ri_D - v_s = 0 \quad \text{KVL}$$


$$(V_D + v_d) + R(I_D + i_d) - (V_S + v_s) = 0$$

$$(V_D + RI_D - V_S) + (\cancel{v_d + Ri_d - v_s}) = 0$$

Separate DC and increments

$$v_s = 0 \Rightarrow v_d = 0, \quad i_d = 0 \quad \text{The cause of variations is } v_s$$
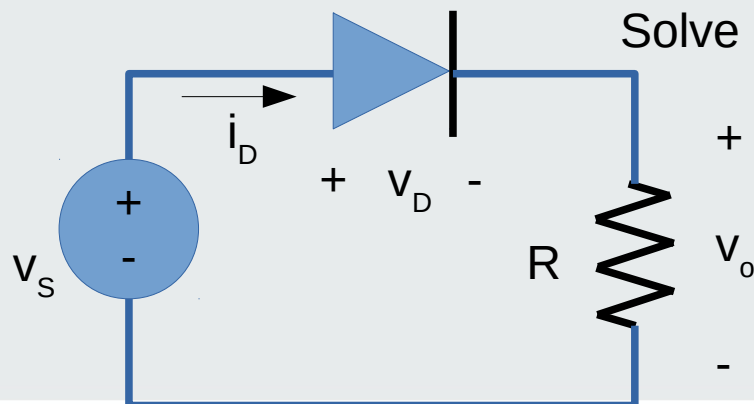
$$V_D + RI_D - V_S = 0 \quad \longrightarrow \text{DC or operating point analysis}$$



Solve non-linear equation to get V_D and I_D (DC values)

Diode incremental model

$$i_D(v_D) = I_S \left(e^{\frac{v_D}{\eta V_T}} - 1 \right) \quad \text{Diode equation}$$

Taylor series expansion


$$i_D(V_D + v_d) = i_D(V_D) + \frac{1}{1!} \frac{di_D}{dv_D}(V_D) v_d + \frac{1}{2!} \frac{d^2 i_D}{dv_D^2}(V_D) v_d^2 + \dots$$

First order approximation for small v_d signal


$$\cancel{I_D} + i_d \approx \cancel{I_D} + \frac{di_D}{dv_D}(V_D) v_d$$

$$i_d \approx \frac{v_d}{r_d} \quad \text{The diode incremental model is approximately a resistor!}$$
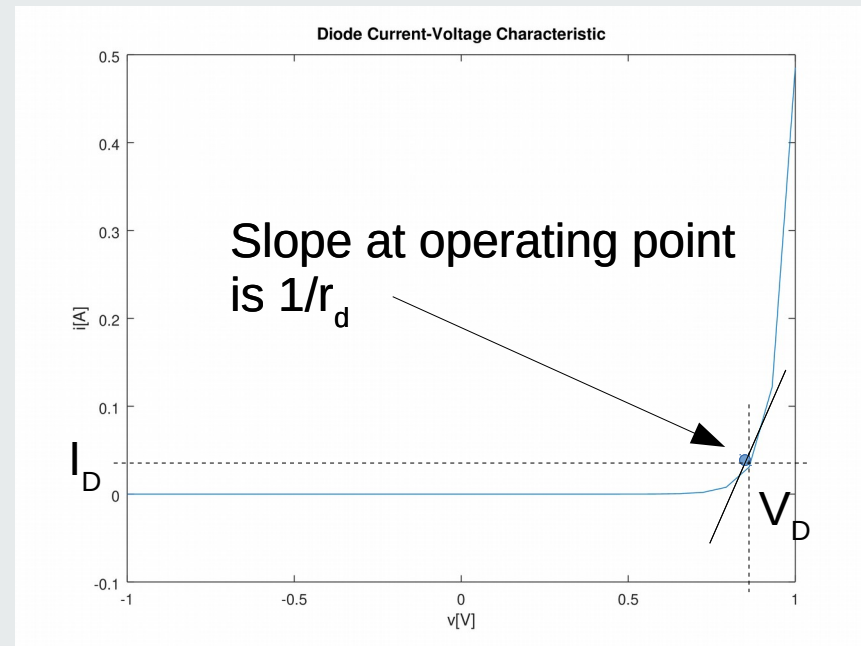
$$r_d = \frac{dv_D}{di_D}(V_D) \quad \text{The diode incremental resistor}$$



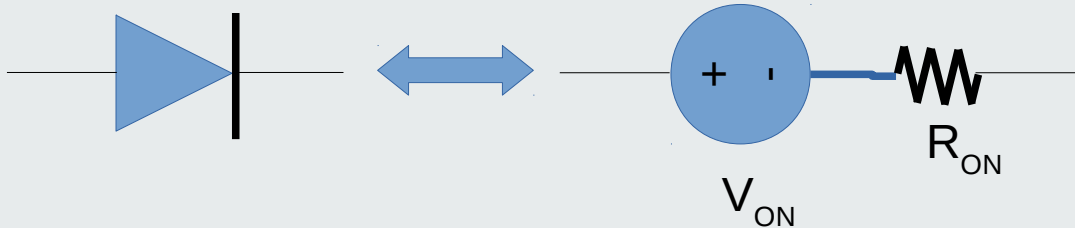
Diode complete model at given operating point



- Attention: model only valid for given operating point!
- DC voltage V_D varies with the operating point (V_D, I_D)!
- Incremental resistor r_d varies with the operating point!
- Model only valid for OP and **small** variations around it!

$$V_D = V_D(V_S)$$

$$r_d = r_d(V_D) = r_d(V_S)$$

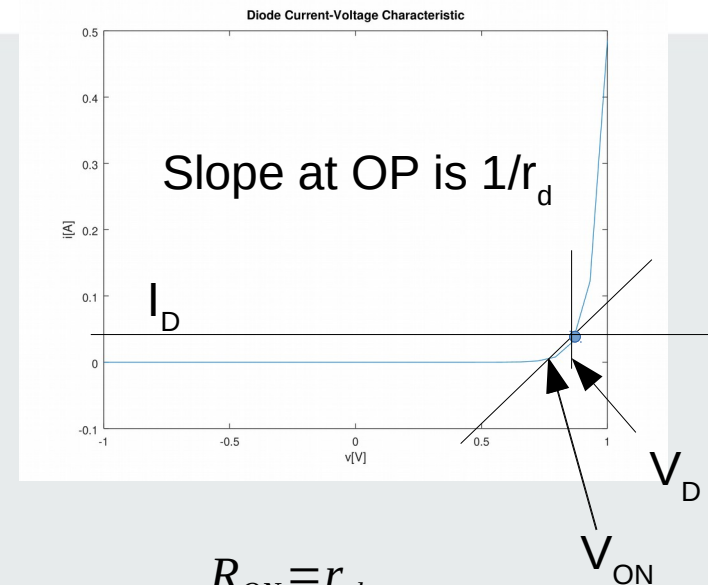

$$R_{ON} = r_d$$

$$r_d = \frac{\eta V_T}{\frac{V_D}{I_S e^{\eta V_T}}}$$

$$V_{ON} = V_D - r_d I_D$$

$$i_D = \begin{cases} 0, & v_D < V_{ON} \\ \frac{v_d - V_{ON}}{R_{ON}}, & v_D \geq V_{ON} \end{cases}$$


Exercise: operating point and incremental analysis

$$v_s(t) = 2 + A \cos(2\pi f t)$$

$$I_s = 1 \text{ nA}$$

$$R = 1 \text{ k}\Omega$$

$$f = 1 \text{ kHz}$$

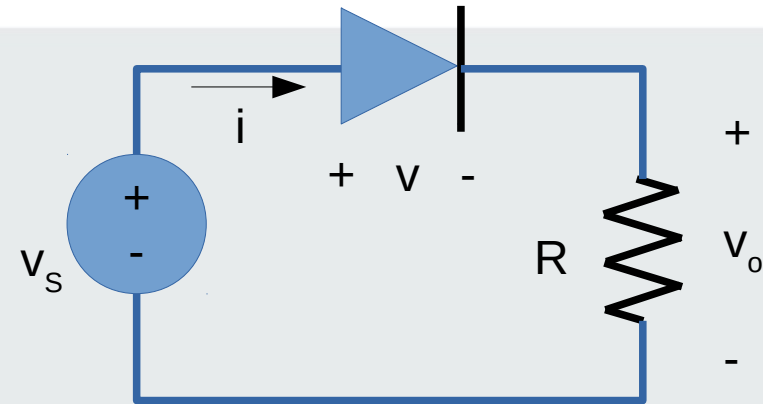

1. Using the diode equation, plot v_o for $A=20\text{mV}$, 200mV and 1.5V , for 5ms
2. Using incremental analysis, plot v_o for $A=20\text{mV}$, 200mV and 1.5V
3. Compare the plots of 1. and 2.


Exercise resolution (1)

$$v_s(t) = 2 + A \cos(2\pi f t)$$

$$I_S = 1 \text{ nA}$$

$$R = 1 \text{ k}\Omega$$

$$f = 1 \text{ kHz}$$

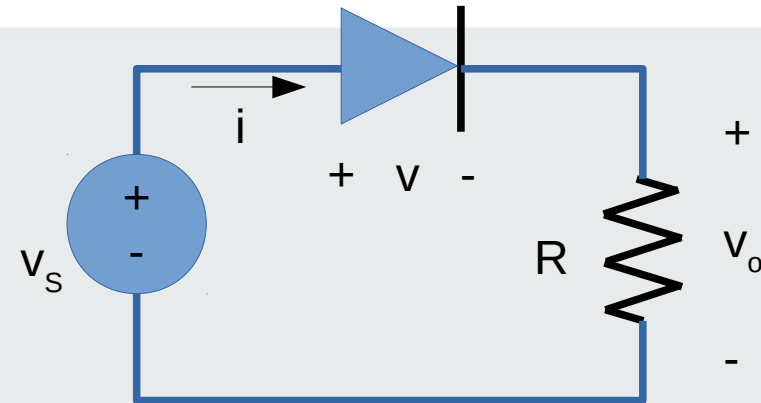


1. Using the diode equation, plot v_o for $A=20\text{mV}$, 200mV and 1.5V , for 5ms

The diode equation was taught in Lecture 11. Using the same Octave functions, the v_o is plotted for the 3 values of A (see Octave script l12_exercise.m)

For $A=1.5\text{V}$ the distortion is visible (maxima sharper than minima)

For $A=200\text{mV}$ distortion is not visible but it is there. Spectral analysis would reveal it.

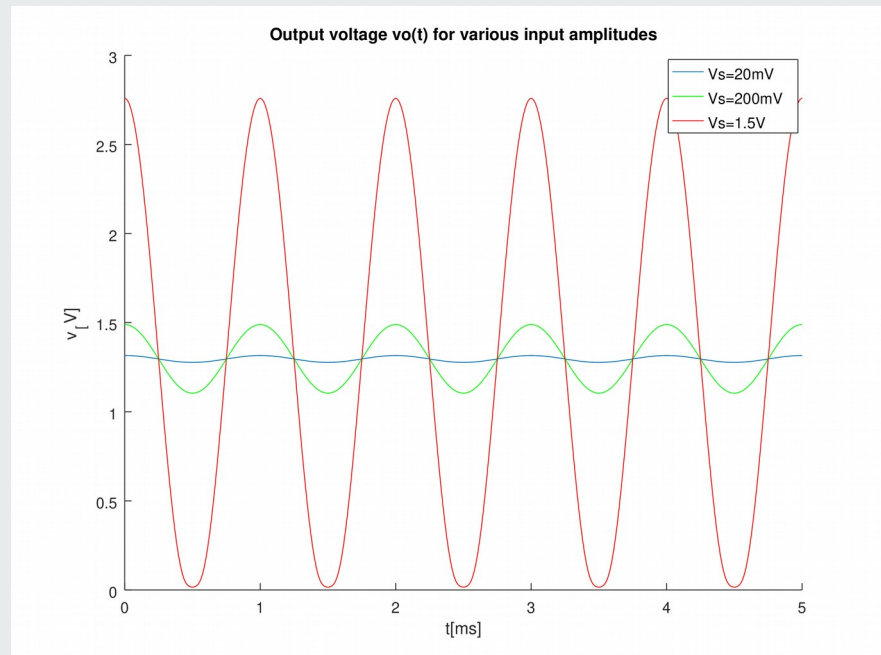For $A=20\text{mV}$ the distortion is very low and the waveform is almost a pure tone.



Exercise resolution (2)


$$v_s(t) = 2 + A \cos(2\pi f t)$$

$$I_S = 1 \text{ nA}, R = 1 \text{ k}\Omega, f = 1 \text{ kHz}$$

$$v_o = \frac{R}{R + r_d} v_s \quad \text{Incremental output voltage}$$



$$V_O = R I_D \quad \text{DC output voltage}$$

$$v_o = V_O + v_o$$

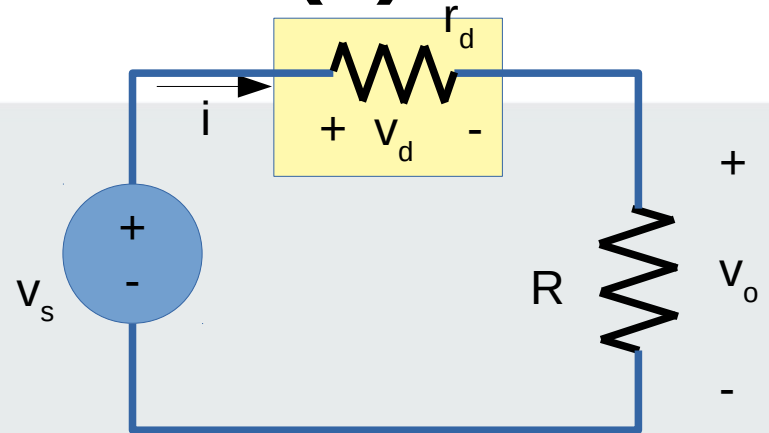


Incremental circuit model: LINEAR!

Total output voltage

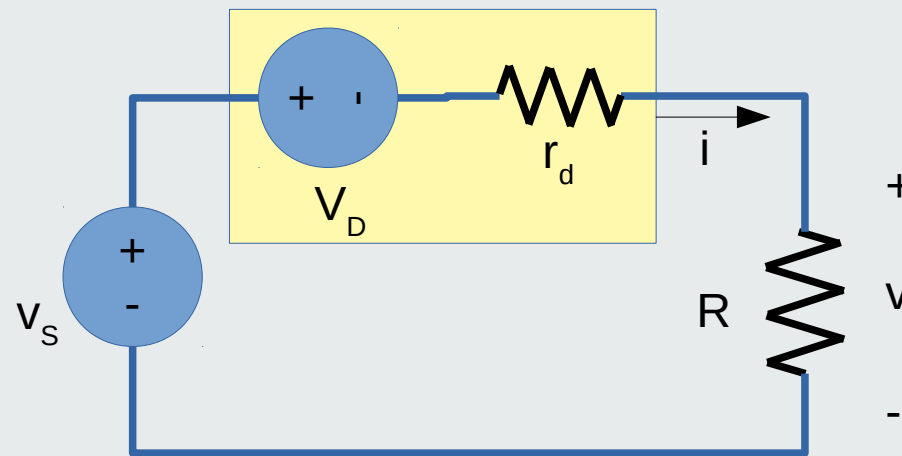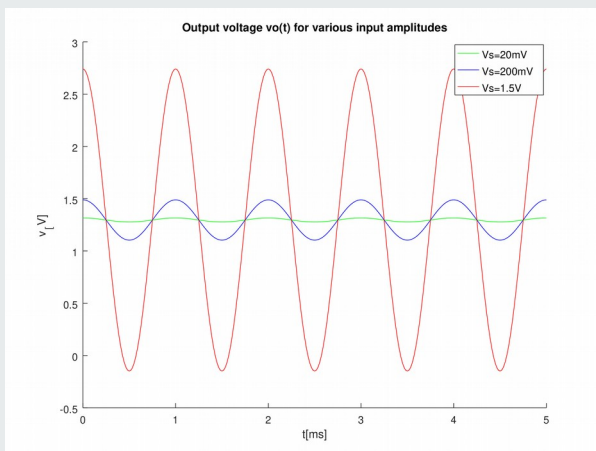


Complete circuit model via incremental analysis: LINEAR!

Exercise resolution (3)

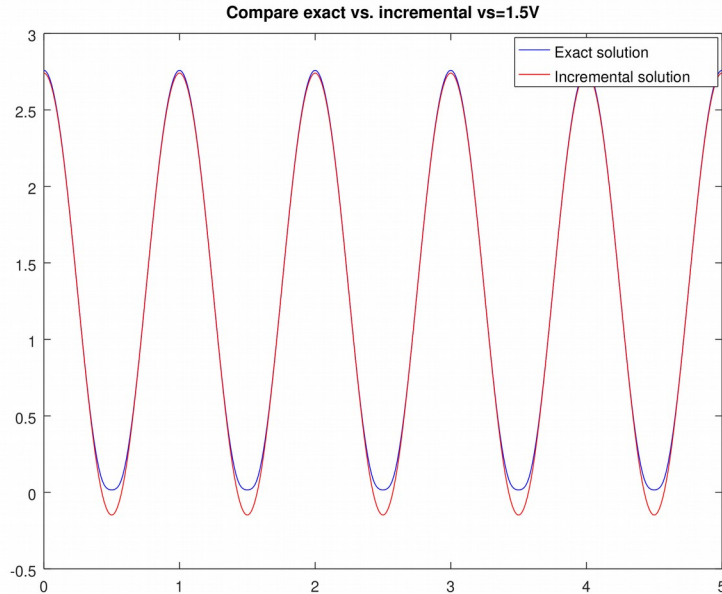

Non-linear and incremental solutions differ visibly

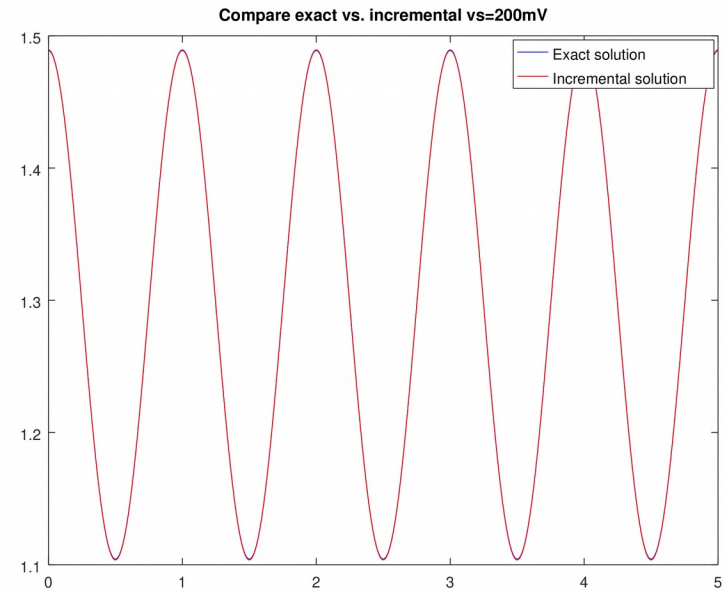Incremental solution bad for large signals!



Exact and incremental solutions differ little

Incremental solution good for small signals!

Even better for $v_s=20mV$ though not shown

Conclusion

- Ideal diode model
- Voltage source diode model
- Voltage source plus resistor diode model
- Piecewise linear diode model
- Incremental diode model
- Exercise