

TEST 2 EXAMPLE 2 SOLVED

1.


a) $I_S = 1 \text{ mA} \Rightarrow \text{LED OFF}$

$$R = R_2 // R_3 = 2 \text{ k}\Omega$$


I_S D_1 also OFF $V_o = R I_S = 4 \text{ V}$ but this is impossible because $V_{D1} \leq 0.5$

So $V_o = V_{D1 \text{ ON}} = 0.5 \text{ V}$

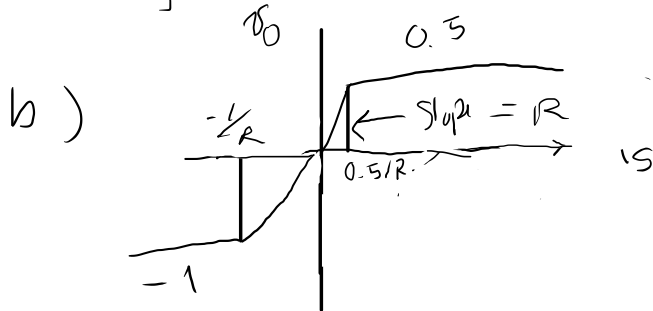$I_S = 1 \text{ mA} \Rightarrow D_1 \text{ OFF LED ON } V_o = -V_{\text{LED ON}} = -1 \text{ V}$
(same reasoning)



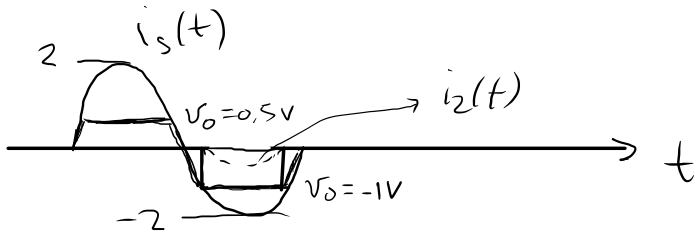c) $i_s(t) = 2 \sin(\omega t) \text{ mA}$



d) Max current in $D_1 = I_{S_{\text{MAX}}} - \frac{V_{D1\text{ON}}}{R_2 \parallel R_3} = I_{D1\text{MAX}}$

Max power in $D_1 = V_{D1\text{ON}} \times I_{D1\text{MAX}}$


Max current in LED $= I_{\text{LEDMAX}} = I_{S_{\text{MAX}}} - \frac{V_{\text{LEDON}}}{R_3 \parallel R_2}$

Max power in LED $= V_{\text{LEDON}} \times I_{\text{LEDMAX}}$

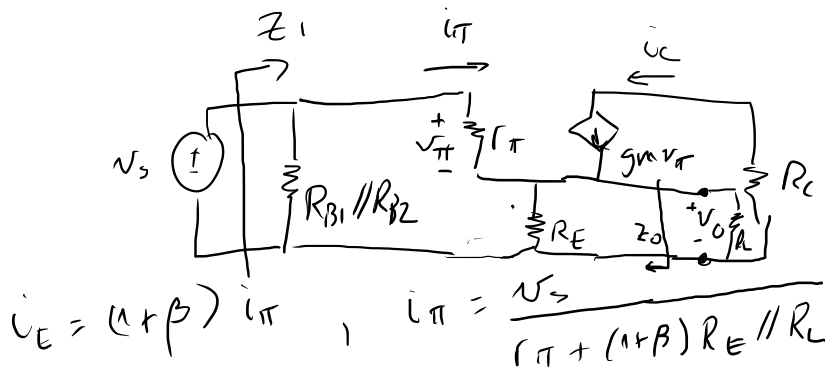2. R_{B2} is meant between base and V_{CC} negative terminal (typo R_{B1}). Capacitors are open at O.P.

$$V_B = V_E + 0.7, \quad I_E = \frac{V_E}{R_E}, \quad I_B = \frac{I_E}{1+\beta}, \quad I_{B1} = \frac{V_{CC} - V_B}{R_{B1}}$$

$$I_{B2} = \frac{V_B}{R_{B2}}, \quad I_{B2} = I_{B1} - I_B \Rightarrow \boxed{R_{B2} = \frac{V_B}{I_{B1} - I_B}}$$



$$g_m v_\pi = \beta i_\pi$$

$$v_o = R_E \parallel R_C i_E$$

$$i_E = (1+\beta) i_\pi, \quad i_\pi = \frac{v_s}{r_\pi + (1+\beta) R_E \parallel R_C}$$

$$A_v = \frac{v_o}{v_s} = R_E \parallel R_C (1+\beta) \frac{1}{r_\pi + (1+\beta) R_E \parallel R_C}$$

$$Z_i = R_{B1} \parallel R_{B2} \parallel (r_\pi + (1+\beta) R_E)$$

$$Z_o = \frac{v_o}{i_E - i_\pi - i_c} \quad \begin{matrix} \text{(NO } R_L!) \\ \text{(} v_s = 0!) \end{matrix}$$

$$i_E = \frac{v_o}{R_E}, \quad i_\pi = \frac{-v_o}{r_\pi}$$

$$i_c = \beta i_\pi$$

$$c) \omega_L = \frac{1}{R_{eq} C_0}, \quad R_{eq} = R_L + Z_0$$

3. a) $V_A = 2V$, $V_B = 5V$, use Superposition, switch = 1.
inverting and non inverting amp formulae

$$V_O = -\frac{R_F}{R_A} V_A + \frac{R_{B2}}{R_{B1} + R_{B2}} \left(1 + \frac{R_F}{R_A}\right) V_B$$

$$= -2 \times 2 + \frac{0.2}{2.2} \times 3 \times 5 \quad V \text{ (no saturation)}$$

b) Switch = 2 \Rightarrow P_{OFF} and $V_D = \frac{2}{2.2} V_B (< 0)$
 $V_A = 3V$, $V_B = -1V$ Using eq. (3a) $V_O < -5V$ which
 is impossible as op-amp saturates at $V_O = -5V$ //

c) Superposition, Switch = 2
 $V_A = -1V$, $V_B = 2 \cos \omega t$ V

$$V_{A'} = -1 \times 2 = -2V$$

$$V_O = V_{OA} + V_{OB}$$

D OFF : $V_{OB} = \frac{R_{B2}}{R_{B1} + R_{B2}} \left(1 + \frac{R_F}{R_A} \right) V_B$ as before


D ON : $V_{OB} = \left(1 + \frac{R_F}{R_A} \right) (V_B - 0.7)$

Diode switches ON when $V_{RB1} = 0.7V$ that is

when $\frac{R_{B1}}{R_{B1} + R_{B2}} V_B \geq 0.7V \Rightarrow V_B \geq 0.7 \times \frac{2.2}{2} V$

V_{RB1} with diode OFF
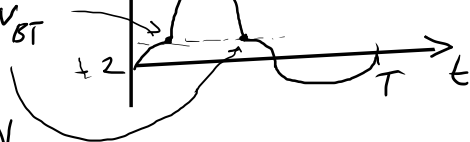
$$V_O(t) = \begin{cases} -2 + \frac{0.2}{2.2} \times 3 V_B(t), & V_B < 0.7 \times \frac{2.2}{2} V = V_{BT} \\ -2 + 3(V_B - 0.7), & V_B \geq 0.7 \times \frac{2.2}{2} V \end{cases}$$




d) switch = 3, $V_A = -1V$, $V_B = \cos(\omega t)$, $f = 1kHz$

Superposition $V_O = V_{OA} + V_{OB} = -2 + V_{OB}$

$$V_{OB}(s) = \left(1 + \frac{R_F}{R_A}\right) \frac{R_{B2}}{R_{B1} \parallel \frac{1}{sC} + R_{B2}} V_B(s)$$

Make $s = j\omega = j2\pi f$ and compute $\frac{V_{OB}(j\omega)}{V_B(j\omega)} = T$
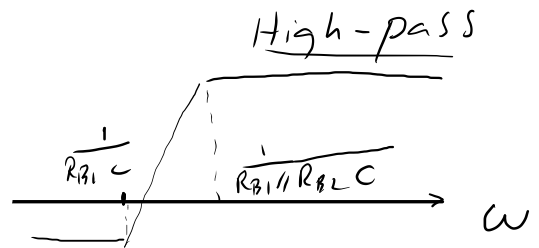
$$V_O(t) = 1 + 1 \cos(\omega t + \angle T)$$



$$\begin{aligned} T(s) &= \frac{R_{B2} \times 3}{\frac{R_{B1} \parallel \frac{1}{sC}}{R_{B1} + \frac{1}{sC}} + R_{B2}} = \frac{R_{B2} \times 3}{\frac{R_{B1}}{1 + R_{B1}Cs} + R_{B2}} = \frac{3R_{B2}(1 + R_{B1}Cs)}{R_{B1} + R_{B2}(1 + R_{B1}Cs)} \\ &= \frac{3R_{B2}(1 + R_{B1}Cs)}{R_{B1} + R_{B2} + R_{B1}R_{B2}Cs} = \frac{3R_{B2}}{R_{B1} + R_{B2}} \frac{1 + R_{B1}Cs}{1 + \frac{R_{B1}R_{B2}}{R_{B1} + R_{B2}}Cs} \end{aligned}$$