


Circuit Theory and Electronics Fundamentals

Lecture 20: MOS Amplifiers

- Common source amplifier
 - OP, Gain, input and output impedances
- Common drain amplifier
 - OP, Gain, input and output impedances

The common source amplifier

Goal: amplify voltage

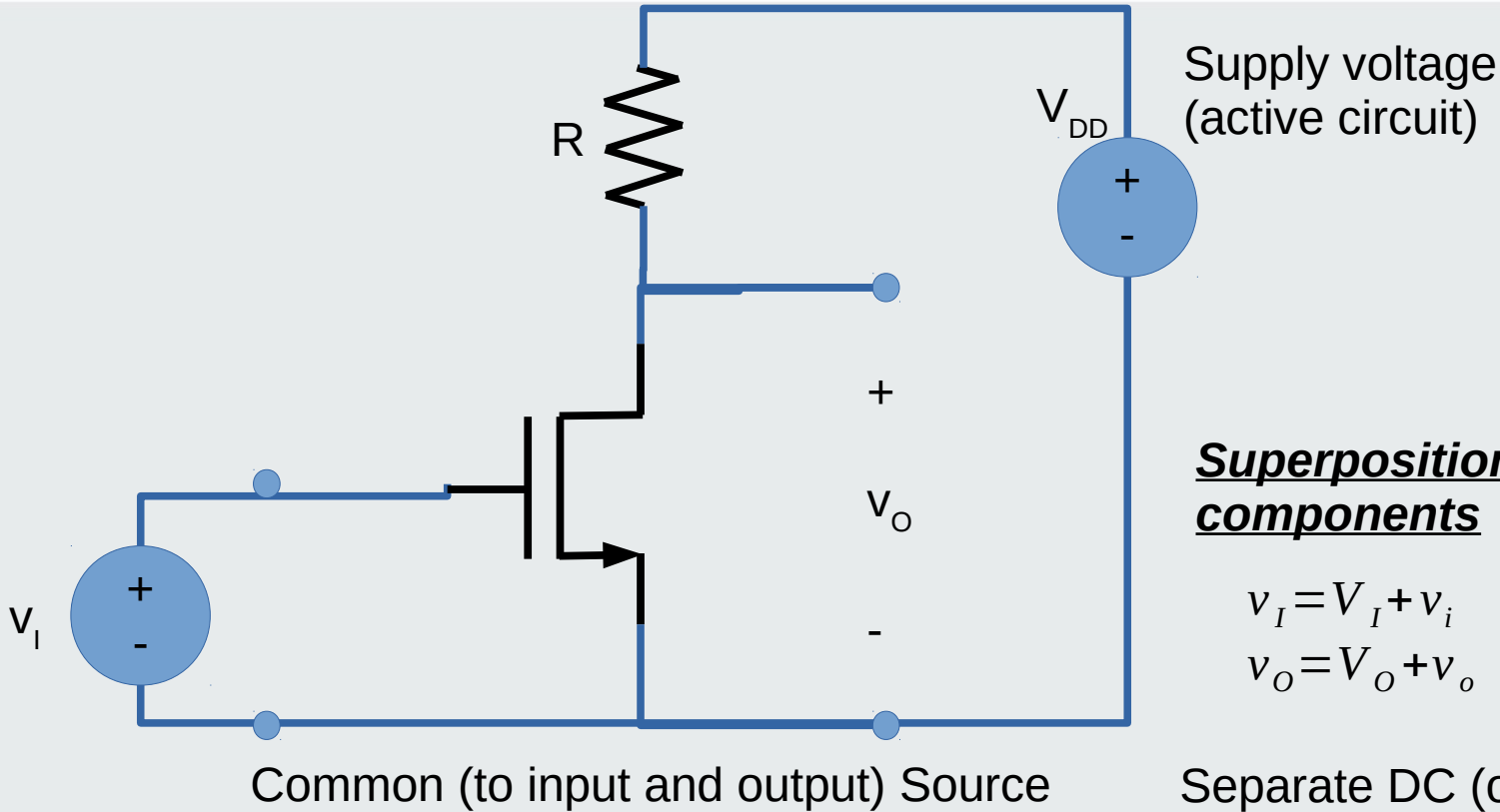

Superposition of DC and AC components

$$v_I = V_I + v_i$$

$$v_O = V_O + v_o$$


Separate DC (operating point) and AC (incremental) analyses

Transistor must operate in the Saturation Region:

$$v_O = v_{DS} > V_{GS} - V_T$$

The common source amplifier

Operating Point (OP) analysis

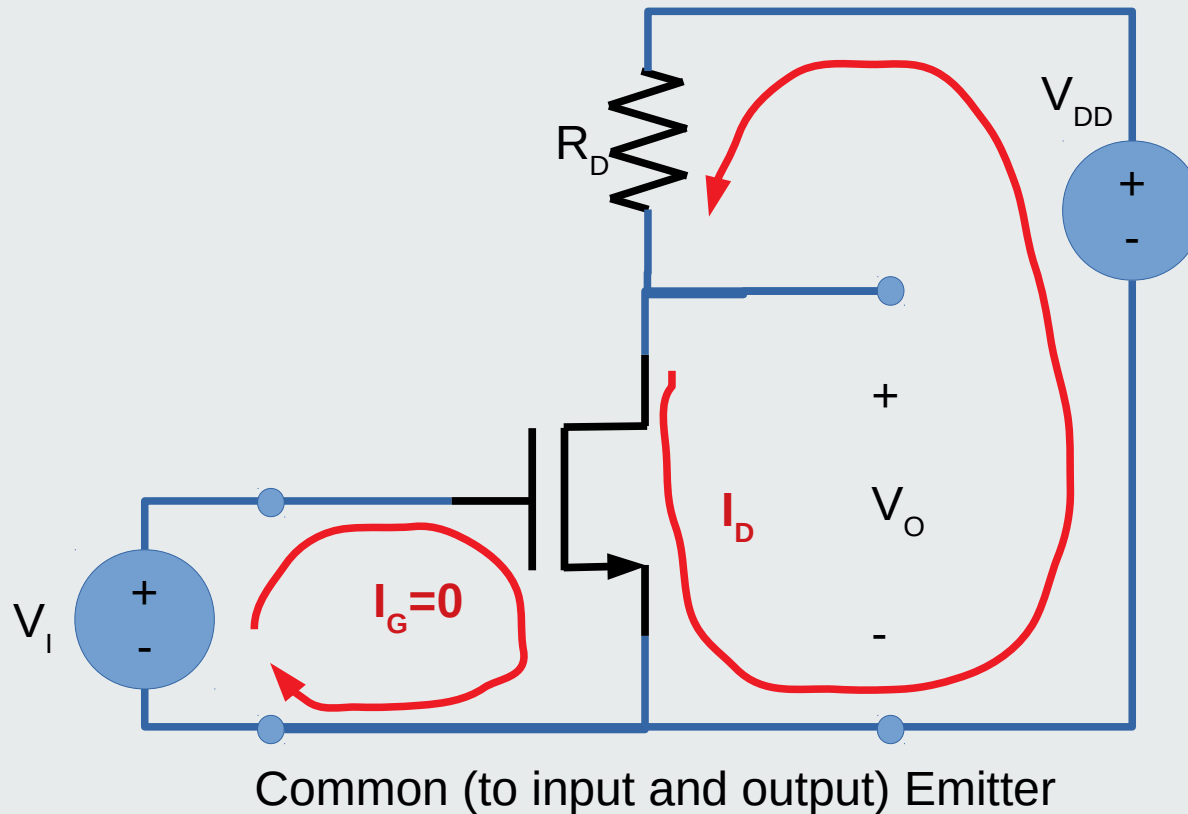

Supply voltage
(active circuit)

Mesh analysis

$$\begin{cases} -V_I + V_{GS} = 0 \text{ (mesh G)} \\ R_D I_D + V_O - V_{DD} = 0 \text{ (mesh D)} \end{cases}$$

$$V_O = V_{DD} - R_D I_D$$

$$I_D = k(V_I - V_T)^2$$


$$V_O = V_{DD} - R_D k(V_I - V_T)^2$$

Non linear model!

Saturation Region condition: $v_{DS} = V_O > v_{GS} - V_T = v_I - V_T$

The common source amplifier

Incremental analysis: gain

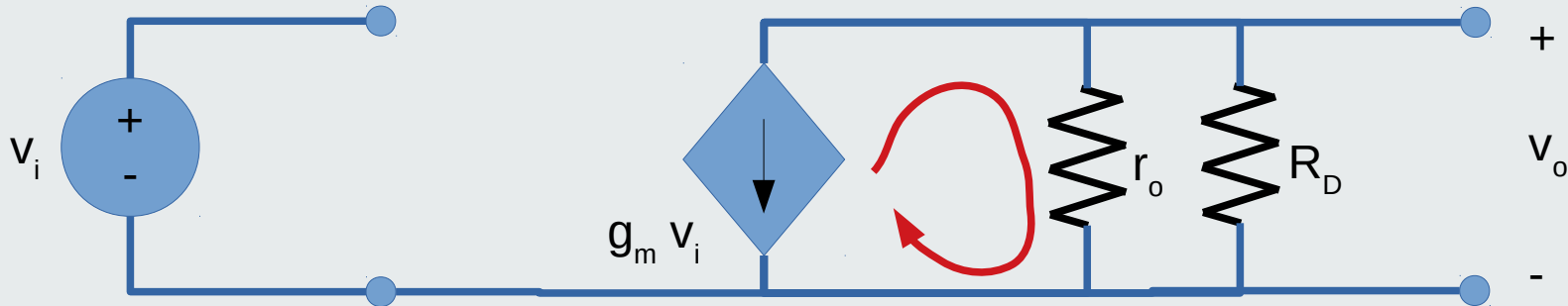

Compute incremental parameters after OP

$$g_m = \frac{2 I_D}{V_I - V_T}$$

$$r_o \approx \frac{\lambda^{-1}}{I_D}$$

$$v_o = -g_m (r_o \parallel R_D) v_i$$

$$A_V = \frac{v_o}{v_i} = -\frac{g_m}{\cancel{\frac{1}{r_o}} + \frac{1}{R_D}} \approx -g_m R_D$$


Gain is negative and moderately high (I_D compared to $v_i - v_T$)

Gain is temperature Dependent due to V_T !

I_D increases with the temperature

The common source amplifier

Input impedance

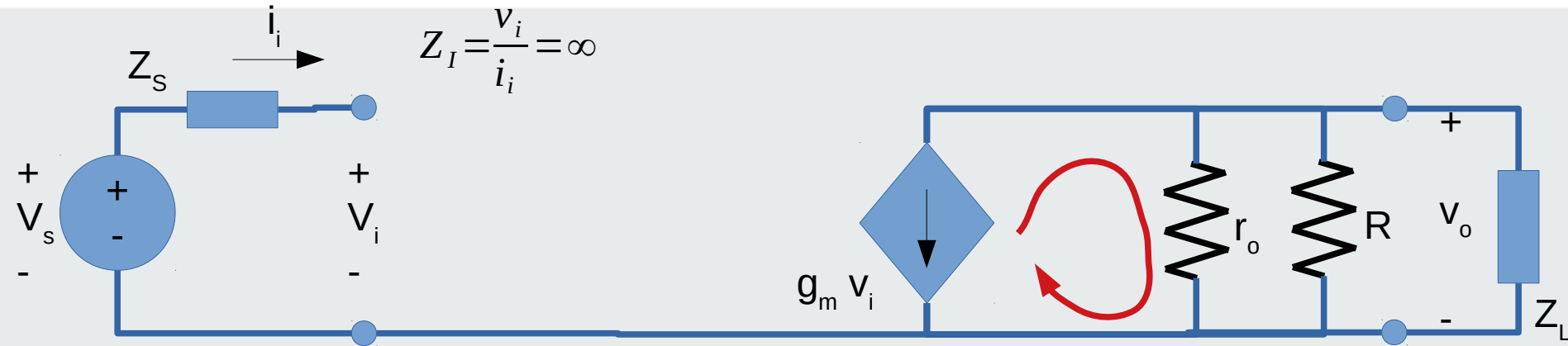


Apply
Input
Voltage

Measure
Input
Current

- If you are the source S you are happy to know that Z_i is infinite – in practice there's a small impedance due to the gate capacitance
- In the above circuit Z_i is independent of the load , which is good!
- A wide range of sources can be connected
- However a very high gate voltage v_s may damage the thin oxide gate
- By convention, Z_i is often given for when the load is absent (short-circuit for current and open-circuit for voltage)

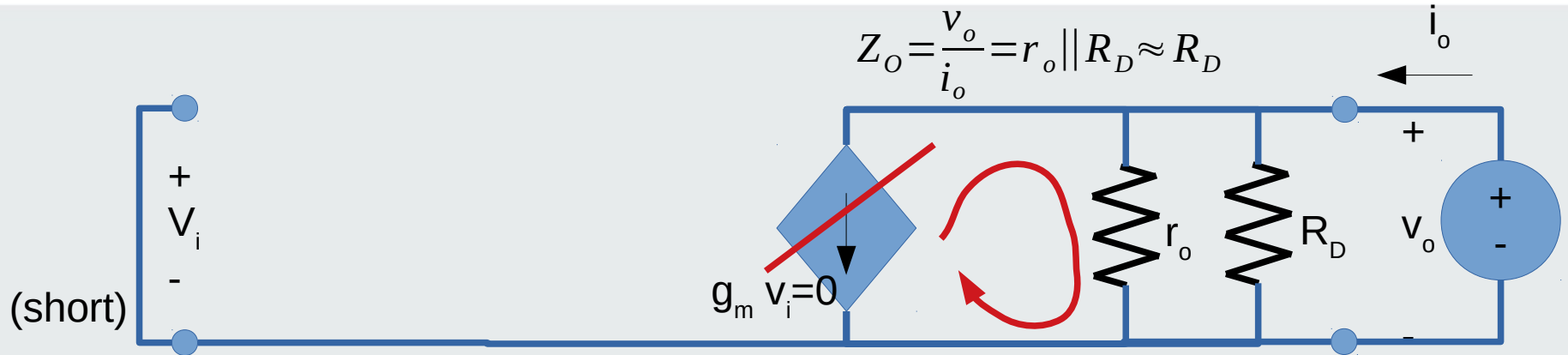The common source amplifier: output impedance




- If you are the load L , you want to know Z_o ; if Z_o does not combine with Z_L , the connection may fail and damage may occur!
- Z_o depends on the source S .
- The nature of the dependence must be stated; otherwise you don't know what you are connecting to.
- By convention, Z_o is given for when the source is off (short-circuit for voltage and open-circuit for current)

Apply
Output
Voltage

Measure
Output
Current


Feed-forward amplifier incremental model

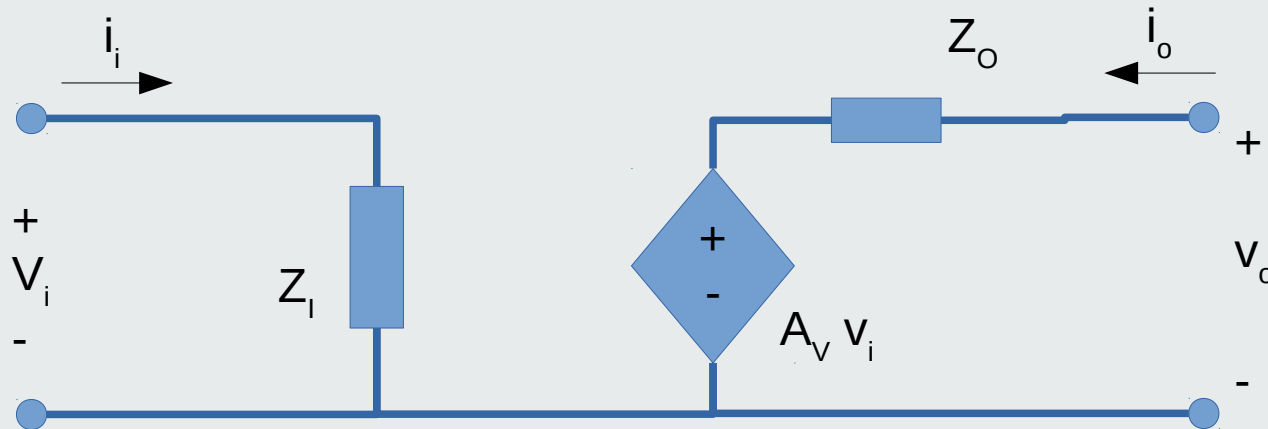

- Amplifier fully characterized by 3 parameters
- Thévenin equivalent at output (A_v , Z_o)
- Equivalent impedance at input (Z_i)

The common source amplifier with degeneration

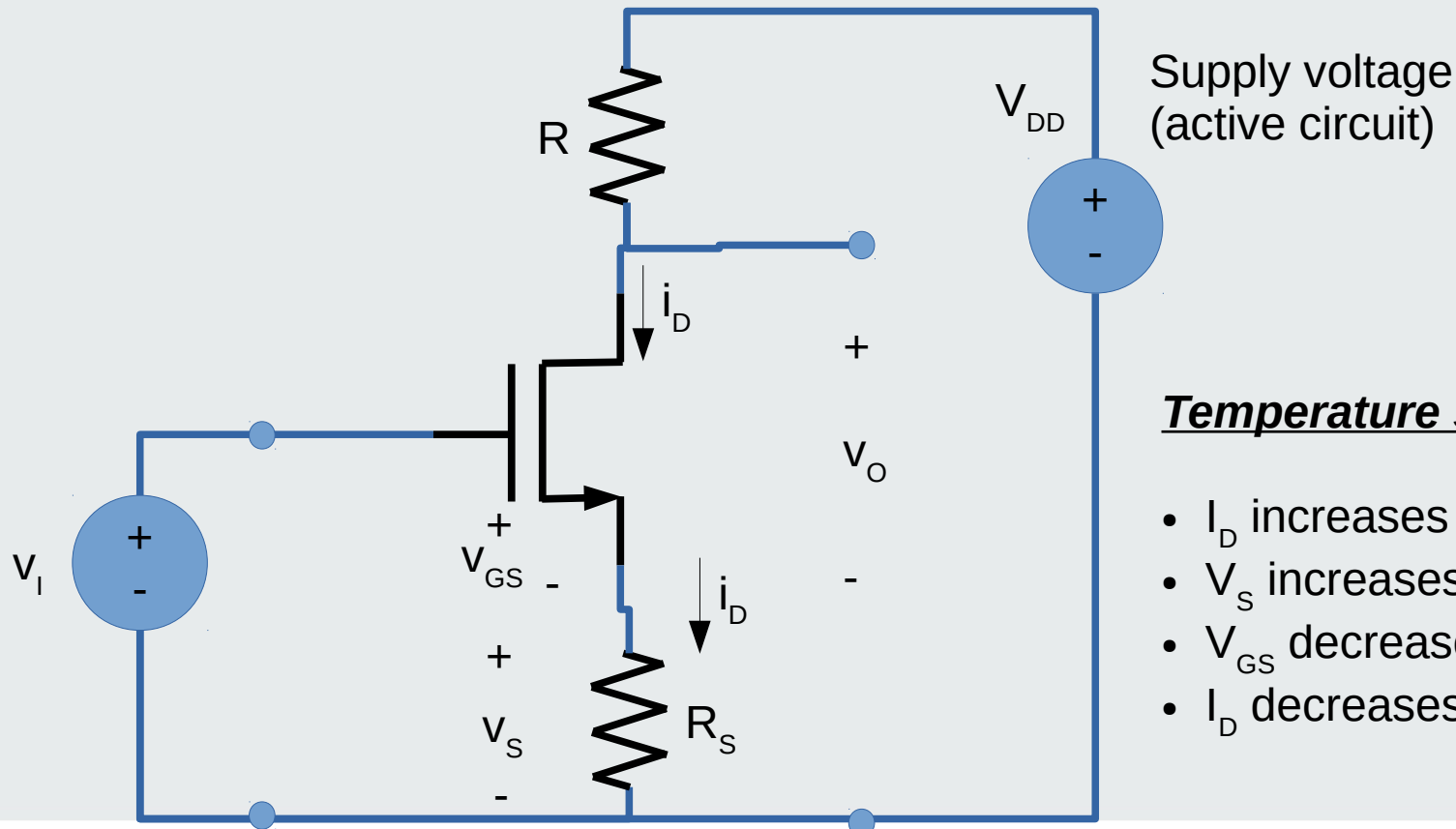Goal: linearise DC gain, improve temperature dependency




Temperature stabilisation

- I_D increases with T
- V_S increases
- V_{GS} decreases
- I_D decreases



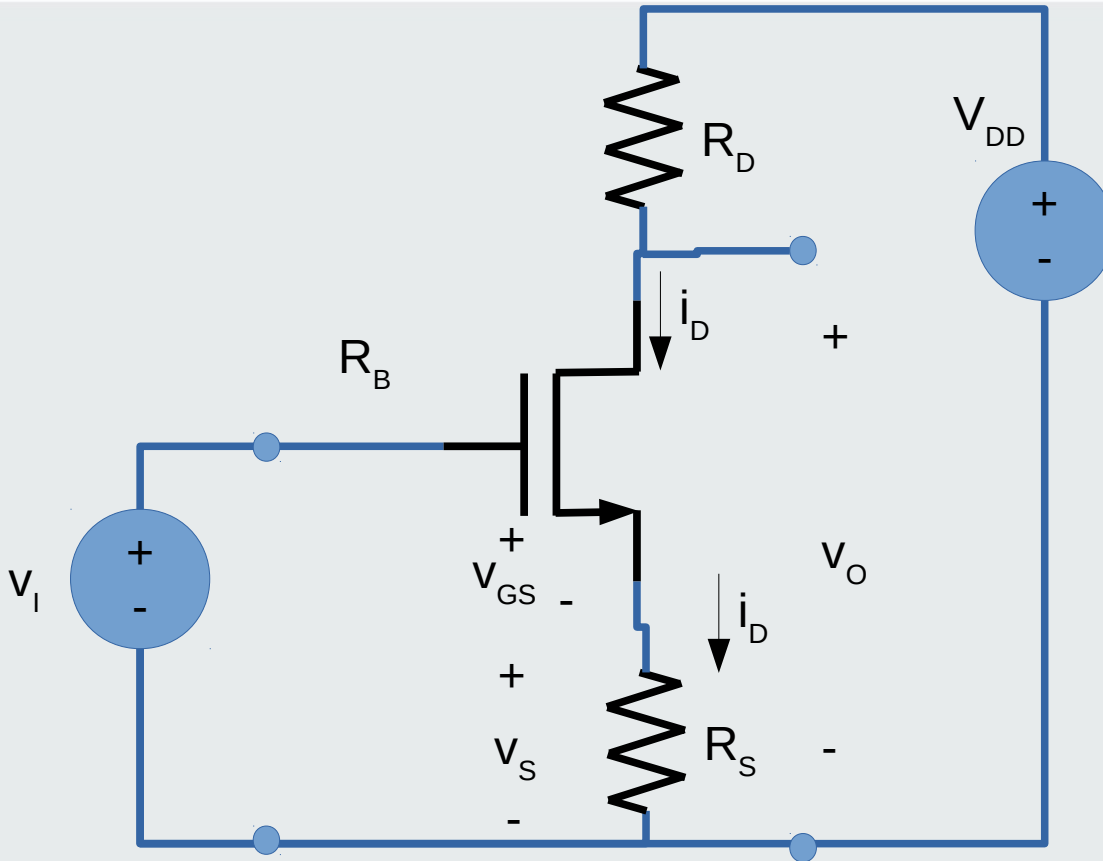The common source amplifier with degeneration: OP



$$I_D = k(V_{GS} - V_T)^2$$

$$V_{GS} - V_T = \sqrt{\frac{I_D}{k}}$$

Mesh analysis

$$\begin{cases} -V_I + V_{GS} + R_S I_D = 0 \text{ (mesh G)} \\ -R_D I_D + V_{DD} - V_O = 0 \text{ (mesh D)} \\ -V_I + V_{GS} + R_S I_D = 0 \\ -R_D I_D + V_{DD} - V_O = 0 \\ -V_I + V_T + \sqrt{\frac{I_D}{k}} + R_S I_D = 0 \\ I_D = \frac{V_{DD} - V_O}{R_D} \\ V_{DS} > V_{GS} - V_T \end{cases}$$

Last condition must be verified for Transistor to be saturated.

Imposes upper limit on v_i

The common source amplifier with degeneration: OP


$$\begin{cases} -V_I + V_T + \sqrt{\frac{I_D}{k}} + R_S I_D = 0 \\ I_D = \frac{V_{DD} - V_O}{R_D} \end{cases}$$

$$V_O = -\frac{R_D}{R_S} (V_I - V_T) - \frac{R_D}{R_S} \sqrt{\frac{4}{k R_S} (V_I - V_T) + \frac{1}{4 k^2 R_S^2}} + V_{DD} - \frac{1}{2 k R_S}$$

Quadratic but still nasty to solve!

Valid for large signals also. Linear term in v_i more important than term in $\text{sqrt}(v_i)$

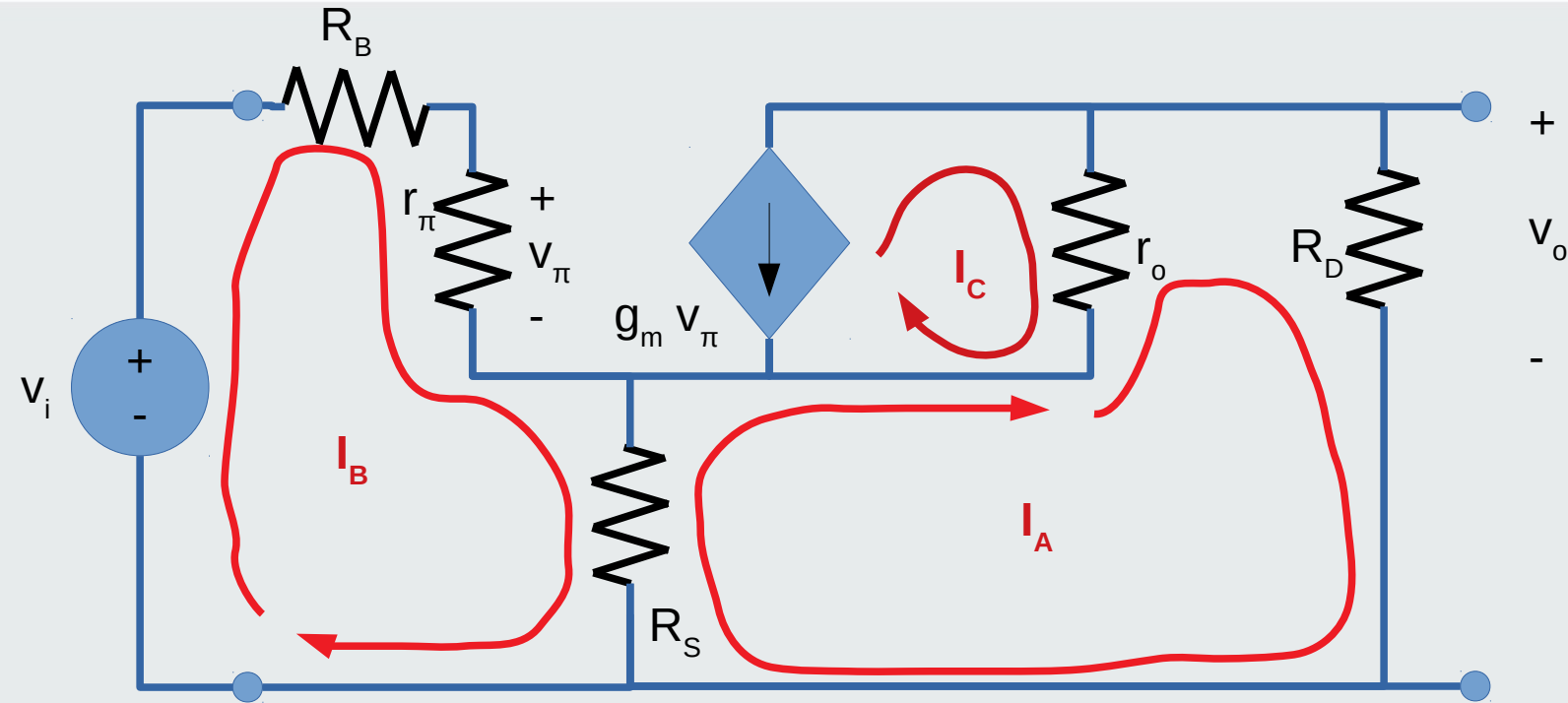The common source amplifier with degeneration: gain (1)



Almost similar to BJT's common emitter with

$$\begin{cases} r_\pi = \infty \\ R_B = 0 \end{cases} \Leftrightarrow \begin{cases} g_\pi = 0 \\ R_B = 0 \end{cases}$$

The common source amplifier with degeneration: gain (2)

$$\frac{v_o}{v_i} = R_D \frac{R_S - g_m r_\pi r_o}{(r_o + R_D + R_S)(R_B + r_\pi + R_S) + g_m R_S r_o r_\pi - R_S^2}$$

$$r_\pi \rightarrow \infty, R_B = 0 \Rightarrow \frac{v_o}{v_i} = - \frac{g_m R_D r_o}{r_o + R_D + R_S + g_m R_S r_o}$$

$$r_o \rightarrow \infty \Rightarrow \frac{v_o}{v_i} = - \frac{g_m R_D}{1 + g_m R_S}$$

$$g_m R_S \gg 1 \Rightarrow \frac{v_o}{v_i} = - \frac{R_D}{R_S}$$

Degenerated common source amp. : input impedance

$$Z_i = \frac{v_i}{i_g}$$


$$i_g = 0$$

$$Z_i = \infty$$

$$Z_i = \frac{1}{j \omega C_{gs}}$$

Small parasitic capacitance \rightarrow high input impedance

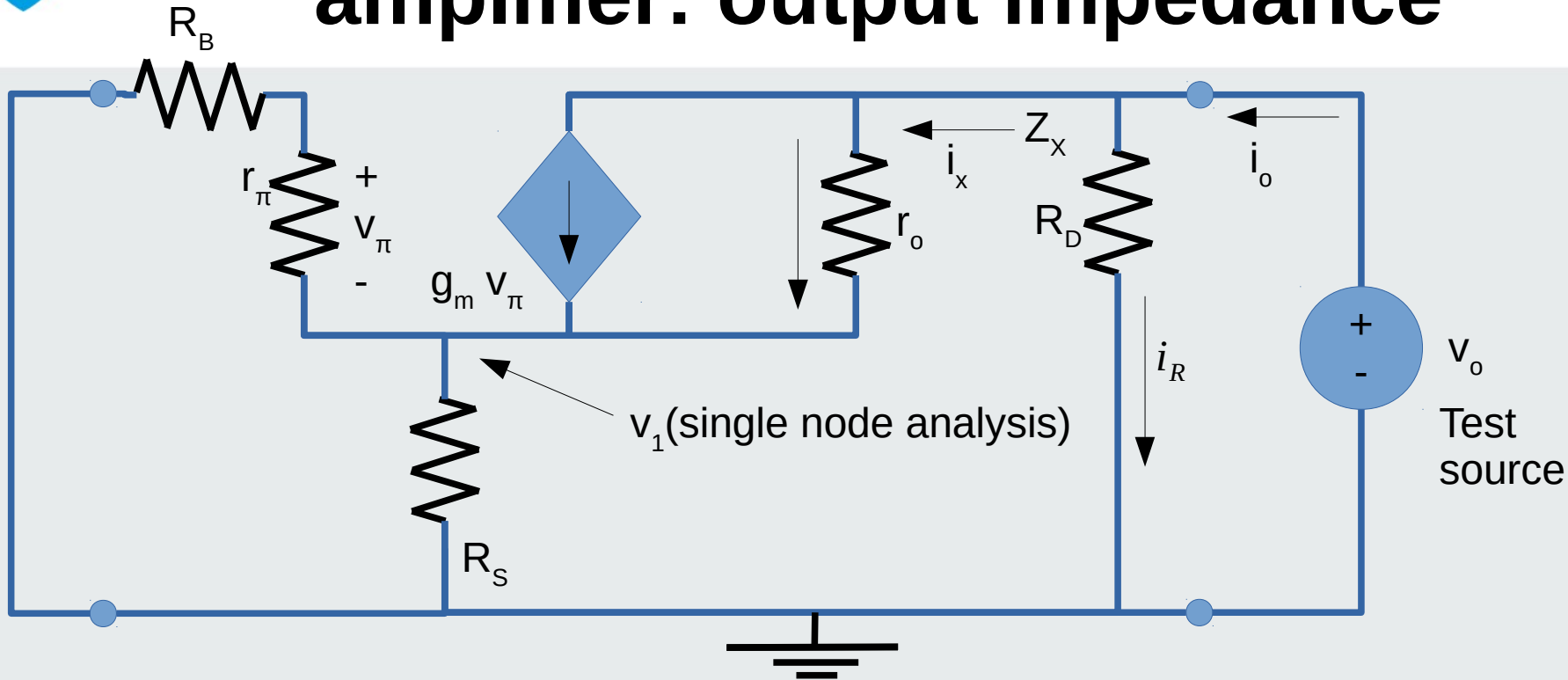Degenerated common source amplifier: output impedance



Almost similar to BJT's common emitter with

$$\begin{cases} r_\pi = \infty \\ R_B = 0 \end{cases} \Leftrightarrow \begin{cases} g_\pi = 0 \\ R_B = 0 \end{cases}$$

Degenerated common source amplifier: output impedance

$$Z_o = R_D \parallel \frac{r_o [(R_B + r_\pi) \parallel R_S]}{r_o \parallel r_\pi + R_B \parallel R_S \parallel \frac{r_\pi + R_B}{g_m r_\pi}}$$

$$r_\pi \rightarrow \infty, R_B = 0 \Rightarrow Z_o = R_D \parallel \frac{r_o R_S}{r_o \parallel R_S \parallel \frac{1}{g_m}}$$


$$Z_o = R_D \parallel r_o R_S \left(\frac{1}{r_o} + \frac{1}{R_S} + g_m \right)$$

$$Z_o = R_D \parallel (R_S + r_o + g_m R_S r_o)$$

$$r_o \rightarrow \infty \Rightarrow Z_o = R_D$$

A high R_D is important for high gain but makes Z_o high... :-)

Common source amplifier problem

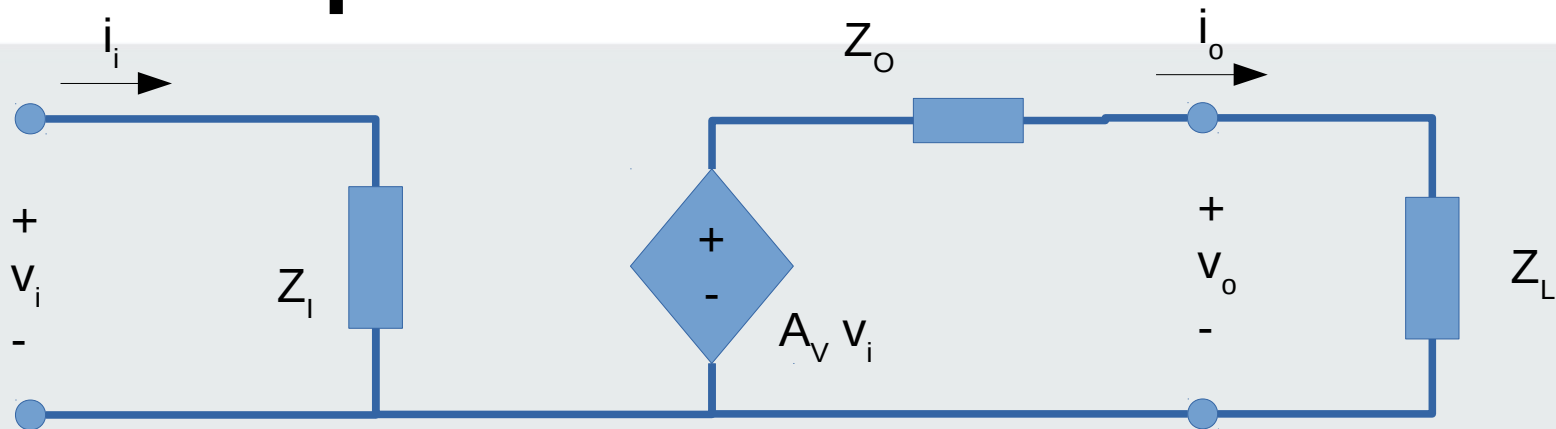

Problem: because Z_o is high, a common load Z_L gets a small voltage only!


$$v_o = \frac{Z_L}{Z_L + Z_o} A_v v_i$$

This output voltage divider wastes the high voltage gain A_v :-)

The common drain amplifier

Goal: supply enough current to load

Common (to input and output) drain

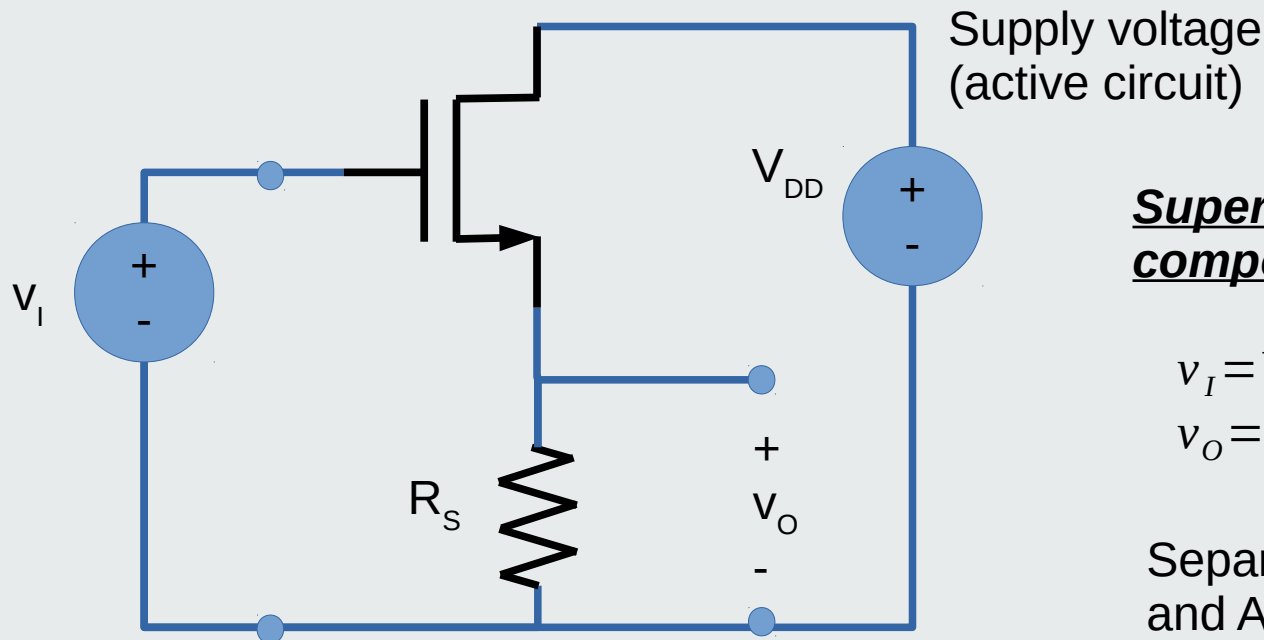


Superposition of DC and AC components

$$v_I = V_I + v_i$$

$$v_O = V_O + v_o$$

Separate DC (operating point) and AC (incremental) analyses

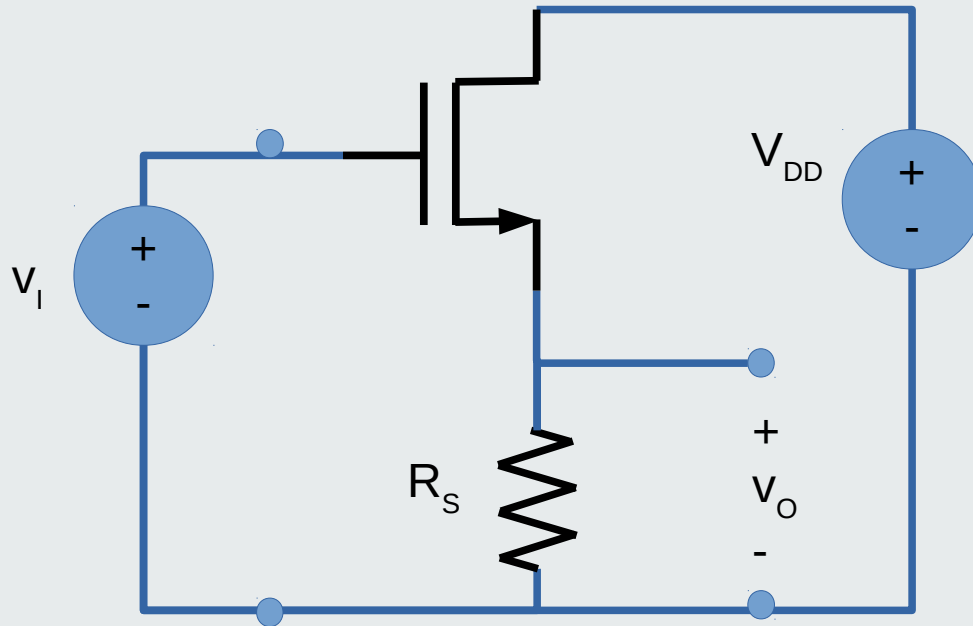The common drain amplifier: operating point



Mesh analysis

$$\begin{cases} -V_I + V_{GS} + R_S I_D = 0 \\ V_O = R_S I_D \end{cases}$$


$$V_{GS} - V_T = \sqrt{\frac{I_D}{k}}$$

$$V_O = V_i - V_T + \frac{1}{2} \left(\sqrt{\frac{4}{kR_S} (V_i - V_T) + \frac{1}{k^2 R_S^2}} + \frac{1}{2kR_S} \right)$$

Emitter follows base voltage with constant difference V_{ON}

Source Follower Circuit

The common drain amplifier: voltage gain

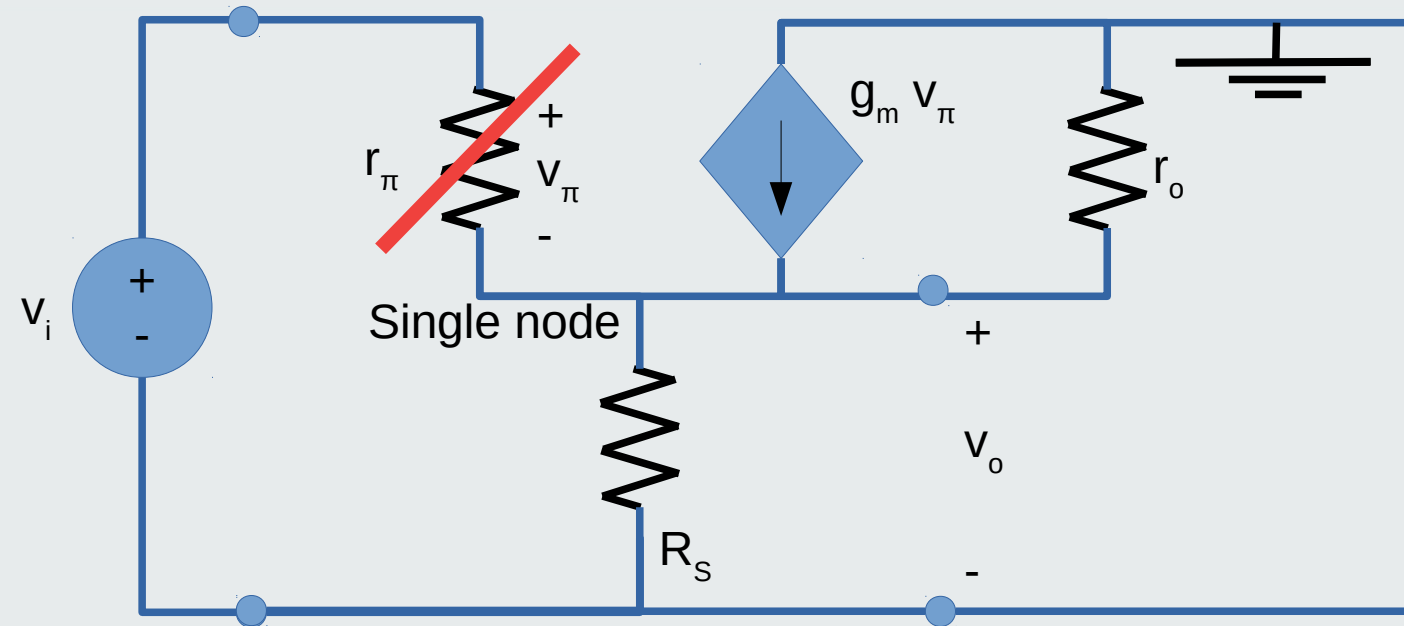

$$g_{\pi} = 0$$

$$g_s = \frac{1}{R_S}$$


$$g_o = \frac{1}{r_o}$$

$$\frac{v_o}{v_i} = \frac{g_m}{g_s + g_o + g_m} \approx 1$$

$$g_s, g_o \ll g_m$$

Use BJT model with infinite input resistance

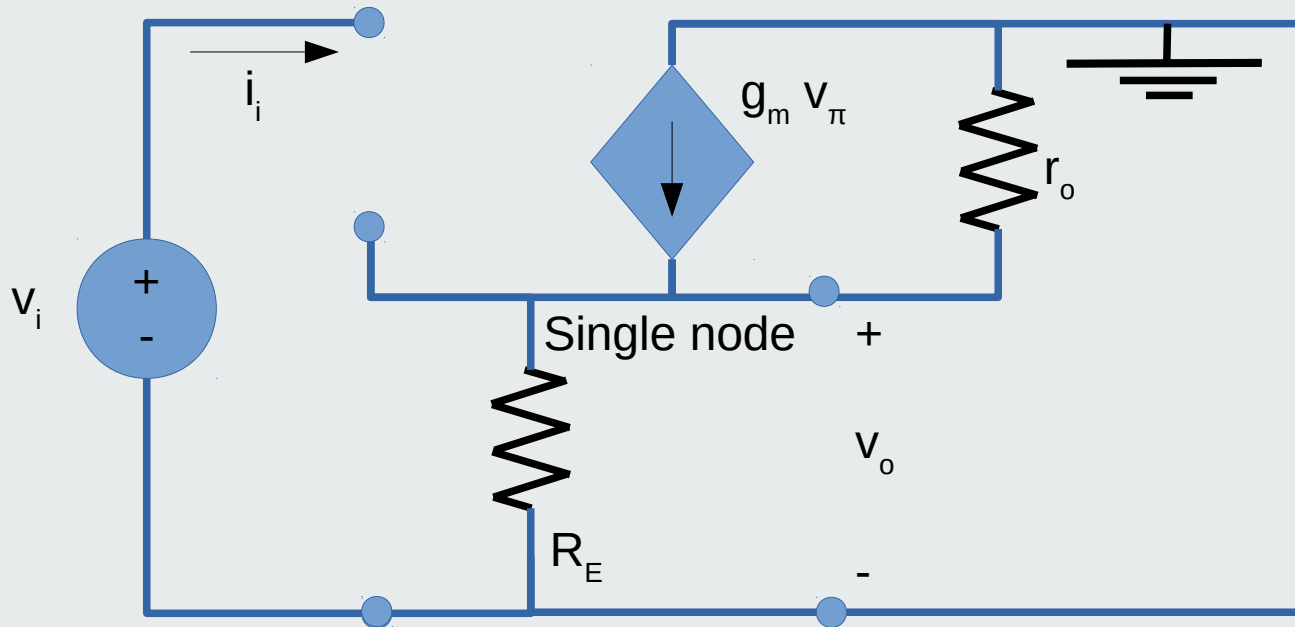The common collector amplifier: input impedance




$$Z_I = \frac{v_i}{i_i}$$

$$i_i = 0$$

$$Z_I = \infty$$

Use BJT model with infinite input impedance

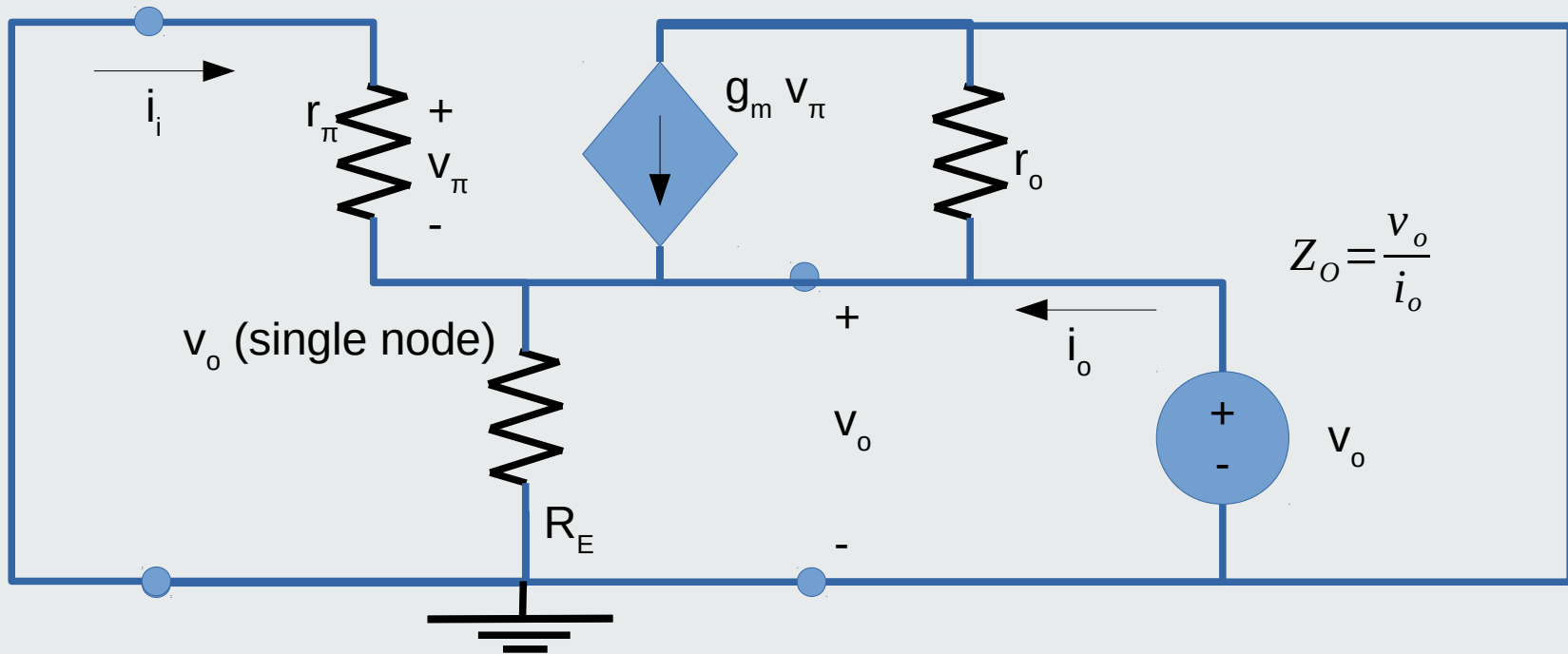The common collector amplifier: output impedance




$$g_\pi = 0$$

Use BJT model with infinite input resistance

$$Z_O = \frac{v_o}{i_o} = \frac{1}{g_s + g_o + g_m}$$

$$g_s, g_o \ll g_m \Rightarrow Z_O \approx \frac{1}{g_m} \quad \text{LOW!}$$

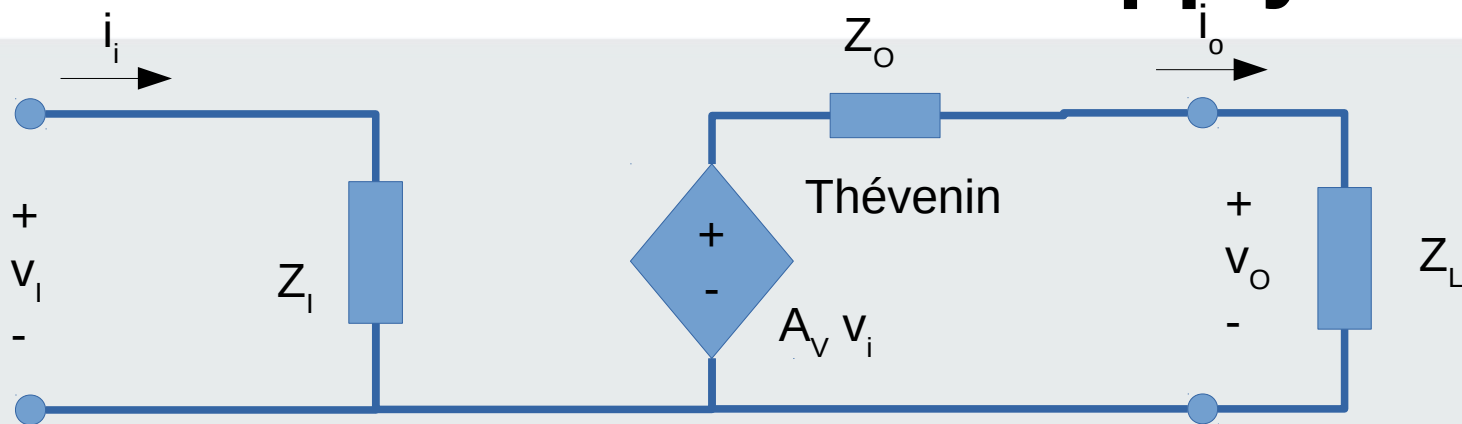Common collector amplifier: solves current supply



Common Source

$$v_o = \frac{Z_L}{Z_L + Z_O} A_V v_i$$

Common Drain

$$A_V \approx 1$$

$$Z_O \ll Z_L$$

Depends
On Z_L !

$$A_V' = \frac{Z_L}{Z_L + Z_O} A_V$$

Effective Gain

$A_V' \approx 1$ Unaffected by Z_L !

Depends
On Z_O !

$$i_o = \frac{v_o}{Z_L} = \frac{A_V}{Z_L + Z_O} v_i$$


Load Current

$$i_o = \frac{v_o}{Z_L} = \frac{A_V}{Z_L} v_i$$

Unaffected by Z_O !

Good voltage amplifier

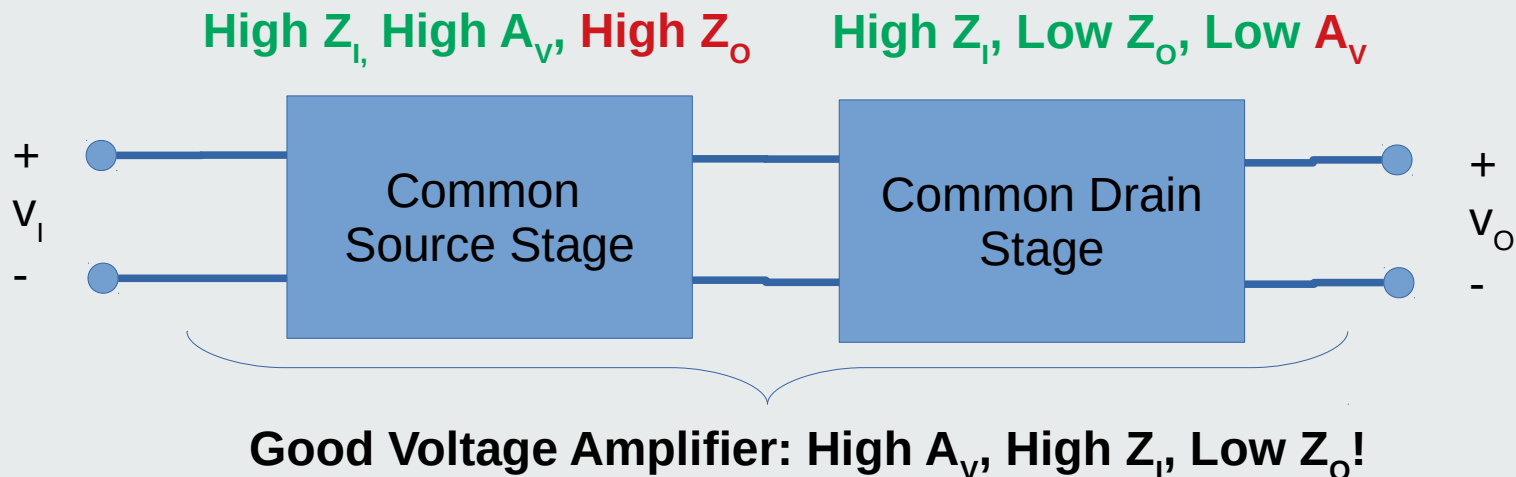- Input is voltage
- Output is voltage
- Z_i should be high to not degrade input voltage
- Z_o should be low to not degrade output signal
- A_v should be high because we want to amplify



Conclusion

- MOSFET amplifiers presented
- Common source amplifier
 - High gain, input and output impedances
 - High output impedance not good for voltage amplifier
- Common drain amplifier
 - Low gain, high input impedance and low output impedances
 - Low gain is not good for voltage amplifier
- Combining common source and common drain stages results in a good voltage amplifier design